

# NATIONAL UNIVERSITY OF SCIENCES AND TECHNOLOGY

COLLEGE OF ELECTRICAL AND MECHANICAL ENGINEERING

---

*Network Analysis*

*Experiment # 1*

*THEVENIN THEOREM*

*GROUP MEMBERS:*

1) \_\_\_\_\_

2) \_\_\_\_\_

3) \_\_\_\_\_

4) \_\_\_\_\_

***Objectives:***

- *To verify Thevenin theorem.*
- *To draw Thevenin equivalent of a passive resistive network.*

*Instructor:* \_\_\_\_\_

*Date:* \_\_\_\_\_

## THEORY

Any two terminal, bilateral, linear networks can be replaced by an equivalent voltage source in series with an equivalent resistance connected across the load.

The load current is given by

$$I_L = V_{TH} / (R_{TH} + R_L)$$

## EQUIPMENT

Power supply	Variable resistor
Digital multimeter	Jumper wires
Resistors: 10K $\Omega$ (3), 4.7 K $\Omega$ , 1 K $\Omega$	Bread board

## CIRCUIT DIAGRAM



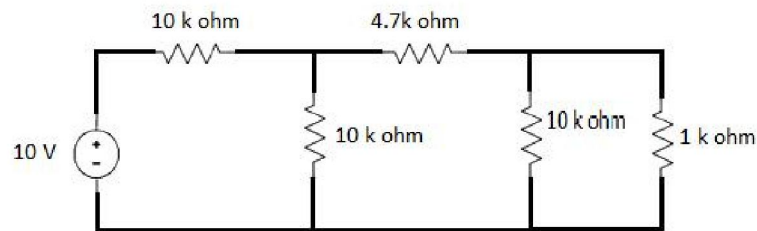



Figure 1: Actual Network

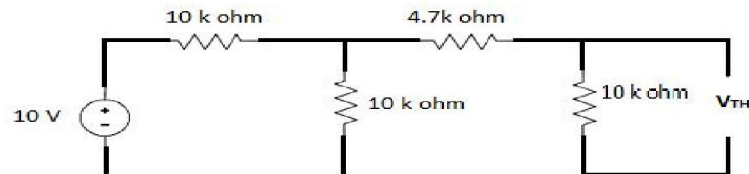

**Figure 2: Measuring  $V_{TH}$**

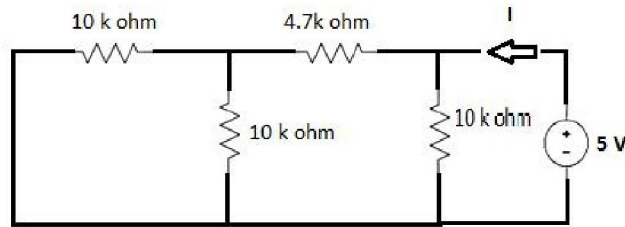

**Figure 3: Finding  $R_{TH}$**

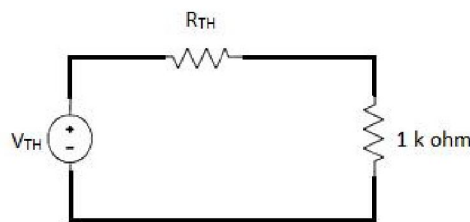

**Figure 4: Thevenin Equivalent Circuit**

## PROCEDURE

1. Connect the components as shown in Figure 1.
2. Measure the voltage ( $V_{L1}$ ) and current ( $I_{L1}$ ) in 1 k $\Omega$  resistance and note these values.
3. Remove 1 k $\Omega$  resistor as shown in Figure 2 and find  $V_{TH}$  across the open circuit terminals from where 1 k $\Omega$  was removed.
4. Connect the circuit according to Figure 3 and measure the current  $I$  to find  $R_{TH}$ .
5. Now connect the circuit as shown in Figure 4 by changing resistance of variable resistor equal to  $R_{TH}$  and voltage of power supply adjusted to  $V_{TH}$ .
6. With this Thevenin equivalent circuit, measure the voltage ( $V_{L2}$ ) and current ( $I_{L2}$ ) in 1 k $\Omega$  resistance and note these values.
7. Compare  $V_{L2}$  and  $I_{L2}$  with  $V_{L1}$  and current  $I_{L1}$ . If these values are same, Thevenin theorem is verified.

## RESULTS

	Theoretical Results	Measured Results
$V_{L1}$		
$I_{L1}$		
$V_{TH}$		
$R_{TH}$		
$V_{L2}$		
$I_{L2}$		