

## Lecture 10b


### EE-215 Electronic Devices and Circuits

Asst Prof Muhammad Anis Chaudhary

## BJT: Device Structure and Physical Operation

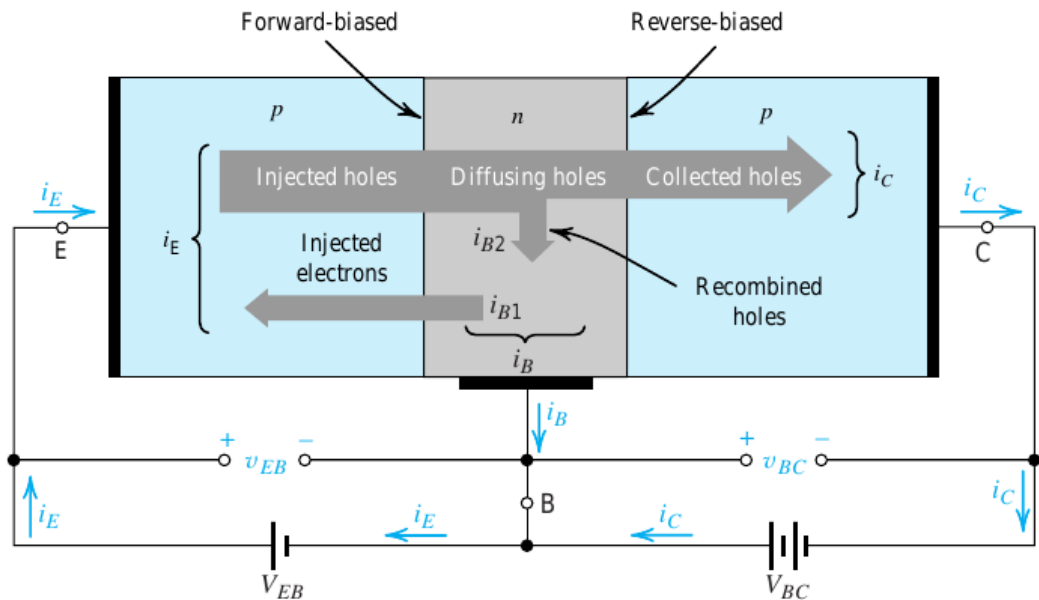
### The pnp Transistor

- figure shows a pnp transistor biased to operate in the active mode



- Figure 6.10 Current flow in a pnp transistor biased to operate in the active mode.

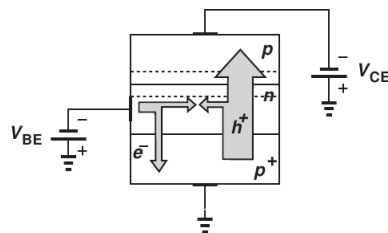
- to achieve active mode of operation, EBJ is forward-biased while CBJ is reverse-biased
  - Unlike the npn transistor, current in the pnp transistor
    - is mainly conducted by holes, injected from the emitter
      - into the base as a result of the forward-bias voltage  $v_{EB}$



pnp (Active Mode: EBJ=Forward-biased  
CBJ=Reverse-biased)


- These holes injected into the base diffuse through the
  - base region into the depletion region of CBJ and are

- then swept away into the collector region under the
  - influence of the electric field, resulting in  $i_C$
- A small number of base majority carriers (electrons) are
  - injected into the emitter (forming  $i_{B1}$ ) or recombined with the
    - holes in the base region (forming  $i_{B2}$ ), thus creating the base current ( $i_B = i_{B1} + i_{B2}$ )
  - thus the pnp transistor operates in a manner similar to that of the npn transistor
    - $\Rightarrow$  the current-voltage relations for the pnp transistor are
      - identical to that of the npn transistor except that  $v_{BE}$  has to be replaced by  $v_{EB}$

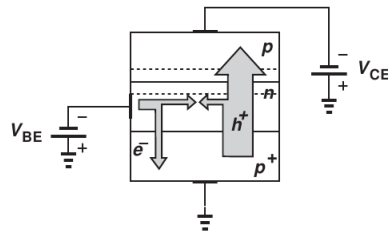

pnp (Active Mode: EBJ=Forward-biased  
CBJ=Reverse-biased)

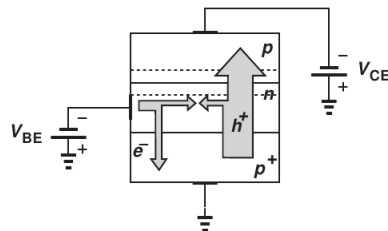- $\Rightarrow$  for a pnp transistor
  - $i_C = I_S e^{v_{EB}/V_T}$
  - $i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{EB}/V_T}$
  - $i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{EB}/V_T}$
  - $i_E = i_C + i_B$
  - where  $\alpha = \frac{\beta}{\beta+1}$ ,  $\beta = \frac{\alpha}{1-\alpha}$



pnp (Active Mode: EBJ=Forward-biased  
CBJ=Reverse-biased)

- Also the large signal operation of a pnp device in active mode can be modeled as




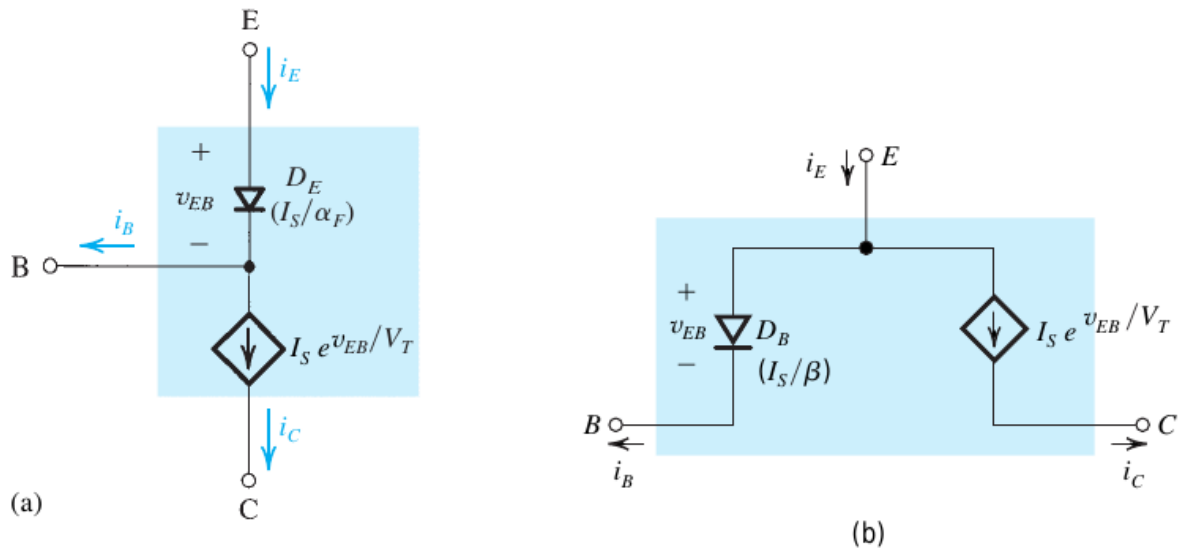


Figure 6.11 Two large-signal models for the pnp transistor operating in the active mode.

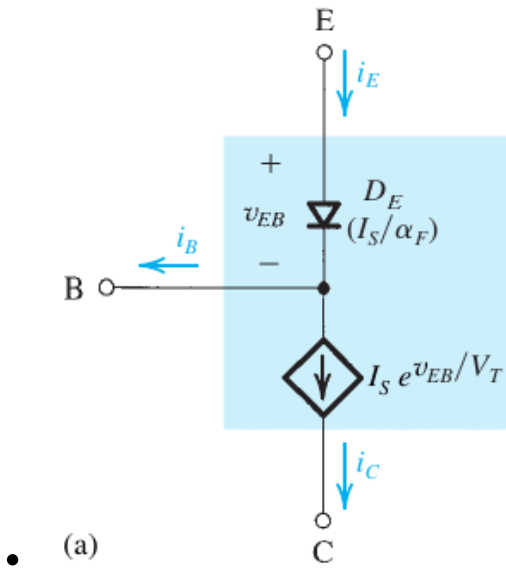


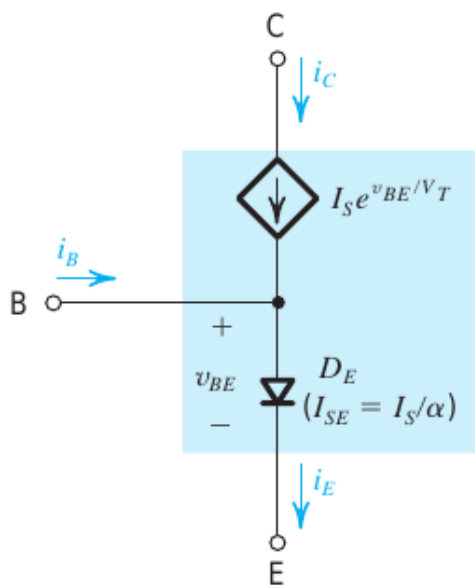

- The npn Transistor

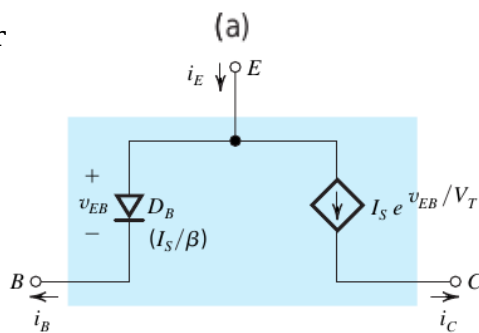


- The pnp Transistor

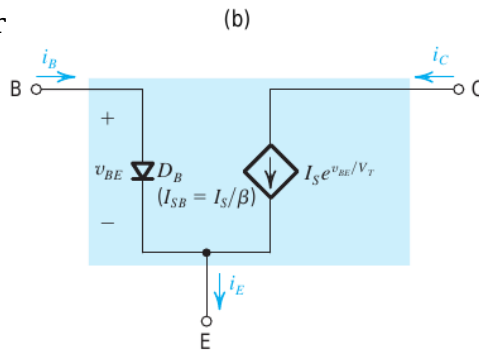


- The npn Transistor

(c)

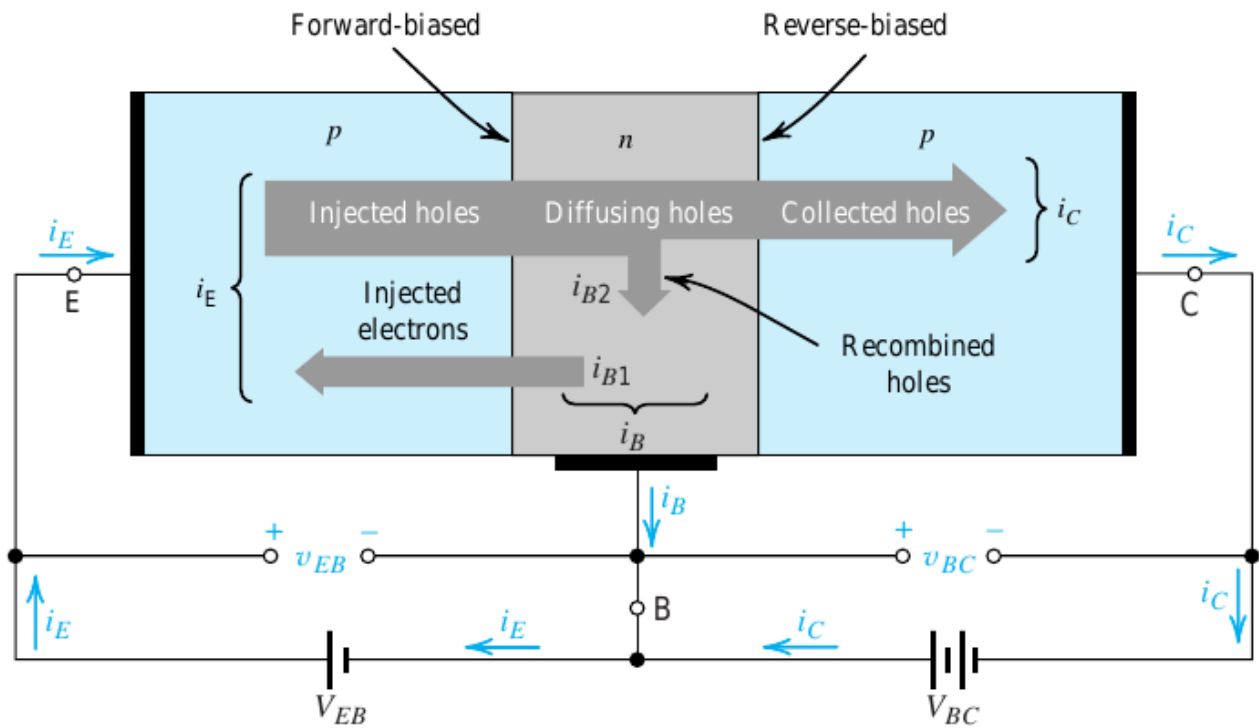


**Figure 6.10** Current flow in a *pnp* transistor biased to operate in the active mode.

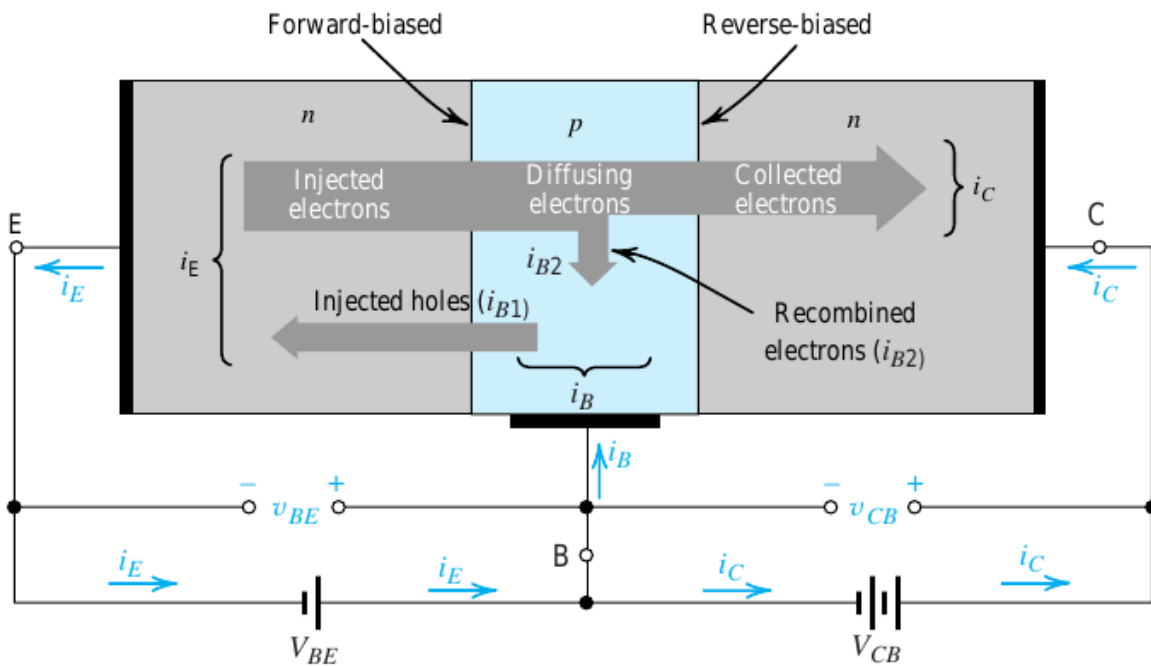

**Figure 6.3** Current flow in an *nnp* transistor biased to operate in the active mode. (Reverse current components due to drift of thermally generated minority carriers are not shown.)

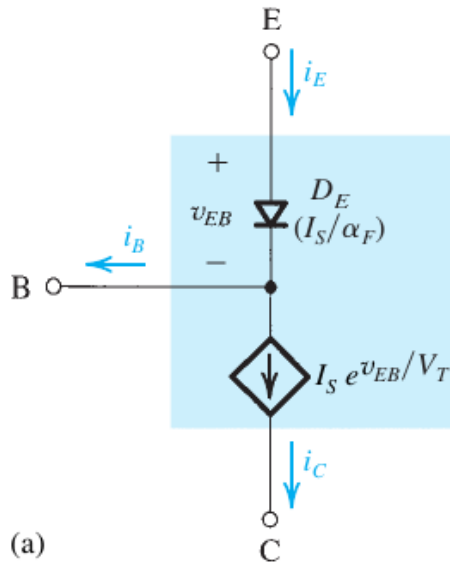
**Exercise 6.10**

- Consider the model in Fig. 6.11(a) applied in the case of a pnp transistor whose base is grounded, the emitter is fed by a constant-current source that supplies a  $2\text{mA}$  current into the emitter terminal, and the collector is connected to a  $-10\text{V}$  dc supply. Find the emitter voltage, the base current, and the collector current if for this transistor  $\beta = 50$  and  $I_S = 10^{-14}\text{A}$ .


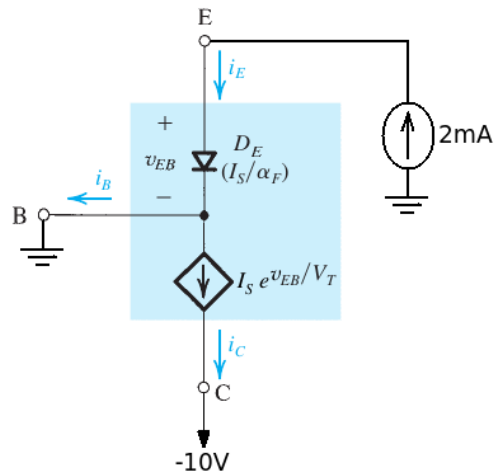
### Solution: Exercise 6.10

- here  $\beta = 50$ ,  $I_S = 10^{-14}\text{A}$ ,  $i_E = 2\text{mA}$ 
  - $v_E = ?$ ,  $i_B = ?$ ,  $i_C = ?$ 
    - $\alpha = \frac{\beta}{\beta+1} = \frac{50}{51} = 0.9804$
    - $\Rightarrow i_E = 2\text{mA} = \frac{i_C}{\alpha} = \frac{i_C}{0.9804}$
    - or  $i_C = 0.9804i_E = 0.9804 \times 2\text{mA} = 1.9608\text{mA}$
    - $i_B = \frac{i_C}{\beta} = \frac{1.9608\text{mA}}{50} = 39.216\mu\text{A}$
    - $I_S e^{v_{EB}/V_T} = i_C = 1.9608\text{mA}$
    - $\Rightarrow v_{EB} = V_T \ln \frac{1.9608\text{mA}}{I_S} = 0.65004\text{V}$
    - $\Rightarrow v_E - v_B = v_E - 0 = 0.65004\text{V}$  or  $v_E = 0.65004\text{V}$



### Exercise 6.11

- For a pnp transistor having  $I_S = 10^{-11} A$  and  $\beta = 100$ , calculate  $v_{EB}$  for  $i_C = 1.5 A$ .

### Solution: Exercise 6.11


- here  $I_S = 10^{-11} A$ ,  $\beta = 100$ ,  $i_C = 1.5 A$ 
  - $v_{EB} = ?$
  - $i_C = I_S e^{v_{EB}/V_T}$
  - $\Rightarrow 1.5 = 10^{-11} e^{v_{EB}/V_T}$
  - or  $e^{v_{EB}/V_T} = \frac{1.5}{10^{-11}}$
  - take natural log on both sides
  - $\frac{v_{EB}}{V_T} = \ln\left(\frac{1.5}{10^{-11}}\right)$
  - $v_{EB} = V_T \ln\left(\frac{1.5}{10^{-11}}\right) = 25m \ln\left(\frac{1.5}{10^{-11}}\right) = 0.64335V$

## BJT:

### Current-Voltage Characteristics

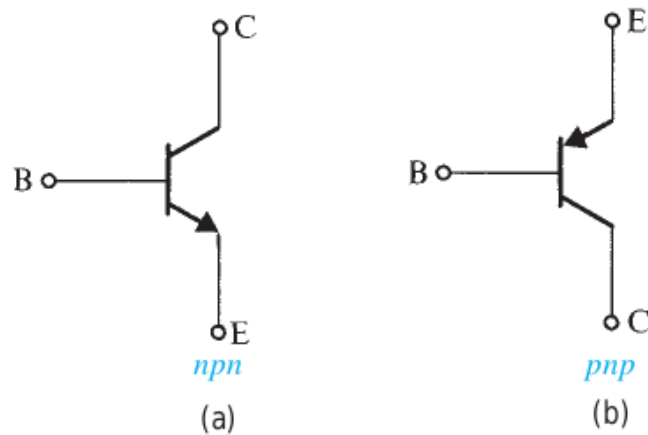
#### Circuit Symbols and Conventions

- the circuit symbols for an npn and pnp transistor are indicated in fig



○ **Figure 6.12** Circuit symbols for BJTs.

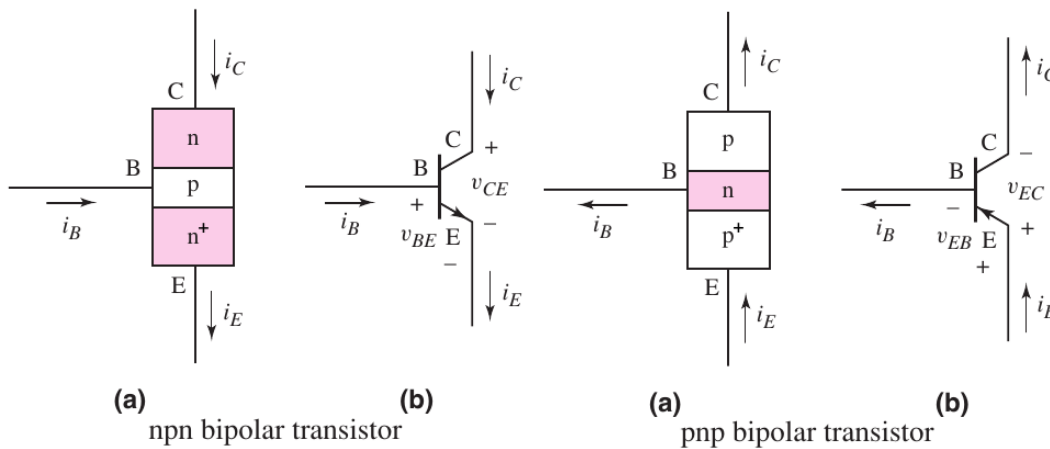- In both symbols, the emitter is distinguished by an arrowhead.
- this distinction is important as practical BJT is not a symmetrical device



- The polarity of the device i.e. npn or pnp
  - is indicated by the direction of the arrowhead on the emitter.
  - This arrowhead points in the direction of the conventional current flow.
- Recall that in npn BJT, current flows from the collector to emitter
  - (as the electrons are flowing from emitter to the collector)
  - in a pnp BJT, the current flows from emitter to the collector
    - (as the holes flow from emitter to the collector)
- A summary of the BJT current-voltage relationships in the active mode of operation can be given as



**Table 6.2** Summary of the BJT Current–Voltage Relationships in the Active Mode

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left(\frac{I_S}{\beta}\right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left(\frac{I_S}{\alpha}\right) e^{v_{BE}/V_T}$$

Note: For the pnp transistor, replace  $v_{BE}$  with  $v_{EB}$ .


$$i_C = \alpha i_E \quad i_B = (1 - \alpha) i_E = \frac{i_E}{\beta + 1}$$

$$i_C = \beta i_B \quad i_E = (\beta + 1) i_B$$


$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1}$$

$$V_T = \text{thermal voltage} = \frac{kT}{q} \approx 25 \text{ mV at room temperature}$$

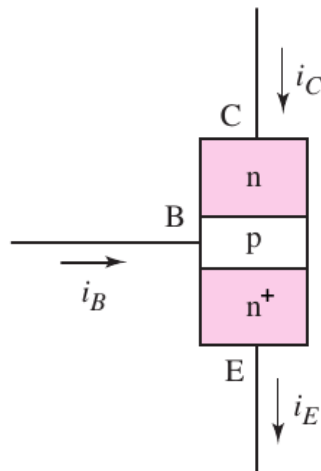- Note that an npn transistor, whose EBJ is forward-biased,
  - will operate in the active mode as long as
    - the collector voltage doesnot fall below that of the base by
      - more than approximately 0.4V
      - i.e.  $v_{CB} > -0.4V$




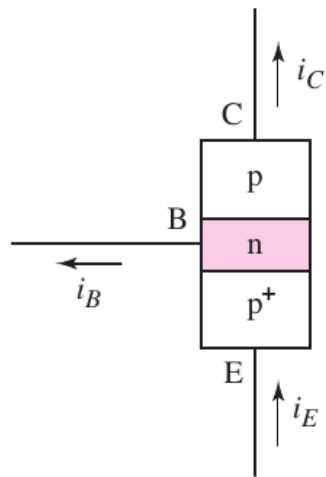- for a pnp transistor whose EBJ is forward-biased
  - will operate in the active mode as long as
    - the collector voltage is not allowed to rise above that
      - of the base by more than 0.4V
      - i.e.  $v_{CB} < 0.4V$
      - or  $v_{BC} > -0.4V$


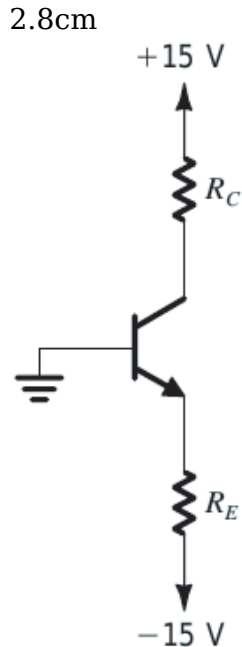
### Example 6.2

- The transistor in the circuit of Fig. 6.14(a) has  $\beta = 100$  and exhibits a  $v_{BE}$  of  $0.7V$  at  $i_C = 1mA$ . Design the circuit so that a current of  $2mA$  flows through the collector and a voltage of  $+5V$  appears at the collector.



### Solution: Example 6.2


- here npn,  $\beta = 100$ ,  $v_{BE1} = 0.7V$  at  $i_{C1} = 1mA$ 
  - $i_C = 2mA$ ,  $v_C = 5V$ 
    - $R_C = ?$ ,  $R_E = ?$
    - As  $i_C = I_S e^{v_{BE}/V_T}$
    - $\Rightarrow i_{C1} = I_S e^{v_{BE1}/V_T}$ ,  $i_{C2} = I_S e^{v_{BE2}/V_T}$
    - dividing
    - $\frac{i_{C2}}{i_{C1}} = \frac{I_S e^{v_{BE2}/V_T}}{I_S e^{v_{BE1}/V_T}} = e^{(v_{BE2} - v_{BE1})/V_T}$

- take natural log on both sides

- $\ln \frac{i_{C2}}{i_{C1}} = (v_{BE2} - v_{BE1}) / V_T$

- $v_{BE2} - v_{BE1} = V_T \ln \frac{i_{C2}}{i_{C1}}$

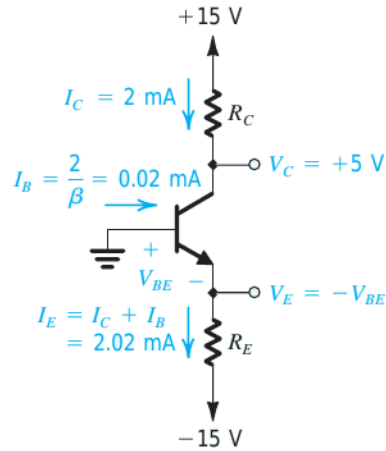- $v_{BE2} = v_{BE1} + V_T \ln \frac{i_{C2}}{i_{C1}}$



- $v_{BE2} = v_{BE1} + V_T \ln \frac{i_{C2}}{i_{C1}}$

o here  $v_{BE1} = 0.7V$  at  $i_{C1} = 1mA$ ,  $i_{C2} = i_C = 2mA$ ,  $v_{BE2} = v_{BE} = ?$

- $\Rightarrow v_{BE} = v_{BE2} = 0.7 + (25m) \ln \frac{2m}{1m} = 0.717V$

- As the base is grounded

- $\Rightarrow v_{BE} = 0.717 = v_B - v_E = 0 - v_E$


- or  $v_E = -0.717V$

- $\alpha = \frac{\beta}{\beta+1} = \frac{100}{101} = 0.9901$

- $i_E = \frac{i_C}{\alpha} = \frac{2m}{0.9901} = 2.02mA$


- By ohm's law

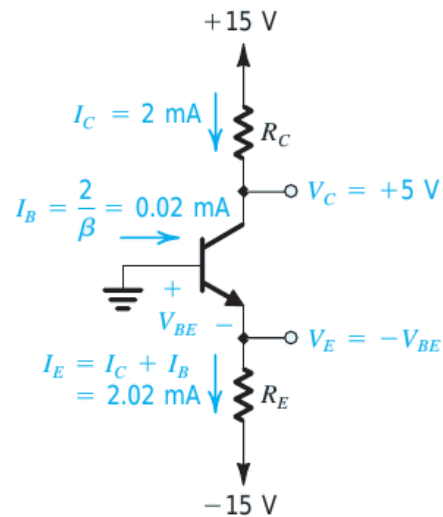- $R_C = \frac{15 - v_C}{i_C} = \frac{15 - 5}{2m} = \frac{10}{2m} = 5k\Omega$




- also by ohm's law
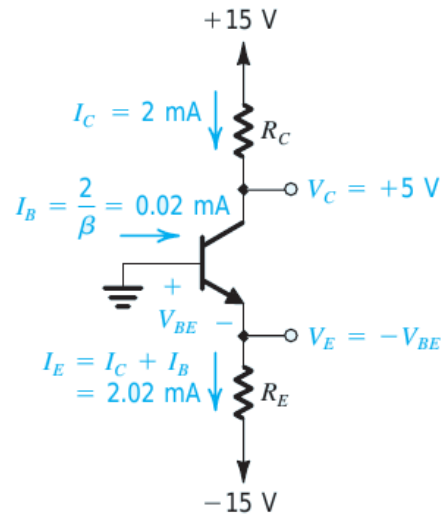
$$\circ R_E = \frac{v_E - (-15)}{i_E} = \frac{-0.717 - (-15)}{2.02\text{m}} = \frac{-0.717 + 15}{2.02\text{m}} = 7.0708\text{ k}\Omega$$


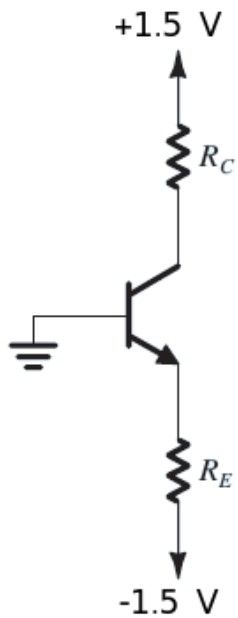
### Exercise D6.12

- Repeat Example 6.2 for a transistor fabricated in a modern integrated-circuit process. Such a process yields devices that exhibit larger  $v_{BE}$  at the same  $i_C$  because they have much smaller junction areas. The dc power supplies utilized in modern IC technologies fall in the range of  $1\text{ V}$  to  $3\text{ V}$ . Design a circuit similar to that shown in Fig. 6.14 except that now the power supplies are  $\pm 1.5\text{ V}$  and the BJT has  $\beta = 100$  and exhibits  $v_{BE}$  of  $0.8\text{ V}$  at  $i_C = 1\text{ mA}$ . Design the circuit so that a current of  $2\text{ mA}$  flows through the collector and a voltage of  $+0.5\text{ V}$  appears at the collector.



### Solution: Exercise D6.12

- here  $\beta = 100$ ,  $v_{BE1} = 0.8V$  at  $i_{C1} = 1mA$

- $i_C = 2mA$ ,  $v_C = 0.5V$

- By ohm's law

- $R_C = \frac{1.5 - v_C}{i_C} = \frac{1.5 - 0.5}{2m} = 500\Omega$

- As  $v_{BE} = v_{BE1} + V_T \ln \frac{i_C}{i_{C1}}$


- $\Rightarrow v_{BE} = 0.8 + (25m) \ln\left(\frac{2m}{1m}\right) = 0.81733V$

- or  $v_{BE} = 0.81733 = v_B - v_E = 0 - v_E = -v_E$


- $\Rightarrow v_E = -0.81733V$

- By ohm's law

- $R_E = \frac{v_E - (-1.5)}{i_E}$

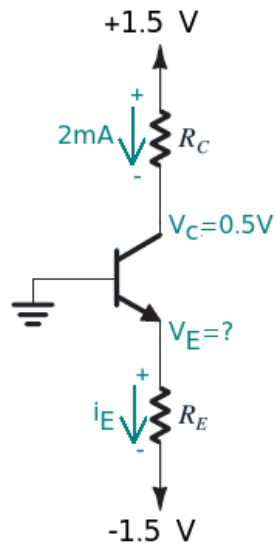


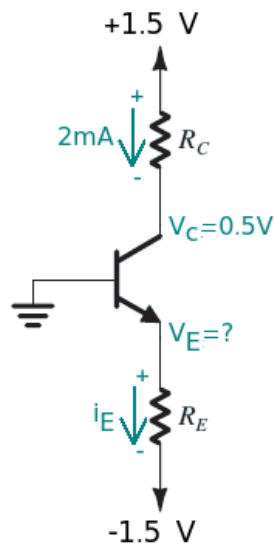- As  $i_E = \frac{i_C}{\alpha} = \frac{2m}{\alpha}$  and  $\alpha = \frac{\beta}{\beta+1} = \frac{100}{101} = 0.9901$ 
  - $\Rightarrow i_E = \frac{2m}{\alpha} = \frac{2m}{0.9901} = 2.02mA$ 
    - $\Rightarrow R_E = \frac{v_E - (-1.5)}{i_E} = \frac{-0.81733 - (-1.5)}{2.02m} = \frac{-0.81733 + 1.5}{2.02m} = 337.96\Omega$



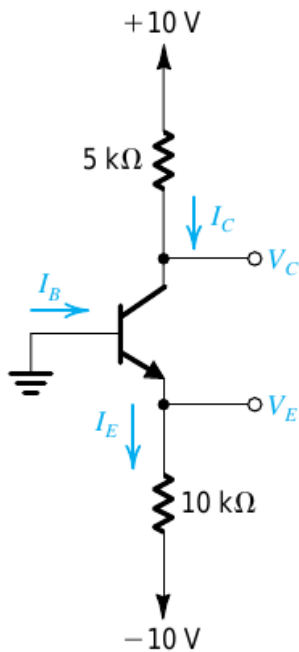
### Exercise 6.13

- In the circuit shown in Fig. E6.13, the voltage at the emitter was measured and found to be  $-0.7V$ . If  $\beta = 50$ , find  $I_E$ ,  $I_B$ ,  $I_C$ , and  $V_C$ .



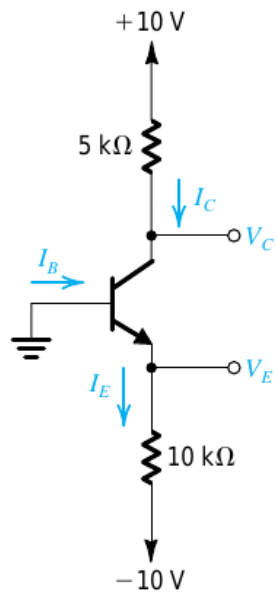
### Solution: Exercise 6.13

- here  $v_E = -0.7V$ ,  $\beta = 50$ 
  - $I_E = ?$ ,  $I_B = ?$ ,  $I_C = ?$ , and  $V_C = ?$ .
    - As  $v_E = -0.7V$  and  $v_B = 0V$ 
      - $\Rightarrow v_{BE} = v_B - v_E = 0 - (-0.7) = 0.7V$
    - by ohm's law
      - $i_E = \frac{v_E - (-10)}{10k} = \frac{-0.7 + 10}{10k} = 0.93mA$
    - as  $i_E = \frac{i_C}{\alpha}$ 
      - $\Rightarrow i_C = \alpha i_E$  where  $\alpha = \frac{\beta}{\beta + 1} = \frac{50}{51} = 0.98039$
      - $i_C = \alpha i_E = 0.98039 \times 0.93m = 0.91176mA$
    - $i_B = \frac{i_C}{\beta} = \frac{0.91176m}{50} = 18.235\mu A$



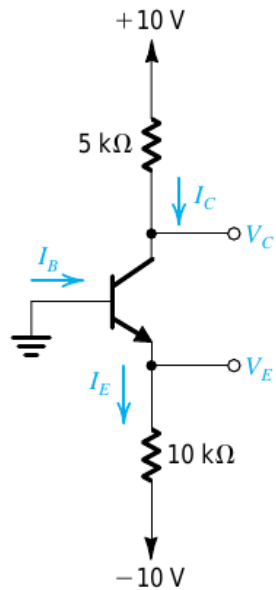
- thus  $i_E = 0.93mA$ ,  $i_C = 0.91176mA$ ,  $i_B = 18.235\mu A$ 
  - by ohm's law
    - $10 - v_C = (5k)i_C = (5k)0.91176m$ 
      - $10 - v_C = 4.559$
      - or  $10 - 4.559 = v_C$
      - $v_C = 5.441V$


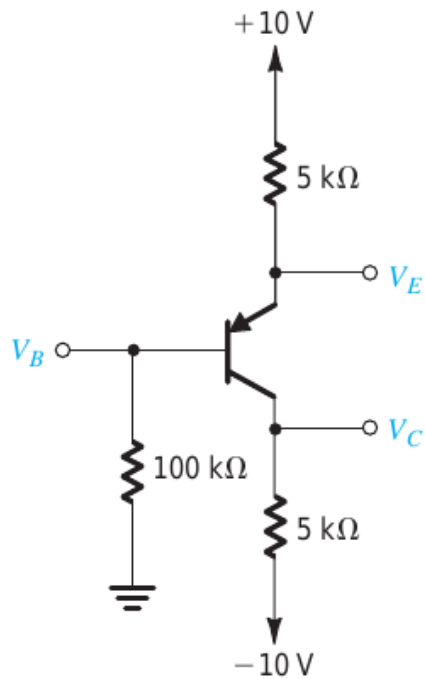
### Exercise 6.14

- In the circuit shown in Fig. E6.14, measurement indicates  $V_B$  to be  $+1.0V$  and  $V_E$  to be  $+1.7V$ . What are  $\alpha$  and  $\beta$  for this transistor? What voltage  $V_C$  do you expect at the collector?





### Solution: Exercise 6.14

- here  $v_B = 1V$  ,  $v_E = 1.7V$ 
  - $\alpha = ?$  ,  $\beta = ?$  ,  $v_C = ?$

■ by ohm's law,

$$\blacksquare i_B = \frac{v_B}{100k} = \frac{1}{100k} = 10\mu A$$

$$\blacksquare \text{ and } i_E = \frac{10 - v_E}{5k} = \frac{10 - 1.7}{5k} = 1.66mA$$

■ As  $i_E = i_C + i_B$


$$\blacksquare \Rightarrow i_C = i_E - i_B = 1.66m - 10\mu = 1.65mA$$

■ as  $i_B = \frac{i_C}{\beta} \Rightarrow \beta = \frac{i_C}{i_B}$

$$\blacksquare \Rightarrow \beta = \frac{i_C}{i_B} = \frac{1.65m}{10\mu} = 165$$

■ as  $i_E = \frac{i_C}{\alpha}$
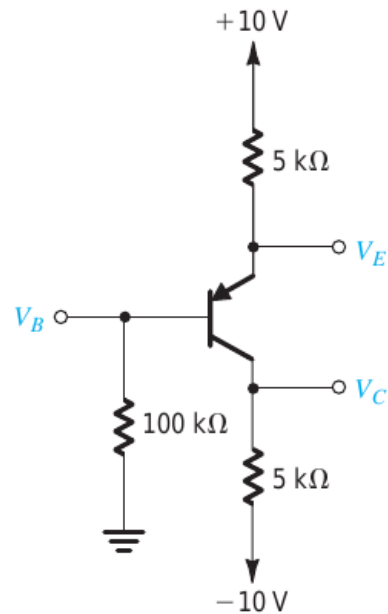
$$\blacksquare \Rightarrow \alpha = \frac{i_C}{i_E} = \frac{1.65m}{1.66m} = 0.99398$$




- by ohm's law

- $v_C - (-10) = 5k(i_C) = 8.25V$

- $v_C + 10 = 8.25$

- or  $v_C = 8.25 - 10 = -1.75V$

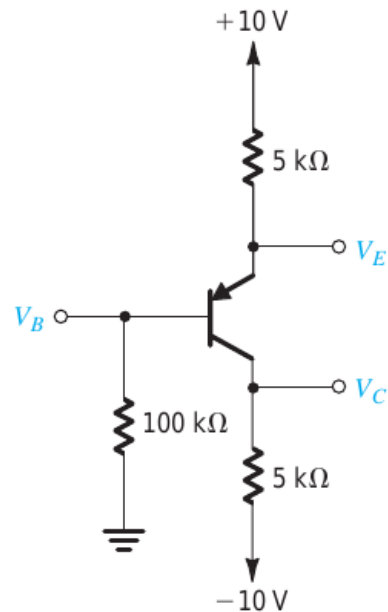

## BJT: Current-Voltage Characteristics

### Graphical Representation of Transistor Characteristics

- for an npn transistor,  $i_C = I_S e^{v_{BE}/V_T}$ 
  - this relation can be represented graphically as
  - also  $i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$  and  $i_E = \frac{I_S}{\alpha} e^{v_{BE}/V_T}$

- $\Rightarrow i_B - v_{BE}$  and  $i_E - v_{BE}$  characteristics are also exponential but with different scale currents
  - $\frac{I_S}{\beta}$  for  $i_B$  and  $\frac{I_S}{\alpha}$  for  $i_E$

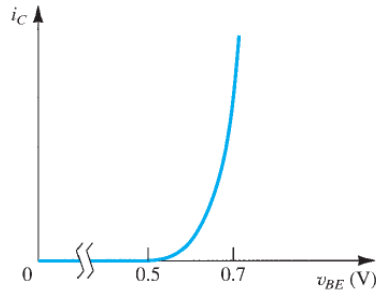


Figure 6.15 The  $i_C - v_{BE}$  characteristic for an npn transistor.

- As the constant of the exponential characteristic is  $\frac{1}{V_T} = \frac{1}{25m} = 40$ 
  - $\Rightarrow$  the curve rises very sharply (you can verify this in matlab/octave)
- for  $v_{BE}$  smaller than about 0.5V (the cut-in voltage of EBJ), the current is negligibly small
  - Note that for most of the normal range,
    - $v_{BE}$  lies in the range of 0.6V to 0.8V
    - $\Rightarrow$  In performing rapid first order dc calculations,
      - we can utilize the constant-voltage drop model
      - by assuming  $v_{BE} \approx 0.7V$


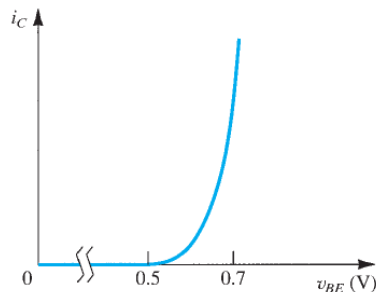



Figure 6.15 The  $i_C - v_{BE}$  characteristic for an npn transistor.

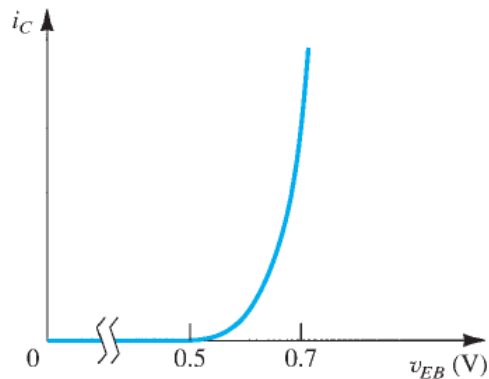- for a pnp transistor,  $i_C = I_S e^{v_{EB}/V_T}$ 
  - $\Rightarrow i_C - v_{EB}$  characteristics will be identical to that of the npn transistor with  $v_{BE}$  replaced with  $v_{EB}$



The  $i_C$ - $v_{EB}$  characteristic for a pnp transistor.

- Note that for a BJT, the voltage across the emitter-base junction
  - decreases by about 2mV for each rise of  $1^\circ\text{C}$  in temperature,
    - provided the junction is operating at a constant current

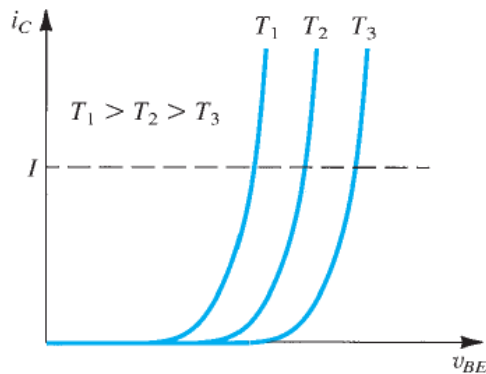

**Figure 6.16** Effect of temperature on the  $i_C$ - $v_{BE}$  characteristic. At a constant emitter current (broken line),  $v_{BE}$  changes by  $-2\text{ mV}/^\circ\text{C}$ .


### Exercise 6.15

- Consider a pnp transistor with  $v_{EB} = 0.7\text{V}$  at  $i_E = 1\text{mA}$ . Let the base be grounded, the emitter be fed by a  $2\text{mA}$  constant-current source, and the collector be connected to a  $-5\text{V}$  supply through a  $1\text{k}\Omega$  resistance. If the temperature increases by  $30^\circ\text{C}$ , find the changes in emitter and collector voltages. Neglect the effect of  $I_{CBO}$


### Solution: Exercise 6.15

- here pnp,  $v_{EB1} = 0.7\text{V}$  at  $i_{E1} = 1\text{mA}$ 
  - change in  $v_E$  and  $v_C$  are ?
    - if  $i_{CBO}$  is neglected
      - $\Rightarrow v_C$  will not change with temperature
      - $\Rightarrow$  change in  $v_C$  with temperature = 0
    - as  $v_{EB}$  decreases by 2mV for every  $1^\circ\text{C}$  rise in temperature
      - $\Rightarrow v_{EB}$  decreases by 4mV for  $2^\circ\text{C}$  rise in temperature
      - $\Rightarrow v_{EB}$  decreases by 6mV for  $3^\circ\text{C}$  rise in temperature
      -

⋮

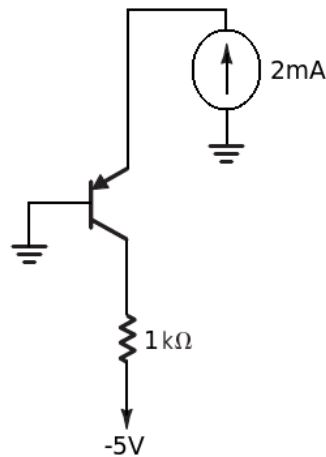


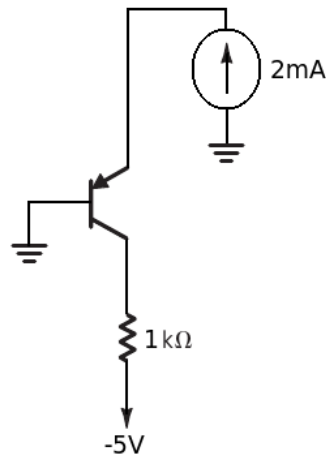- $\Rightarrow v_{EB}$  decreases by 60mV for  $30^\circ C$  rise in temperature
- $v_{EB}$  decreases by 60mV for  $30^\circ C$  rise in temperature
  - as  $v_B = 0 \Rightarrow v_{EB} = v_E - v_B = v_E$ 
    - if  $v_{EB}$  decreases by 60mV  $\Rightarrow v_E$  will also decrease by 60mV



- exact value of  $v_{EB}$  can be determined as follows,
  - As  $i_E = \frac{I_S}{\alpha} e^{v_{EB}/V_T}$ 
    - $\Rightarrow i_{E1} = \frac{I_S}{\alpha} e^{v_{EB1}/V_T}$  ,  $i_{E2} = \frac{I_S}{\alpha} e^{v_{EB2}/V_T}$ 
      - dividing
        - $\frac{i_{E2}}{i_{E1}} = \frac{e^{v_{EB2}/V_T}}{e^{v_{EB1}/V_T}} = e^{(v_{EB2}-v_{EB1})/V_T}$
      - for  $v_{EB1} = 0.7V$  ,  $i_{E1} = 1mA$  ,  $i_{E2} = i_E = 2mA$  ,  
 $v_{EB} = v_{EB2} = ?$ 
        - $\frac{i_{E2}}{i_{E1}} = \frac{2m}{1m} = e^{(v_{EB}-v_{EB1})/V_T} = e^{(v_{EB}-0.7)/25m}$
        - $e^{(v_{EB}-0.7)/25m} = 2$
        - $(v_{EB} - 0.7)/25m = \ln 2$
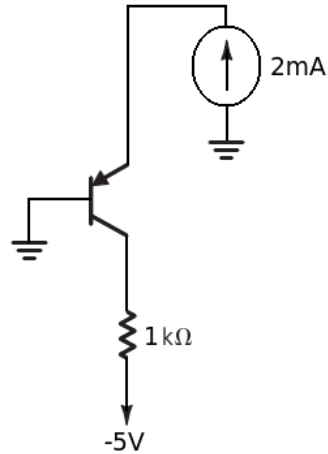
$$\blacksquare v_{EB} = 0.7 + (25m)\ln 2 = 0.71733V$$



$$\bullet v_{EB} = 0.71733V$$

○ when temperature increases by  $30^\circ C$

■  $\Rightarrow v_{EB}$  decreases by 60mV

$$\blacksquare \text{i.e. } v_{EB, (at T+30^\circ C)} = 0.71733 - 60m = 0.65733V$$

$$\blacksquare \Rightarrow v_{EB (at T+30^\circ C)} - v_{EB} = 0.65733 - 0.71733 = -60mV$$