

# Lecture 11b

## EE-215 Electronic Devices and Circuits

Asst Prof Muhammad Anis Chaudhary


---

### Applying the BJT in Amplifier Design

- When operated in active mode, the BJT functions as a voltage-controlled current source.
  - (i.e. the base-emitter voltage  $v_{BE}$  controls the collector current  $i_C$ )
  - this enables us to use the BJT in the design of amplifiers

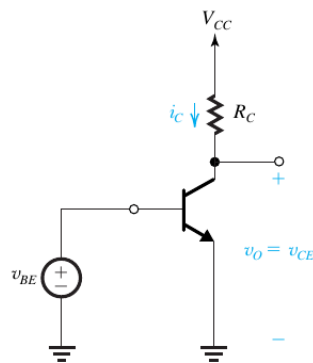
### Obtaining a Voltage amplifier

- A voltage controlled current source can be used as a transconductance amplifier
  - A transconductance amplifier is an amplifier whose input signal is a voltage and output signal is a current
    - we usually are more interested in a voltage amplifier
  - A transconductance amplifier can be converted into a voltage amplifier,
    - by passing the output current through a resistor
    - and taking the voltage across the resistor as output




- in the figure
  - $v_{BE}$  is the input voltage
    - $R_C$  is called the load resistance.
      - $R_C$  converts the collector current  $i_C$  to a voltage  $i_C R_C$
      - $V_{CC}$  is the supply voltage
    - here the output voltage is taken between the collector terminal and the ground (rather than across  $R_C$ )
      - this arrangement enables us to maintain a ground reference through out the circuit
      - $\Rightarrow$

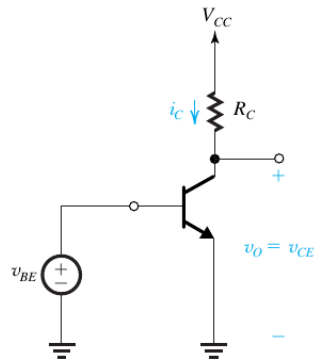- $v_{BE}$  is the input voltage
- $v_{CE}$  is the output voltage




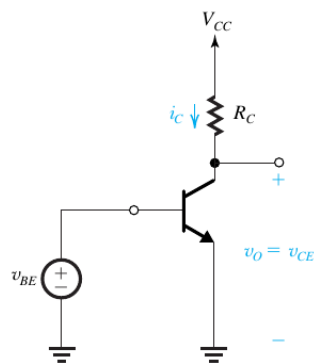- Using KVL, an expression for  $v_{CE}$  can be computed
  - i.e.  $V_{CC} = i_C R_C + v_{CE}$ 
    - or  $v_{CE} = V_{CC} - i_C R_C$
    - $\Rightarrow$  output voltage  $v_{CE}$  is an inverted version of  $i_C R_C$  that is shifted by the constant value of the supply voltage  $V_{CC}$



### The Voltage Transfer Characteristic (VTC)

- VTC is a plot of the output voltage versus the input voltage
  - and it can provide a better insight in to the operation of an amplifier circuit

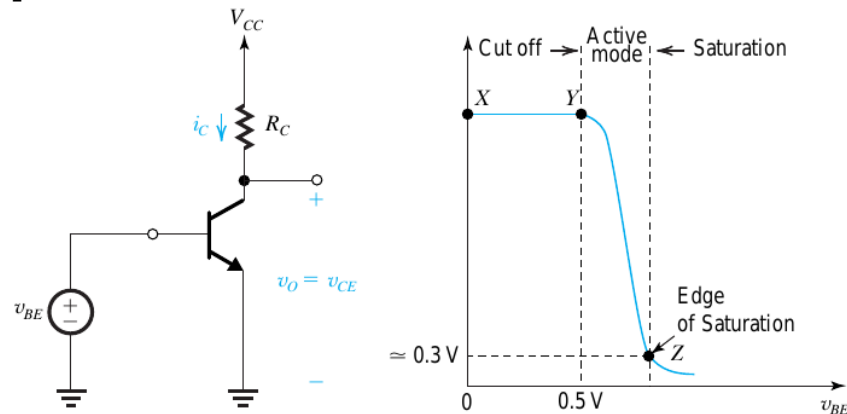


**Figure 6.31** (a) Simple BJT amplifier with input  $v_{BE}$  and output  $v_{CE}$ . (b) The voltage transfer characteristic (VTC) of the amplifier in (a). The three segments of the VTC correspond to the three modes of operation of the BJT.

- Note that for  $v_{BE} < 0.5V$  , the transistor is cut-off  $\Rightarrow i_C = 0$

◦ and  $v_{CE} = V_{CC} - i_C R_C = V_{CC} - (0)R_C = V_{CC}$

- As  $v_{BE}$  exceeds  $0.5V$ , the transistor turns on and  $v_{CE}$  decreases.

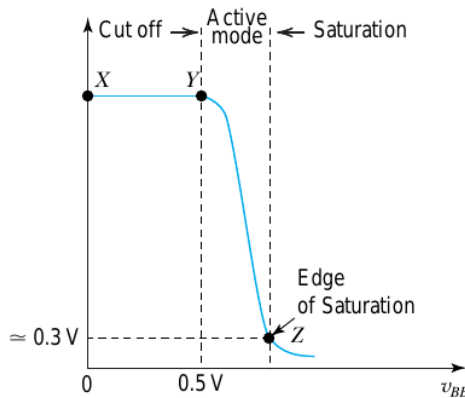
- As initially  $i_C$  is still small
- $\Rightarrow v_{CE}$  is still high
- $\Rightarrow$  BJT is operating in active region (active region:  $v_{CE} \geq 0.3V$ )



- BJT stays in active region as  $v_{BE}$  is increased

- until the value of  $v_{BE}$  is reached for which  $v_{CE}$  becomes lower than  $v_{BE}$  by  $0.4V$  i.e.  $v_{CE} \approx 0.3V$

- this is point Z

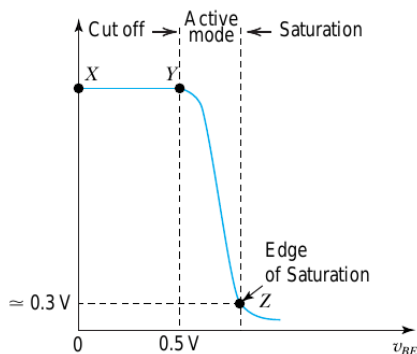


- for  $v_{CE} < 0.3V$  (i.e. beyond point Z), the transistor enters the saturation region,

- from the fig, it is clear that the segment of greatest slope

- (and hence the largest amplifier gain) is that labeled as YZ

- which corresponds to the active mode of operation

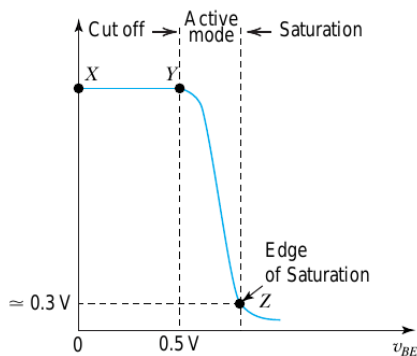
- thus for amplifier application, one will always choose to operate the BJT in active mode



- thus for amplifier application, the BJT will be operated in active mode i.e. in the segment YZ
  - for active mode operation (ignoring base-width modulation or the Early Effect)
    - $i_C = I_S e^{v_{BE}/V_T}$
  - As  $v_{CE} = V_{CC} - i_C R_C$ 
    - $\Rightarrow v_{CE} = V_{CC} - (I_S e^{v_{BE}/V_T}) R_C$
  - $v_{CE} = V_{CC} - R_C I_S e^{v_{BE}/V_T}$
  - Although this is a non-linear relationship, but linear (or almost linear) amplification is possible,
    - by using the technique of biasing the BJT

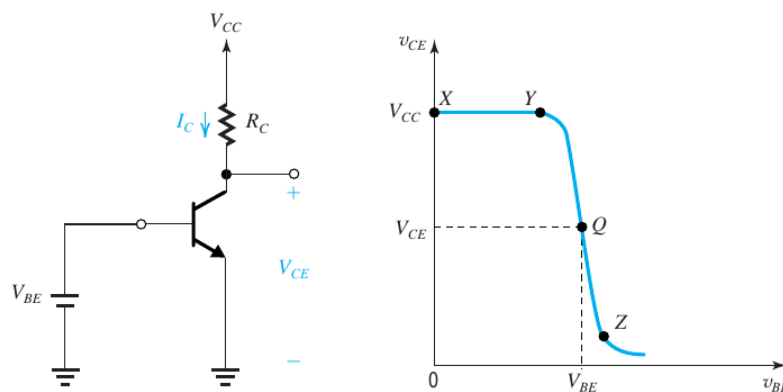
### Biasing the BJT to Obtain Linear Amplification

- Biasing enables us to obtain almost-linear amplification from the BJT



◦ **Figure 6.32** Biasing the BJT amplifier at a point Q located on the active-mode segment of the VTC.

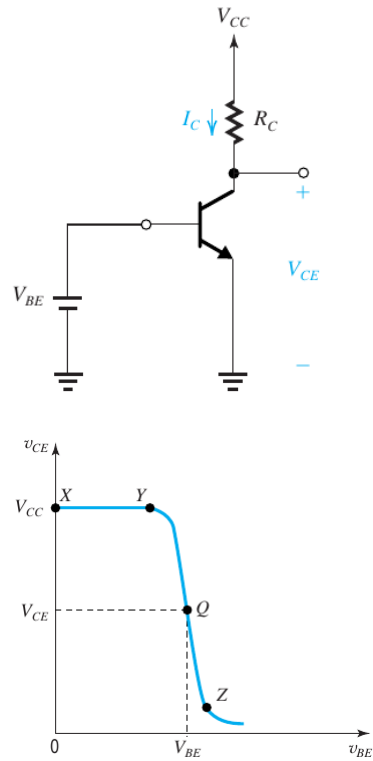- A dc voltage  $V_{BE}$  is selected to obtain operation at a point Q on the segment YZ
- the resulting  $V_{CE}$  can be given as
  - $V_{CE} = V_{CC} - R_C I_S e^{V_{BE}/V_T}$ 
    - Point Q is called the bias point
      - or the dc operating point
      - or the Quiescent point




- Once the Q point is selected, the ac signal to be amplified is superimposed on the bias voltage  $V_{BE}$

◦  $\Rightarrow$  the total instantaneous value of  $v_{BE}$  is

- $v_{BE}(t) = V_{BE} + v_{be}(t)$

- the resulting  $v_{CE}$  is

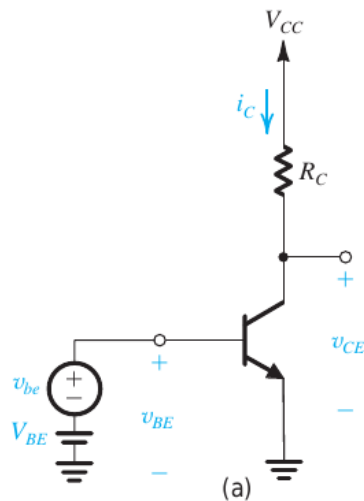
- $v_{CE} = V_{CC} - R_C I_S e^{v_{BE}/V_T}$



- $v_{CE}(t)$  can also be obtained graphically from the VTC

◦ Note that if the amplitude of  $v_{be}$  is small enough to

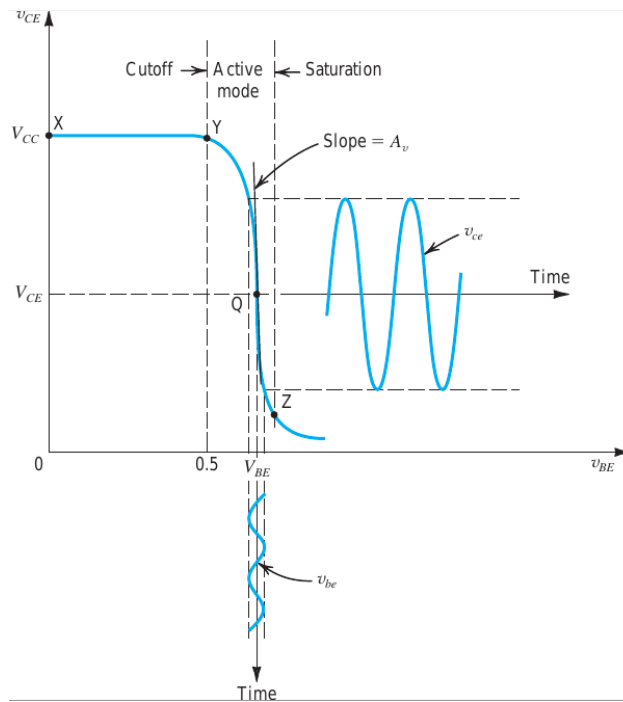
- restrict the signal swing to a short almost-linear segment
  - of the VTC, linear amplification is achieved
- The shorter the segment, the greater the linearity achieved.



### The Small-Signal Voltage Gain

- if the input signal  $v_{be}$  is kept small, the output signal  $v_{ce}$  is nearly proportional to  $v_{be}$ 
  - i.e.  $v_{ce} \propto v_{be}$ 
    - or  $v_{ce} = A_v v_{be}$
    - $A_v$  is the proportionality constant and is the voltage gain of the amplifier
    - $A_v$  is the slope of the almost linear segment of the VTC around Q

$$\blacksquare \text{ i.e. } A_v = \left. \frac{\partial v_{CE}}{\partial v_{BE}} \right|_{v_{BE}=V_{BE}}$$

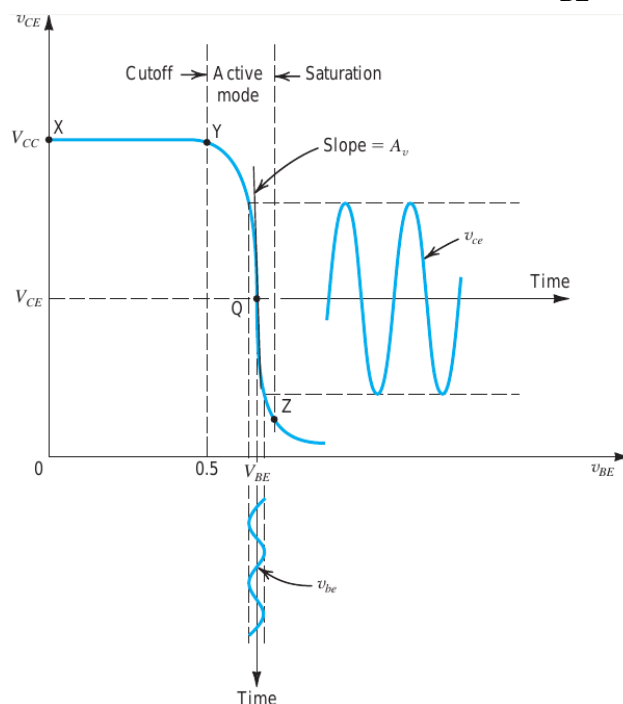

- $A_v = \left. \frac{\partial v_{CE}}{\partial v_{BE}} \right|_{v_{BE}=V_{BE}}$

- using  $v_{CE} = V_{CC} - R_C I_S e^{v_{BE}/V_T}$

- $A_v = \left. \frac{\partial}{\partial v_{BE}} \left[ V_{CC} - R_C I_S e^{v_{BE}/V_T} \right] \right|_{v_{BE}=V_{BE}}$

- $A_v = \left. \left[ 0 - R_C I_S \frac{\partial}{\partial v_{BE}} \left( e^{v_{BE}/V_T} \right) \right] \right|_{v_{BE}=V_{BE}}$

- $A_v = \left. \left[ -R_C I_S e^{v_{BE}/V_T} \frac{\partial}{\partial v_{BE}} \left( v_{BE}/V_T \right) \right] \right|_{v_{BE}=V_{BE}}$

- $A_v = \left. \left[ -\frac{R_C I_S}{V_T} e^{v_{BE}/V_T} \right] \right|_{v_{BE}=V_{BE}}$

- $A_v = -\frac{R_C I_S}{V_T} e^{V_{BE}/V_T} = -\frac{R_C}{V_T} I_S e^{V_{BE}/V_T}$

- $A_v = -\frac{R_C}{V_T} I_C \cdot I_C = I_S e^{V_{BE}/V_T}$

- $\Rightarrow A_v = -\frac{I_C}{V_T} R_C$

- $A_v = -\frac{I_C}{V_T} R_C$

- from this expression, Note that

1. The voltage gain is negative


- $\Rightarrow$  the amplifier is inverting.

- i.e . there is a  $180^\circ$  phase shift between the input and the output

- this inversion is clear from the figure

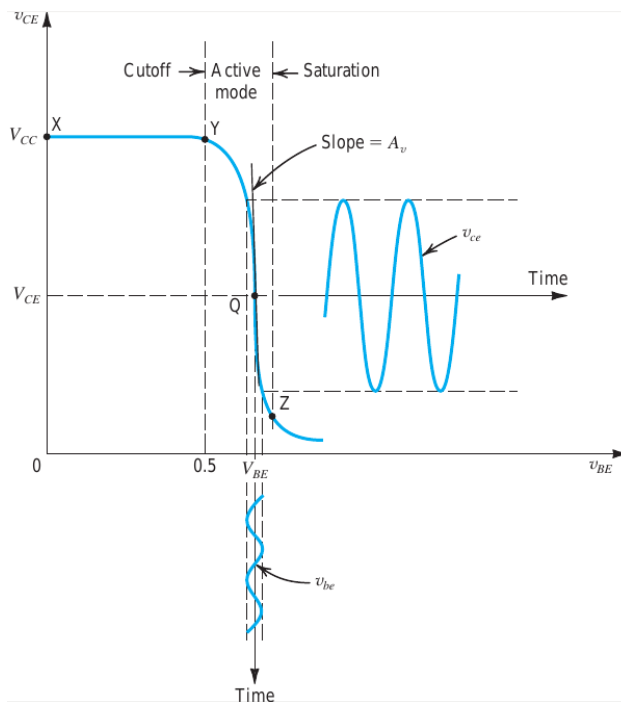2. The gain is proportional to the load resistance  $R_C$ ,

- and to the collector bias current  $I_C$



- $A_v = -\frac{I_C}{V_T} R_C$

- $A_v = -\frac{I_C R_C}{V_T} = -\frac{V_{RC}}{V_T}$ 
  - where  $V_{RC}$  is the dc voltage drop across  $R_C$  i.e.  
 $V_{RC} = V_{CC} - V_{CE}$
- thus the gain is simply the ratio of the dc voltage drop across the load resistor  $R_C$ 
  - to the thermal voltage  $V_T$  ( $\approx 25mV$  at room temperature)
- this relation is useful in determining the absolute upper limit on the magnitude of voltage gain for this amplifier circuit
- Note that
  - the theoretical maximum gain  $A_v$  is obtained by biasing the BJT at the edge of saturation,
    - (which would not leave any room for negative signal swing)
    - The resulting gain can be given as
    - $A_v = -\frac{V_{RC}}{V_T} = -\frac{V_{CC}-V_{CE}}{V_T} = -\frac{V_{CC}-0.3}{V_T} \therefore V_{CE} = 0.3$  at edge of saturation
    - As  $V_{CC} - 0.3 \approx V_{CC}$
  - $A_{vmax} \approx -\frac{V_{CC}}{V_T}$  or  $|A_{vmax}| \approx \frac{V_{CC}}{V_T}$

### Determining the VTC by Graphical Analysis

- Voltage transfer characteristic (VTC) of the amplifier can be determined using graphical method




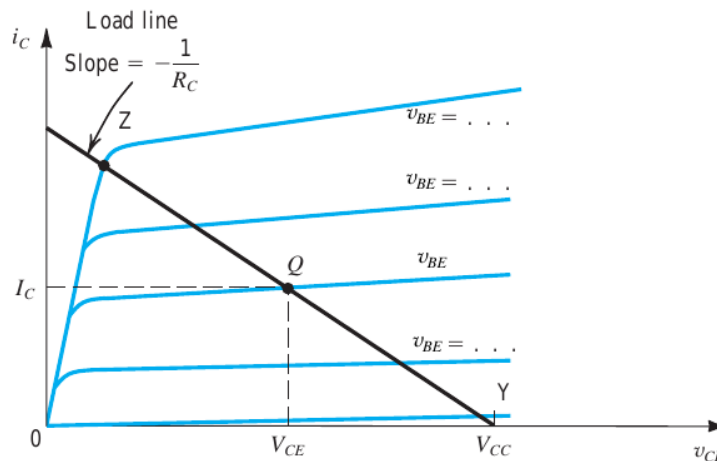


Figure 6.34 Graphical construction for determining the VTC of the amplifier circuit of Fig. 6.33(a).

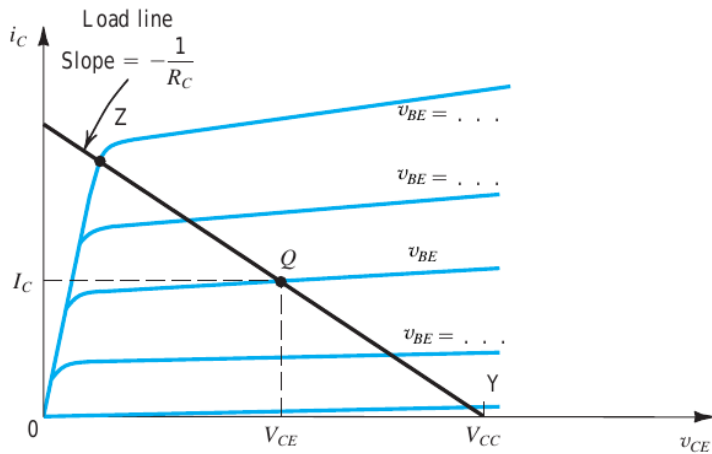

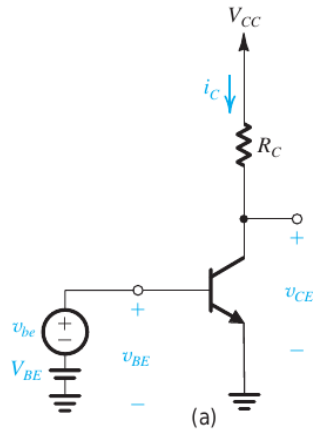

**Figure 6.34** Graphical construction for determining the VTC of the amplifier circuit of Fig. 6.33(a).

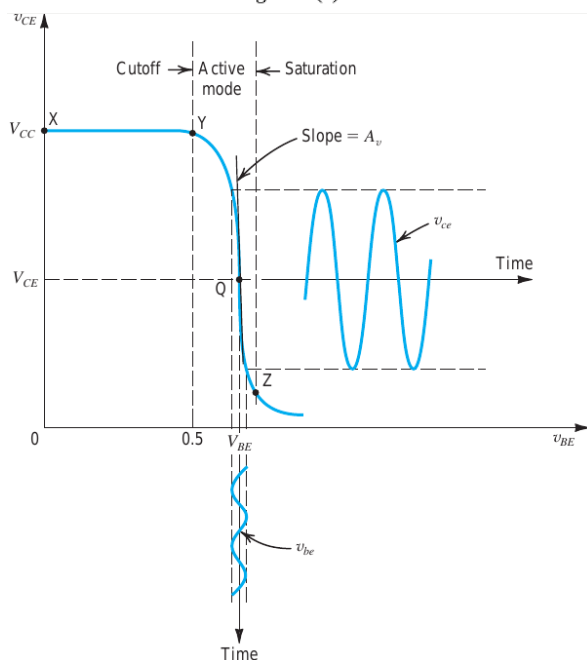

- the graphical analysis is based on the fact
  - for each value of  $v_{BE}$ , the circuit will be operating
    - at the point of intersection of the  $i_C - v_{BE}$  graph
      - corresponding to that particular value of  $v_{BE}$
      - and the straight line representing the KVL eq
      - i.e.  $v_{CE} = V_{CC} - R_C i_C \Rightarrow i_C = \frac{V_{CC}}{R_C} - \frac{v_{CE}}{R_C}$

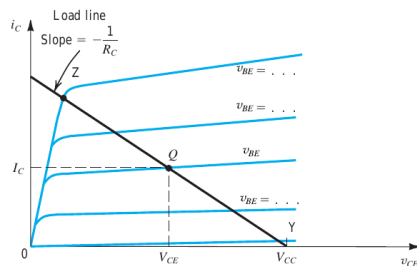


Figure 6.34 Graphical construction for determining the VTC of the amplifier circuit of Fig. 6.33(a).

- The straight line representing this relationship is superimposed on the  $i_C - v_{CE}$  characteristic
- this line intersects the horizontal axis at  $v_{CE} = V_{CC}$  and has a slope of  $-\frac{1}{R_C}$ 
  - this line is called the load line as it represents the load resistance  $R_C$ 
    - the VTC can then be determined point by point
      - here three important points have been labeled
      - At point Y
        - $v_{BE} = 0.5V$  (cutin voltage of EBJ)
      - At point Q
        - BJT can be biased for amplifier application i.e.  $v_{BE} = V_{BE} , v_{CE} = V_{CE}$

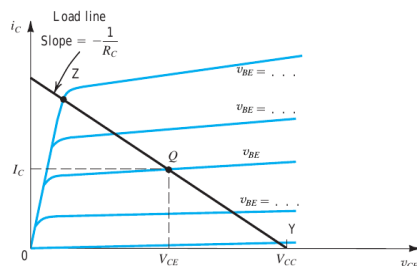


Figure 6.34 Graphical construction for determining the VTC of the amplifier circuit of Fig. 6.33(a).

- At point Z,
  - the BJT leaves the active region and enters the saturation region
    - Note that if the BJT is to be used as a switch, then operating points Y and Z are applicable
      - At Y, the transistor is off (open switch)
      - and at Z the transistor operates as a low valued resistance  $R_{CEsat}$  and has a small voltage drop (closed switch)

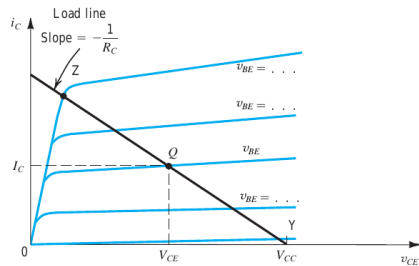


Figure 6.34 Graphical construction for determining the VTC of the amplifier circuit of Fig. 6.33(a).


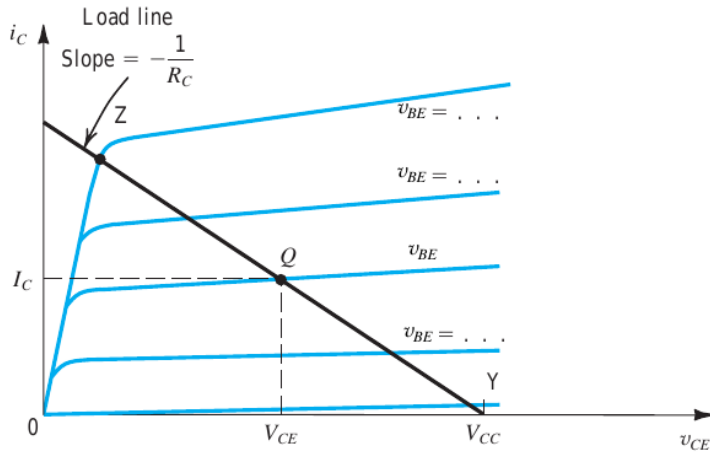


Figure 6.34 Graphical construction for determining the VTC of the amplifier circuit of Fig. 6.33(a).

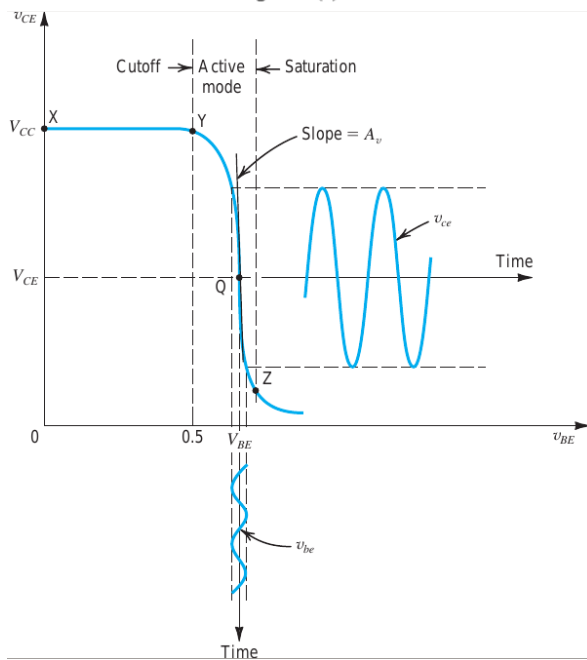

### Locating the Bias Point Q

- The bias point Q is determined by the value of  $v_{BE}$  and that of the load resistance  $R_C$ 
  - Two important considerations in choosing the location of Q are
    - the required gain and
    - the allowable signal swing at the output



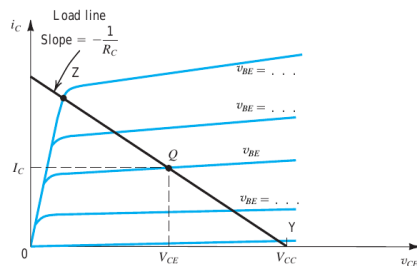


Figure 6.34 Graphical construction for determining the VTC of the amplifier circuit of Fig. 6.33(a).

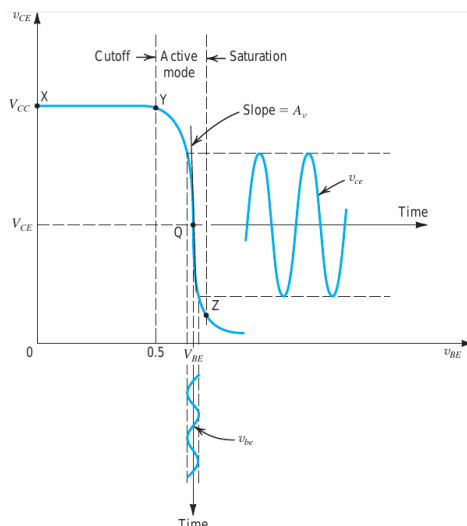- Consider the VTC shown in figure
  - here the value of  $R_C$  is fixed
    - the only remaining variable is the value of  $V_{BE}$
    - Note that the slope increases as we move closer to point Z
      - thus higher gain is achieved by locating Q as close to Z as possible
    - However the closer Q is to the boundary point Z,
      - the smaller the allowable magnitude of negative signal swing



- to decide on the value of  $R_C$ ,  $i_C - v_{CE}$  plane is useful
  - here two load lines are shown which result in two extreme bias points
    - Point  $Q_A$  is too close to  $V_{CC}$ 
      - resulting in a severe constraint on the positive signal swing of  $v_{ce}$
      - Exceeding the allowable +ve maximum will result in positive peaks of the signal being clipped off,
      - since the BJT will turn off for the part of each cycle near the +ve peak
      - we say the circuit does not have sufficient "headroom"

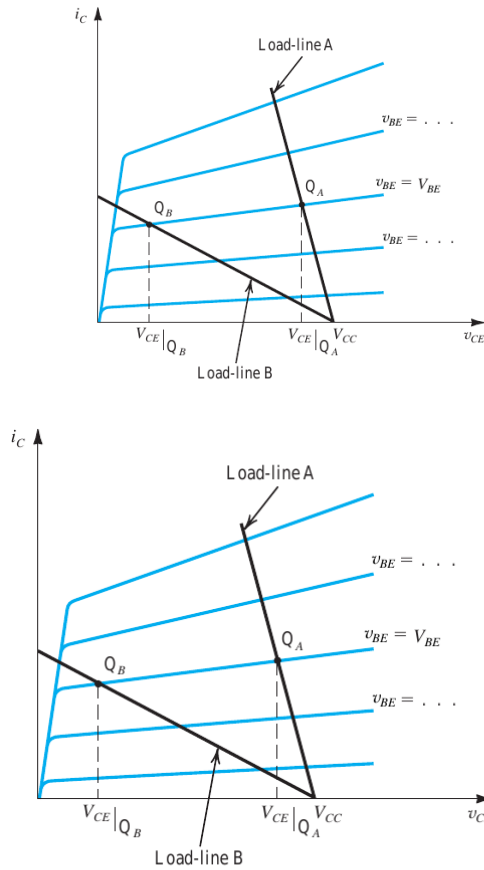

**Figure 6.35** Effect of bias-point location on allowable signal swing: Load line A results in bias point  $Q_A$  with a corresponding  $V_{CE}$  that is too close to  $V_{CC}$  and thus limits the positive swing of  $v_{CE}$ . At the other extreme, load line B results in an operating point,  $Q_B$ , too close to the saturation region, thus limiting the negative swing of  $v_{CE}$ .

- Point  $Q_B$  is very close to the boundary of the saturation region,
  - thus severely limiting the allowable negative signal swing of  $v_{ce}$ 
    - Exceeding this limit results in the transistor entering the saturation region,
      - for part of each cycle near the negative peaks,
      - resulting in a distorted output signal
      - we say the circuit doesnot have sufficient “legroom”

