

Lecture 5b


EE-215 Electronic Devices and Circuits

Asst Prof Muhammad Anis Chaudhary

MOSFET Circuits at DC

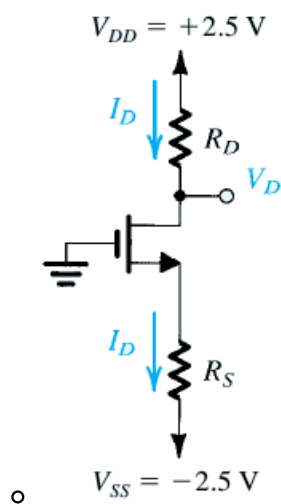
Example 5.3

- Design the circuit of Fig. 5.21, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $L = 1 \mu\text{m}$, and $W = 32 \mu\text{m}$. Neglect the channel-length modulation effect (i.e., assume that $\lambda = 0$).




Solution: Example 5.3

- here
 - $R_D = ?$, $R_S = ?$
 - $I_D = 0.4 \text{ mA}$, $V_D = 0.5 \text{ V}$,
 - $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $L = 1 \mu\text{m}$, $W = 32 \mu\text{m}$, $\lambda = 0$
 - As $V_D = 0.5 \text{ V}$, $I_D = 0.4 \text{ mA}$
 - Ohm's law $\Rightarrow R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.5}{0.4 \text{ mA}} = 5 \text{ k}\Omega$
 - As $I_D \neq 0 \Rightarrow$ the MOSFET is on
 - so the MOSFET can be in triode region or in saturation region

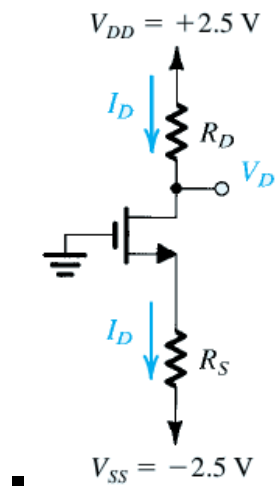


- so the MOSFET can be in triode region or in saturation region
 - As for triode region $v_{DS} < v_{OV} = v_{GS} - V_t$

- and for saturation region $v_{DS} \geq v_{OV} = v_{GS} - V_t$
 - or $v_D \geq (v_G - V_t)$
- here $v_D = 0.5$, $v_G = 0$, $V_t = 0.7 \Rightarrow v_G - V_t = 0 - 0.7$
- $\Rightarrow 0.5 \geq -0.7$ thus the MOSFET is in saturation region
- $i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) v_{OV}^2 = \frac{1}{2} 100 \mu \left(\frac{32}{1} \right) v_{OV}^2$
- $i_D = 0.4m = \frac{1}{2} 100 \mu \left(\frac{32}{1} \right) v_{OV}^2$
- $v_{OV}^2 = \frac{0.4m}{\frac{1}{2} 100 \mu \left(\frac{32}{1} \right)} = 0.25$

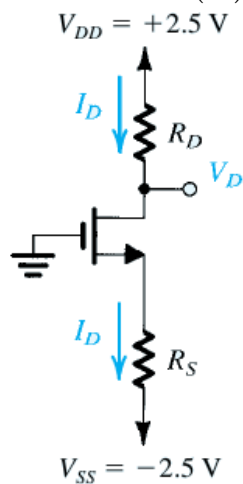


- $v_{OV} = \sqrt{0.25} = 0.5V$
 - $v_{OV} = v_{GS} - V_t = 0.5V \Rightarrow v_{GS} = V_t + 0.5 = 0.7 + 0.5 = 1.2V$
 - $v_G - v_S = 1.2V$
 - $0 - v_S = 1.2V$
 - $v_S = -1.2V$
 - by ohms' law
 - $R_S = \frac{v_S - V_{SS}}{I_D} = \frac{-1.2 - (-2.5)}{0.4m} = \frac{-1.2 + 2.5}{0.4m} = 3.25k\Omega$

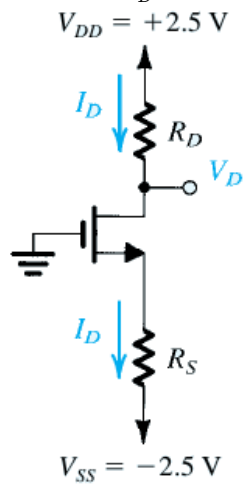

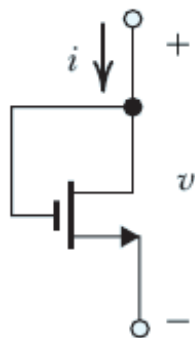Example 5.4


- Figure 5.22 shows an NMOS transistor with its drain and gate terminals connected together. Find the $i - v$ relationship of the resulting two-terminal device in terms of the MOSFET parameters $k_n = k_n' (W / L)$ and V_{tn} . Neglect channel-length modulation (i.e., $\lambda = 0$). Note that this two-terminal device is known as a diode-connected transistor.



o **Figure 5.22**

Solution: Example 5.4


- here $v_G = v_D$
 - o as for saturation region
 - $v_{DS} \geq v_{GS} - V_t$
 - $v_D \geq v_G - V_t$
 - $v_D - v_G \geq -V_t$
 - $0 \geq -V_t$ which is true for an n-channel MOSFET (as V_t is +ve value)
 - \Rightarrow the MOSFET is in saturation
 - i.e. $i_D = \frac{1}{2}k_n' \left(\frac{W}{L}\right) (v_{GS} - V_{tn})^2$
 - from figure for $i = i_D$ and for $v = v_{GS}$
 - $i = \frac{1}{2}k_n' \left(\frac{W}{L}\right) (v - V_{tn})^2 = \frac{1}{2}k_n (v - V_{tn})^2$

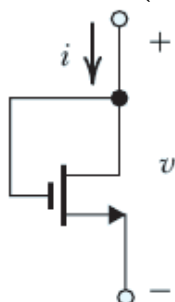

■ **Figure 5.22**

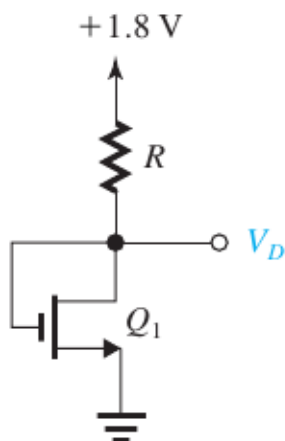Exercise D5.9

- For the circuit in Fig. E5.9, find the value of R that results in $V_D = 0.8V$. The MOSFET has $V_{tn} = 0.5V$ $\mu_n C_{ox} = 0.4mA/V^2$, $\frac{W}{L} = \frac{0.72\mu m}{0.18\mu m}$ and $\lambda = 0$




o **Figure E5.9**

Solution: Exercise D5.9

- here

- $V_D = 0.8V$

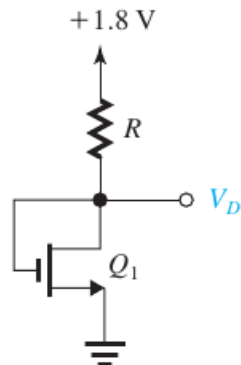- $V_{tn} = 0.5V$, $\mu_n C_{ox} = 0.4mA/V^2$, $\frac{W}{L} = \frac{0.72\mu m}{0.18\mu m}$ and $\lambda = 0$
- from the figure $v_G = v_D$
 - $v_{DS} \geq v_{GS} - V_t$ for saturation region
 - $v_D \geq v_G - V_t$
 - $v_D - v_G \geq -V_t$
 - $v_G - v_D \leq V_t$
 - $0 \leq V_t$ which is true
 - \Rightarrow the MOSFET is in saturation




▪ **Figure E5.9**

- As $v_S = 0$

- $\Rightarrow v_{GS} = v_G - v_S = 0.8 - 0 = 0.8V \therefore v_G = v_D = 0.8V$

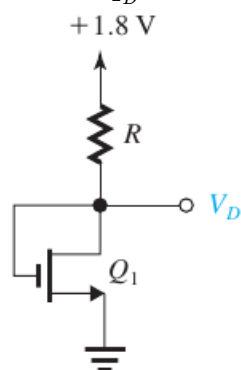
- $i_D = \frac{1}{2}k_n' \left(\frac{W}{L}\right) (v_{GS} - V_{tn})^2$
- $i_D = \frac{1}{2}0.4m \left(\frac{0.72}{0.18}\right) (0.8 - 0.5)^2 = 72\mu A$
- $R = \frac{1.8 - V_D}{I_D} = \frac{1.8 - 0.8}{72\mu} = \frac{1}{72\mu} = 13.889k\Omega$



▪ **Figure E5.9**

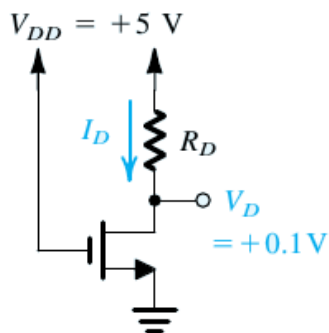Example 5.5


- Design the circuit in Fig. 5.23 to establish a drain voltage of $0.1V$. What is the effective resistance between drain and source at this operating point? Let $V_{tn} = 1V$ and $k_n'(W/L) = 1mA/V^2$.



o **Figure 5.23**

Solution: Example 5.5


- here $v_{GS} = v_G - v_S = V_{DD} - 0 = 5 - 0 = 5V$
 - o $v_{DS} = v_D - v_S = 0.1 - 0 = 0.1V$
 - $\Rightarrow v_{DS} < v_{GS} - V_t$
 - $0.1 < 5 - 1$
 - $0.1 < 4 \Rightarrow$ triode region
 - for triode region
 - $i_D = k_n' \left(\frac{W}{L}\right) \left[(v_{GS} - V_{tn})v_{DS} - \frac{1}{2}v_{DS}^2 \right]$
 - $i_D = 1m \left[(5 - 1)0.1 - \frac{1}{2}(0.1)^2 \right]$
 - $i_D = 1m[0.4 - 0.005] = 0.395mA$
 - $r_{DS} = \frac{v_{DS}}{i_D} = \frac{0.1}{0.395m} = 253.16\Omega$
 - $R_D = \frac{V_{DD} - v_D}{i_D} = \frac{5 - 0.1}{0.395m} = 12.405k\Omega$

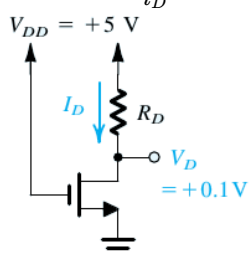

■ **Figure 5.23**

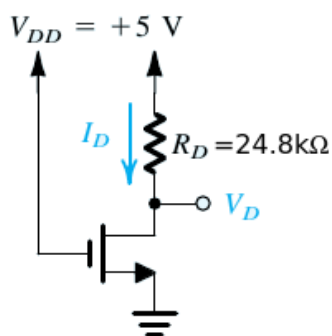Exercise 5.11

- If in the circuit of Example 5.5 the value of R_D is doubled, find approximate values for I_D and V_D .




o **Figure for Exercise 5.11**

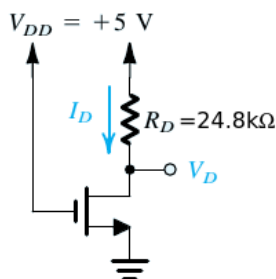Exercise 5.11: (Exact Analysis)

- Now R_D is doubled
 - o $\Rightarrow R_D = 2 \times 12.4k\Omega = 24.8k\Omega$


- As $V_{GS} > V_t$ i.e. $5 > 1 \Rightarrow$ mosfet is not cutoff
- Assume Saturation mode
 - $I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} (1m) (4)^2 = \frac{16m}{2} = 8mA$
 - ohms law $\Rightarrow V_{DD} - V_D = I_D R_D$
 - $5 - V_D = (8m)(24.8k)$
 - $5 - V_D = 198.4$
 - $\Rightarrow 5 - 198.4 = V_D$
 - or $V_D = -193.4V$
 - Now for saturation $V_{DS} \geq V_{GS} - V_t \Rightarrow -193.4 \geq 5 - 1$ which is not true
 - \Rightarrow MOSFET is not in saturation
 - Also note that $V_D = -193.4V$ is not possible in the given circuit as there is no -ve power supply present.
- Assume triode mode
 - $\Rightarrow I_D = k_n' \frac{W}{L} [(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2]$
 - $I_D = 1m [(4) V_{DS} - \frac{1}{2} V_{DS}^2]$
 - by ohm's law $I_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{5 - V_{DS}}{24.8k}$
 - eliminating I_D from the above two equations
 - $\Rightarrow \frac{5 - V_{DS}}{24.8k} = 1m [4V_{DS} - \frac{1}{2} V_{DS}^2]$
 - $5 - V_{DS} = 24.8 [4V_{DS} - \frac{1}{2} V_{DS}^2]$
 - $5 - V_{DS} = 99.2V_{DS} - \frac{24.8}{2} V_{DS}^2$
 - $5 - V_{DS} = 99.2V_{DS} - 12.4V_{DS}^2$
 - $12.4V_{DS}^2 + 5 - V_{DS} - 99.2V_{DS} = 0$
 - $12.4V_{DS}^2 - 100.2V_{DS} + 5 = 0$
 - $V_{DS} = V_D \because V_S = 0$
 - $V_{DS} = V_D = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{100.2 \pm \sqrt{(-100.2)^2 - 4(12.4)(5)}}{2(12.4)}$
 - $\Rightarrow V_D = 4.0403 \pm 3.9901 = 8.0304V, 0.0502V$
 - $V_D = 8.0304V$ not possible $\because V_{DD} = +5V$ i.e. V_D can not exceed 5V
 - $\Rightarrow V_D = 0.0502V$
 - $I_D = \frac{5 - V_{DS}}{24.8k} = \frac{5 - V_D}{24.8k} = \frac{5 - 0.0502}{24.8k} = 0.19959mA$
- now to verify the MOSFET is in triode region
 - $V_{DS} < V_{GS} - V_t$
 - or $0.0502 < 4$ which is TRUE
 - \Rightarrow MOSFET is indeed in triode region.



○ Figure for Exercise 5.11

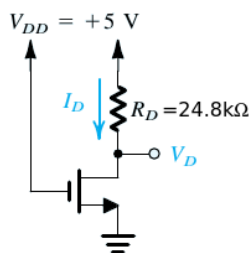Exercise 5.11: (Approximate Analysis)

- Now R_D is doubled
 - $\Rightarrow R_D = 2 \times 12.4k\Omega = 24.8k\Omega$
 - $I_D = \frac{V_{DD}-V_D}{R} = \frac{5-V_D}{24.8k}$ (A)
 - Approximation comes from assuming that r_{DS} stays the same as before
 - i.e. $r_{DS} = \frac{V_{DS}}{I_D} = 253\Omega$
 - $\Rightarrow I_D = \frac{V_{DS}}{r_{DS}} = \frac{V_D-V_S}{253} = \frac{V_D}{253}$ (B)
 - (A) and (B)
 - $\Rightarrow \frac{5-V_D}{24.8k} = \frac{V_D}{253} \Rightarrow \frac{5}{24.8k} - \frac{V_D}{24.8k} = \frac{V_D}{253}$
 - $\frac{5}{24.8k} - \frac{V_D}{24.8k} = \frac{V_D}{253} \Rightarrow \frac{5}{24.8k} = \frac{V_D}{253} + \frac{V_D}{24.8k}$
 - $V_D = \left(\frac{5}{24.8k}\right) / \left(\frac{1}{253} + \frac{1}{24.8k}\right) = 0.0505V$




■ Figure for Exercise 5.11

◦ and from (A), $I_D = \frac{5-V_D}{24.8k} = \frac{5-0.0505}{24.8k} = 0.19958mA$

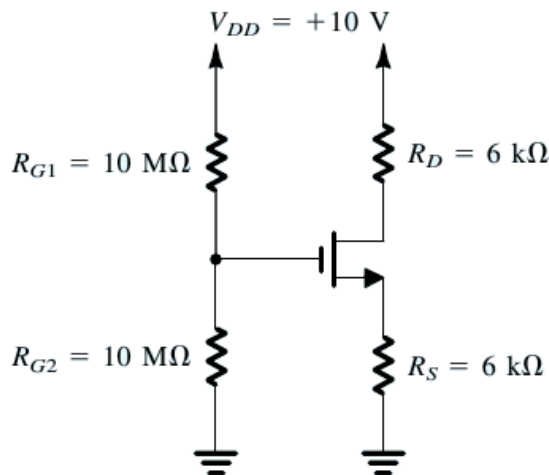Example 5.6

- Analyze the circuit shown in Fig. 5.24(a) to determine the voltages at all nodes and the currents through all branches. Let $V_{tn} = 1V$ and $k_n'(W/L) = 1mA/V^2$. Neglect the channel-length modulation effect (i.e., assume $\lambda = 0$).




◦ (a)

Solution: Example 5.6

- here
 - $V_{tn} = 1V, k_n'(W/L) = 1mA/V^2, \lambda = 0$
 - as no current flows into the gate terminal
 - by voltage divider
 - $v_G = \frac{R_{G2}}{R_{G1}+R_{G2}} V_{DD} = \frac{10M}{20M} (10) = 5V$

$$\blacksquare I_{R_{G1}} = I_{R_{G2}} = \frac{v_G - 0}{R_{G2}} = \frac{5}{10M} = 0.5\mu A$$

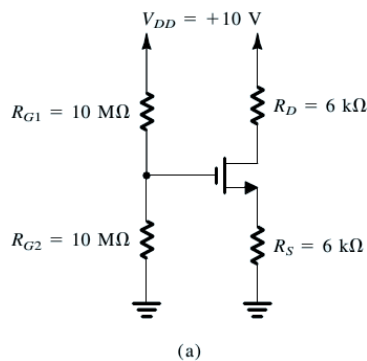- As a +ve gate voltage exists, it is expected
 - \Rightarrow the transistor is ON
- however, we dont know whether it is operating in triode or saturation region



- let's solve by assuming the NMOS transistor is operating in saturation region,
 - and then check the validity of our assumption.
 - if our assumption turns out to be invalid,
 - we will have to solve the problem again for the triode region of operation.


■ thus for saturation region,

$$\blacksquare i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$$

$$\blacksquare I_D = \frac{1}{2} (1m) (V_G - V_S - V_{tn})^2$$

$$\blacksquare I_D = 0.5m(5 - V_S - 1)^2$$

$$\blacksquare I_D = 0.5m(4 - V_S)^2$$

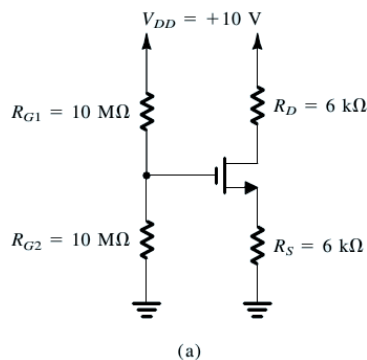

• $I_D = 0.5m(4 - V_S)^2$

◦ also $I_D = \frac{V_S - 0}{6k} = \frac{V_S}{6k} \Rightarrow V_S = (6k)I_D$

■ substitute V_S into above expression for I_D

$$\blacksquare \Rightarrow I_D = 0.5m(4 - V_S)^2 = 0.5m(4 - (6k)I_D)^2$$

$$\blacksquare I_D = 0.5m(16 + (36M)I_D^2 - 2(4)(6k)I_D)$$

$$\blacksquare I_D = 0.5m(16 + (36M)I_D^2 - 2(4)(6k)I_D)$$

$$\blacksquare I_D = 8m + (18k)I_D^2 - 24I_D$$


$$\blacksquare 25I_D = 8m + (18k)I_D^2$$

$$\blacksquare (18k)I_D^2 - 25I_D + 8m = 0$$

■ this quadratic equation has the solution of

$$\blacksquare I_D = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{25 \pm \sqrt{(25)^2 - 4(18k)(8m)}}{2(18k)}$$
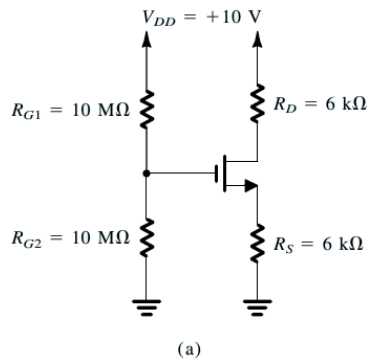
$$\blacksquare I_D = \frac{25 \pm 7}{36k} = 0.89mA, 0.5mA$$



• $I_D = \frac{25 \pm 7}{36k} = 0.89mA, 0.5mA$

◦ As $V_S = (6k)I_D$

■ $\Rightarrow V_S = 5.34V$ for $I_D = 0.89mA$

■ and $V_S = 3V$ for $I_D = 0.5mA$

■ Note that for $V_S = 5.34V$ ($I_D = 0.89mA$)

$\Rightarrow V_{GS} = 5 - 5.34 = -0.34$


■ \Rightarrow the MOSFET is off, so no I_D can't be equal to 0.89mA

■ thus this case is invalid

■ $\Rightarrow V_S = 3V$ and $I_D = 0.5mA$

■ $V_{GS} = 5 - 3 = 2V$

■ $V_{GS} - V_{tn} = 2 - 1 = 1V$

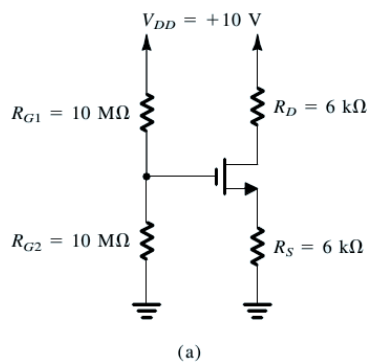

• As $I_D = \frac{V_{DD} - V_D}{R_D} = \frac{10 - V_D}{6k}$

◦ $\Rightarrow I_D = \frac{V_{DD} - V_D}{R_D} = \frac{10 - V_D}{6k}$

■ $0.5m = \frac{10 - V_D}{6k}$

■ $3 = 10 - V_D \Rightarrow V_D = 10 - 3 = 7V$


■ $V_{DS} = V_D - V_S = 7 - 3 = 4V$

■ \Rightarrow here $V_{DS} = 4V, V_{GS} - V_t = 2 - 1 = 1V$

■ $\Rightarrow V_{DS} > V_{GS} - V_t$


■ i.e. $4V > 1V$

■ \Rightarrow the initial assumption was correct, the transistor is in saturation region.

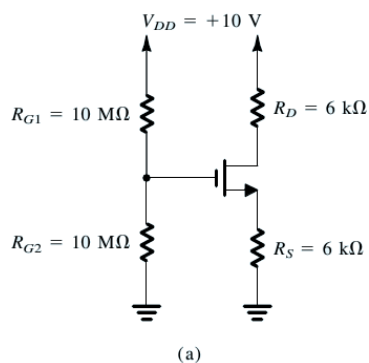

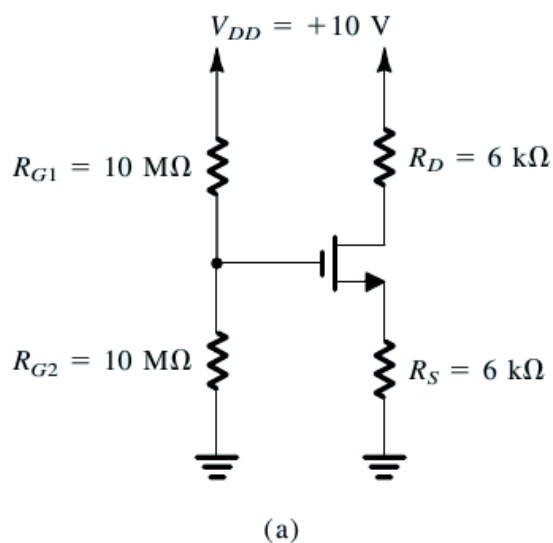
Exercise 5.12

- For the circuit of Fig. 5.24, what is the largest value that R_D can have while the transistor remains in the saturation mode?




Solution: Exercise 5.12

- for Saturation mode
 - $v_{DS} \geq v_{GS} - V_t$
 - or $v_D \geq v_G - V_t$
 - for $\lambda = 0$, I_D remains constant in saturation region w.r.t v_{DS}
 - as $R_D = \frac{V_{DD} - V_D}{I_D}$
 - R_D is largest when V_D is smallest. As V_{DD} and I_D are constants.
 - $\Rightarrow R_D = ?$ when $V_D = V_G - V_t = 5 - 1 = 4V$
 - $R_D = \frac{V_{DD} - V_D}{I_D} = \frac{10 - 4}{I_D} = \frac{6}{I_D}$
 - where $i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$

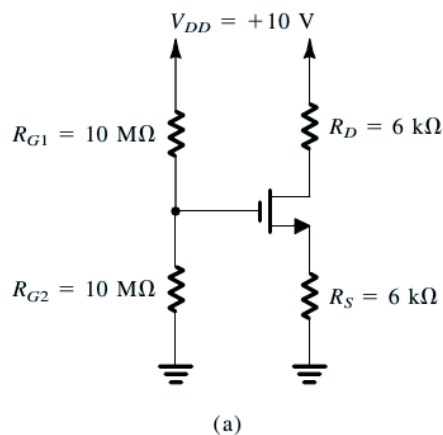


- $i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$
 - As R_S has not changed, $\Rightarrow v_{GS}$ is not changed
 - $I_D = 0.5m(V_G - V_S - 1)^2 = 0.5m(5 - V_S - 1)^2 = 0.5m(4 - V_S)^2$
 - also $I_D = \frac{V_S - 0}{6k} \Rightarrow V_S = I_D 6k$
 - these two equations have already been solved in Example 5.6
 - $\Rightarrow I_D = 0.5mA$
 - $\Rightarrow R_D = \frac{6}{I_D} = \frac{6}{0.5m} = 12k\Omega$

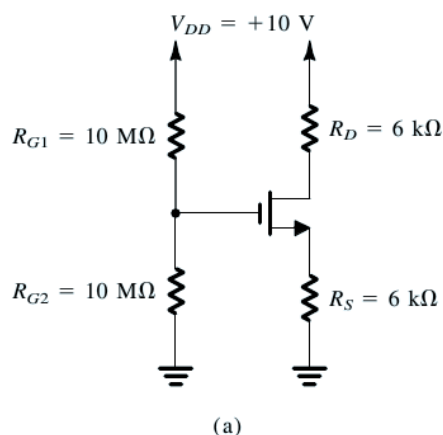

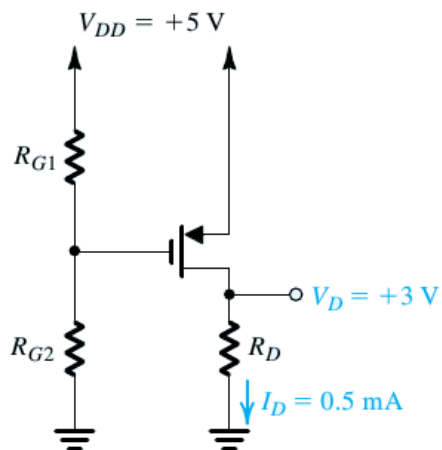Example 5.7

- Design the circuit of Fig. 5.25 so that the transistor operates in saturation with $I_D = 0.5mA$ and $V_D = +3V$. Let the enhancement-type PMOS transistor have $V_{tp} = -1V$ and $kp'(W/L) = 1mA/V^2$. Assume $\lambda = 0$. What is the largest value that R_D can have while maintaining saturation-region operation?



o **Figure 5.25** Circuit for Example 5.7.

Solution: Example 5.7

- here
 - o saturation region and $I_D = 0.5mA$
 - $V_{tp} = -1V, k_p' \left(\frac{W}{L}\right) = 1m\frac{A}{V^2}, \lambda = 0$
 - in saturation region
 - $i_D = \frac{1}{2}k_p' \left(\frac{W}{L}\right) (v_{SG} - |V_{tp}|)^2$
 - $0.5m = \frac{1}{2}(1m)(v_{SG} - 1)^2$
 - $0.5m = (0.5m)(v_{SG} - 1)^2$
 - $(v_{SG} - 1)^2 = 1 \Rightarrow v_{SG} - 1 = \pm 1$
 - or $v_{SG} = 1 \pm 1 = 2, 0$
 - $v_{SG} = 0$ doesnot make any sense as it means the device is cutoff but the given $I_D = 0.5mA$, so the device cannot be cutoff

▪ $\Rightarrow V_{SG} = 2V$

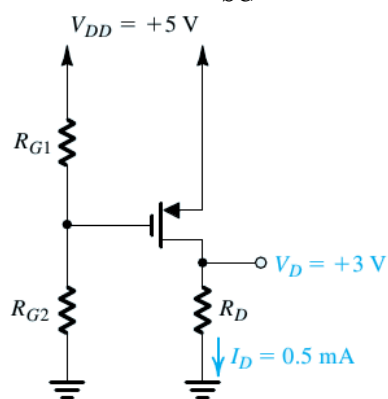


Figure 5.25 Circuit for Example 5.7.

- $V_{SG} = 2V$
 - o $V_S - V_G = 2V$
 - or $5 - V_G = 2V$
 - $V_G = 5 - 2 = 3V$
 - from the figure
 - $V_G = \frac{R_{G2}}{R_{G1} + R_{G2}} V_{DD}$ and $\frac{5}{I_{R_{G1}}} = R_{G1} + R_{G2}$

- for $I_{R_{G1}} = 1\mu A \Rightarrow R_{G1} + R_{G2} = \frac{5}{1\mu} = 5M\Omega$
- $V_G = \frac{R_{G2}}{R_{G1}+R_{G2}} V_{DD} \Rightarrow \frac{3}{5} = \frac{R_{G2}}{R_{G1}+R_{G2}} = \frac{R_{G2}}{5M} \Rightarrow$
 $R_{G2} = \frac{3}{5} \times 5M = 3M\Omega$
- $R_{G1} = 5M - R_{G2} = 2M\Omega$

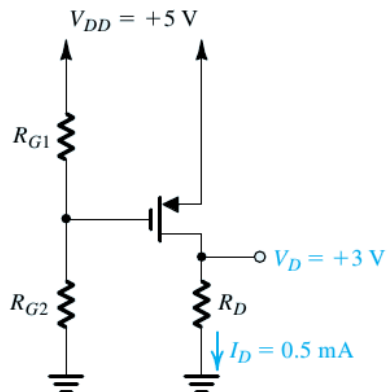


Figure 5.25 Circuit for Example 5.7.

- for saturation

- $v_{SD} \geq v_{SG} - |V_{tp}|$

- $v_S - v_D \geq v_S - v_G - |V_{tp}|$

- $-v_D \geq -v_G - |V_{tp}|$

- $-v_D \geq -v_G - 1$

- $v_D \leq v_G + 1$

- at the edge (i.e. at the start of saturation region)

- $v_D = v_G + 1 = 3 + 1 = 4V$

- $\Rightarrow R_D = \frac{V_D - 0}{I_D} = \frac{4 - 0}{0.5m} = 8k\Omega$

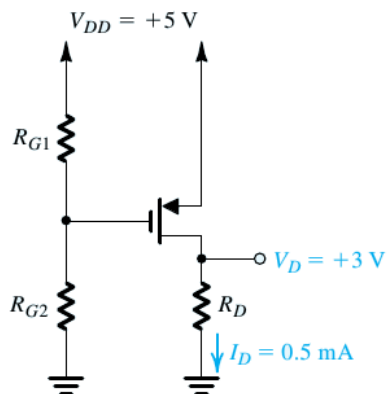


Figure 5.25 Circuit for Example 5.7.