


Lecture 7a

EE-215 Electronic Devices and Circuits


Asst Prof Muhammad Anis Chaudhary

Small-Signal Equivalent Circuit Models

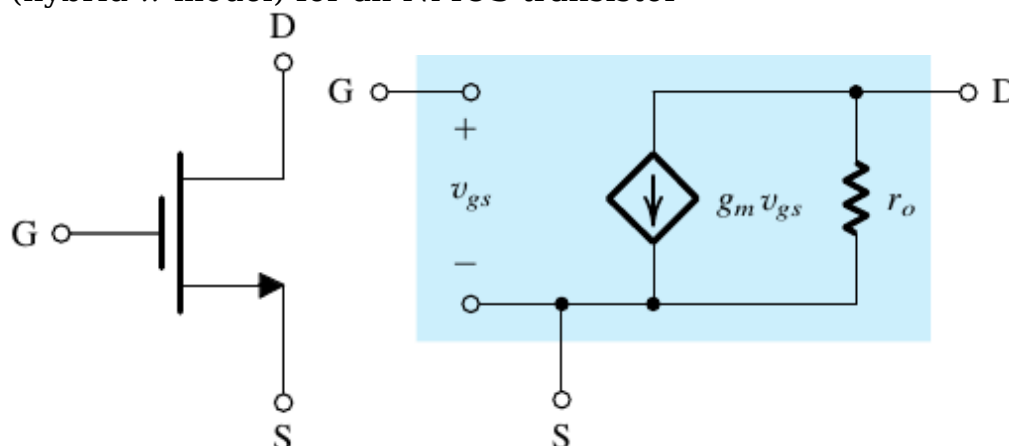
- we had already seen the small-signal equivalent circuit model (hybrid- π model) for an NMOS transistor



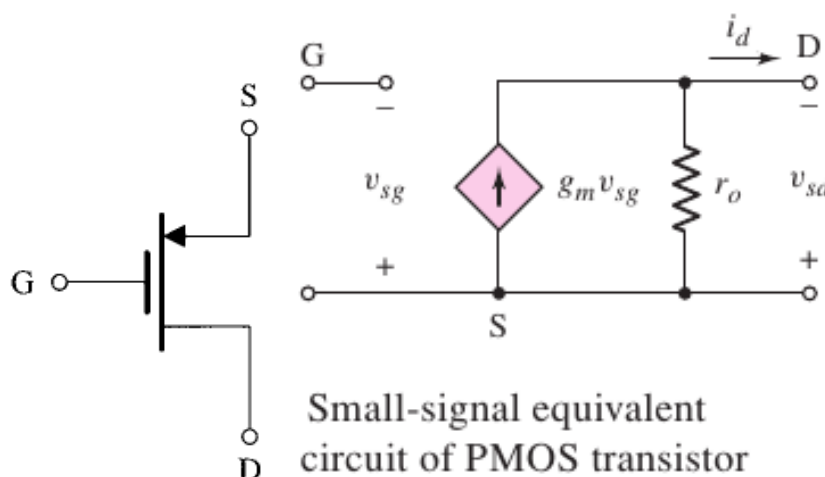- also for PMOS transistor, the MOSFET acts as a voltage controlled current source.
 - thus the small-signal model for the p-channel MOSFET can be given as



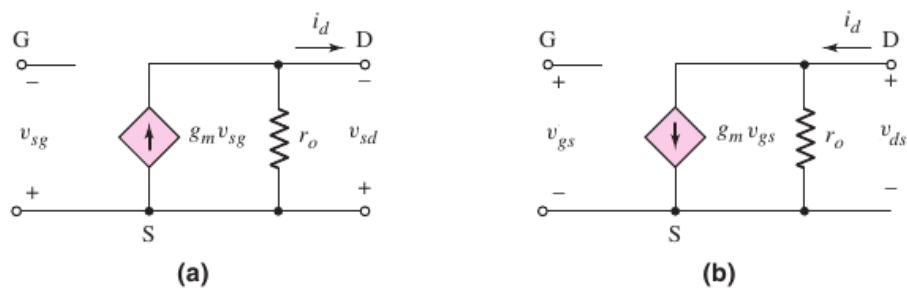- In the small-signal model of PMOS transistor,
 - if we substitute, $v_{sg} = -v_{gs}$
 - $\Rightarrow g_m v_{sg} = -g_m v_{gs}$
 - i.e. if the control voltage polarity is reversed, then the dependent current direction is also reversed.
 - also $v_{sd} = -v_{ds}$




Small signal equivalent circuit of a p-channel MOSFET showing (a) the conventional voltage polarities and current directions and (b) the case when the voltage polarities and current directions are reversed.


- thus the resultant equivalent circuit (fig b) for the PMOS transistor is exactly the same as that of the NMOS transistor
 - we conclude that the small-signal equivalent circuit model (hybrid- π model) is
 - exactly the same for both the NMOS and the PMOS transistors

The T Equivalent-Circuit Model

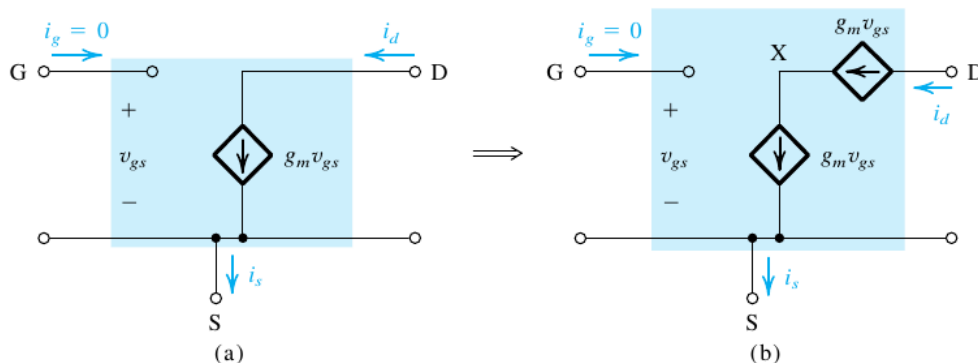
- A simple circuit transformation can lead to an alternative
 - equivalent circuit model for a MOSFET
 - we start with the hybrid- π model




- here we have placed a 2nd $g_m v_{gs}$ current source in series with the original controlled source.
 - Note that, this new current source doesnot change the terminal currents and is thus allowed
- the new node X, can be connected to the gate.
 - As because of KCL, still the gate current $i_g = 0$.
 - so the gate current is still zero (i.e. this connection doesnot change the terminal characteristics)

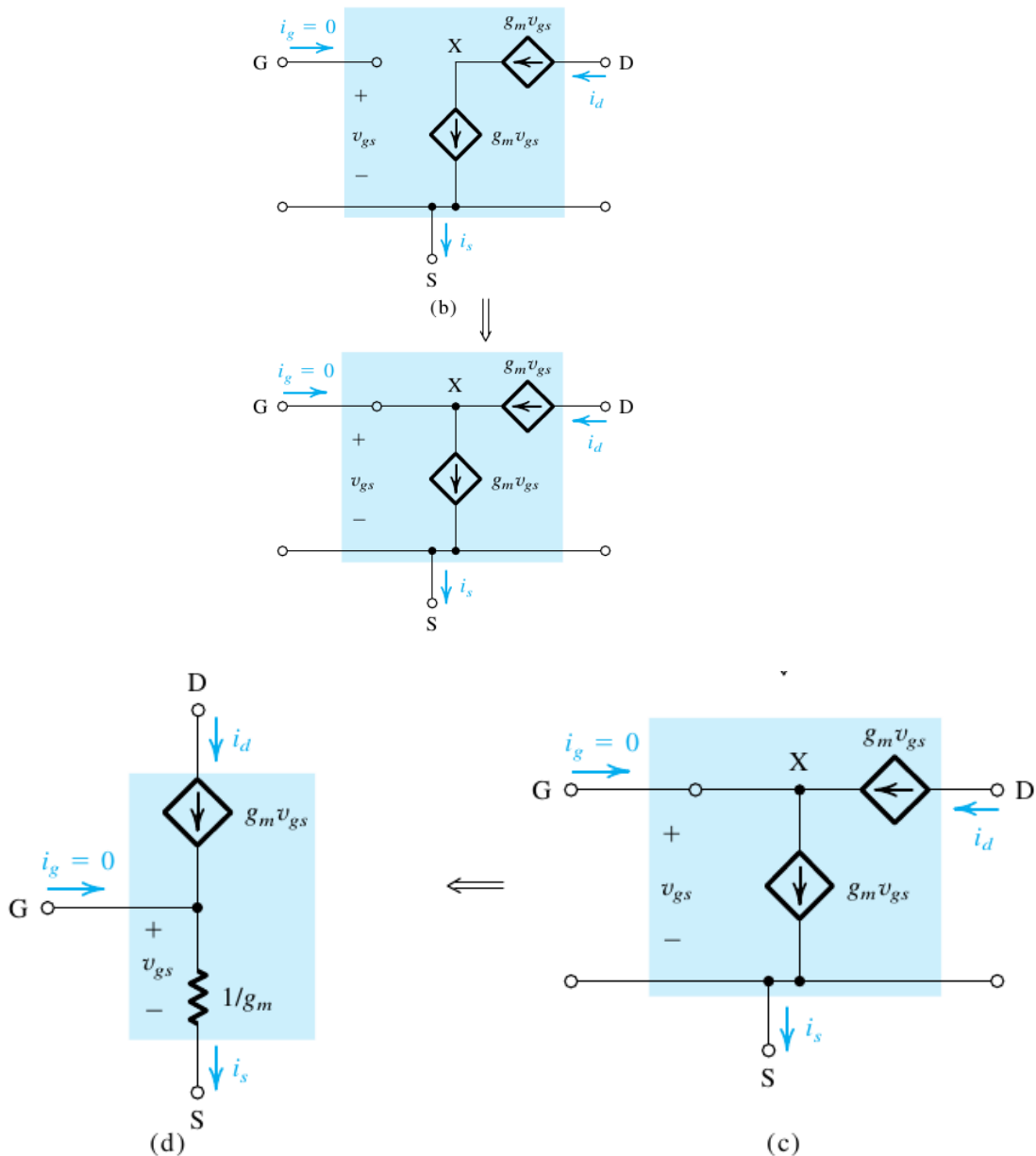

- Note that, here we have a controlled current source $g_m v_{gs}$
 - whose current is controlled by the control voltage v_{gs}
 - where v_{gs} is across itself
 - \Rightarrow this current source can be replaced by a resistor of value $\frac{v_{gs}}{g_m v_{gs}} = \frac{1}{g_m}$
- Note that the resistance between the gate and the source,
 - looking in to the source terminal is $1/g_m$
 - and looking in to the gate terminal is infinite

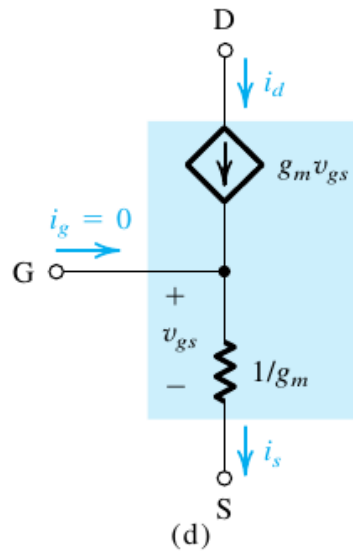

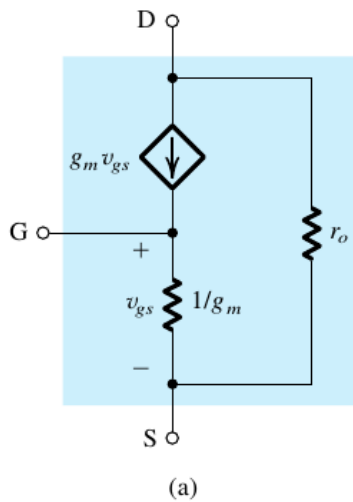- if the channel-length modulation effect cannot be ignored,
 - we can include r_o in the T-model between the drain and the source terminal



- Also we can have an alternative representation of the T model,
 - where we can replace the voltage-controlled current source by
 - a current controlled current source

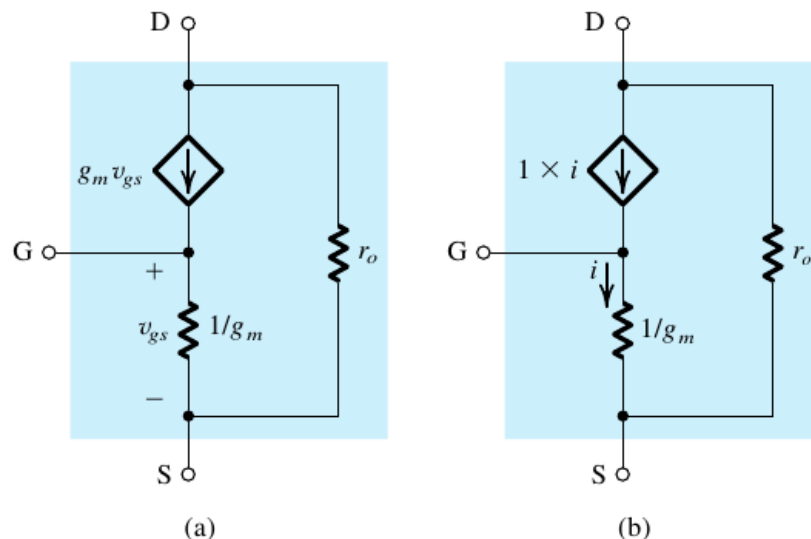


Figure 5.41 (a) The T model of the MOSFET augmented with the drain-to-source resistance r_o . (b) An alternative representation of the T model.


Small-Signal Operation and Models

Table 5.3 Small-Signal Equivalent-Circuit Models for the MOSFET	
Small-Signal Parameters	
NMOS transistors	
■ Transconductance:	$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$
■ Output resistance:	$r_o = V_A / I_D = 1 / \lambda I_D$
PMOS transistors	
Same formulas as for NMOS except using $ V_{OV} $, $ V_A $, and replacing μ_n with μ_p .	
Small-Signal Equivalent Circuit Models	
<p>The diagram shows three models for a MOSFET with terminals G, D, and S. The Hybrid-π model shows a dependent current source $g_m v_{gs}$ between D and S, and a resistor $1/g_m$ between G and S. The T models (left) show a dependent current source $g_m v_{gs}$ between D and S, a resistor $1/g_m$ between G and S, and a resistor r_o between D and S. The T models (right) show a current source i between D and S, a resistor $1/g_m$ between G and S, and a resistor r_o between D and S.</p>	

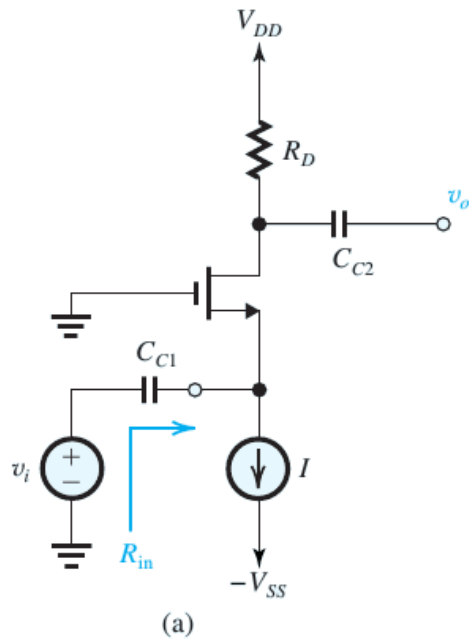Example 5.11


- Figure 5.42(a) shows a MOSFET amplifier biased by a constant-current source I . Assume that the values of I and R_D are such that the MOSFET operates in the saturation region. The input signal v_i is coupled to the source terminal by utilizing a large capacitor C_{C1} .

Similarly, the output signal at the drain is taken through a large coupling capacitor C_{C2} . Find the input resistance R_{in} and the voltage gain v_o / v_i . Neglect channel-length modulation.



Solution:

- here $\lambda = 0$, $R_{in} = ?$, $A_v = \frac{v_o}{v_i} = ?$
 - as an ac source is connected at the source terminal of the MOSFET, it is more convenient to use T-model.
 - thus for ac analysis,
 - suppress dc sources i.e. V_{DD} is replaced by short circuit
 - and I is replaced by an open circuit
 - C_{C1} , C_{C2} are replaced by short circuits
 - MOSFET is replaced by its T-model

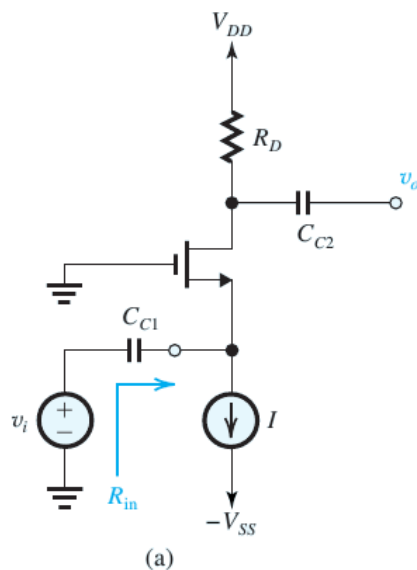


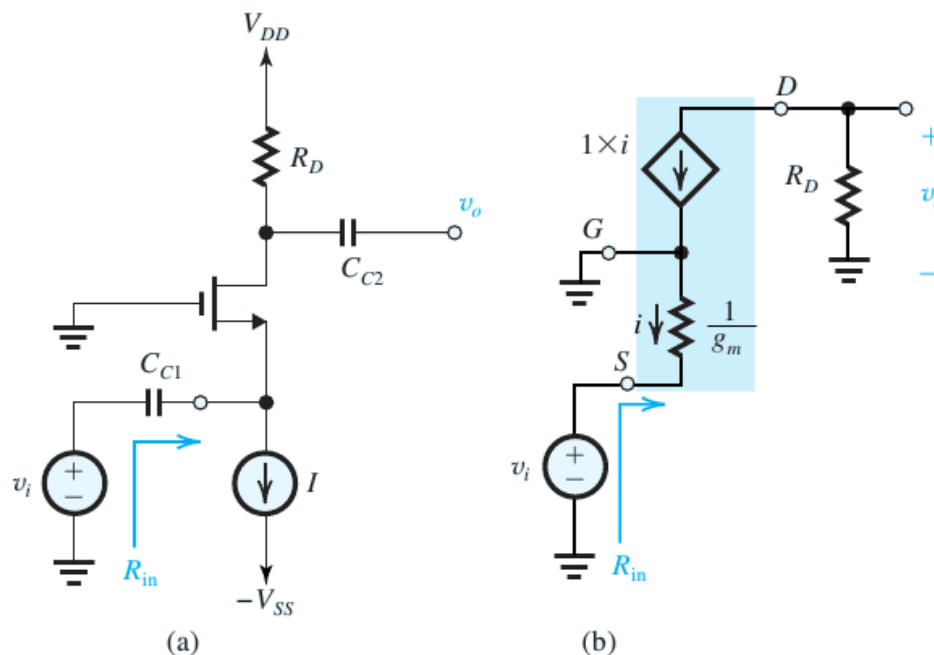


Figure 5.42 (a) Amplifier circuit for Example 5.11; (b) Small-signal equivalent circuit of the amplifier in (a).

- as $\frac{v_{gs}}{i} = \frac{1}{g_m}$ and $v_{gs} = -v_i$
 - $\Rightarrow \frac{-v_i}{i} = \frac{1}{g_m}$
 - and $R_{in} = \frac{v_i}{i_i} = \frac{v_i}{-i} = \frac{-v_i}{i} = \frac{1}{g_m}$
 - by ohm's law at R_D
 - $v_o = (-i)R_D$
 - As $i = \frac{v_{gs}}{1/g_m} = g_m v_{gs}$
 - $\Rightarrow v_o = -g_m v_{gs} R_D$
 - or $v_o = -g_m (-v_i) R_D \because v_{gs} = -v_i$
 - $v_o = g_m v_i R_D \Rightarrow A_v = \frac{v_o}{v_i} = g_m R_D$

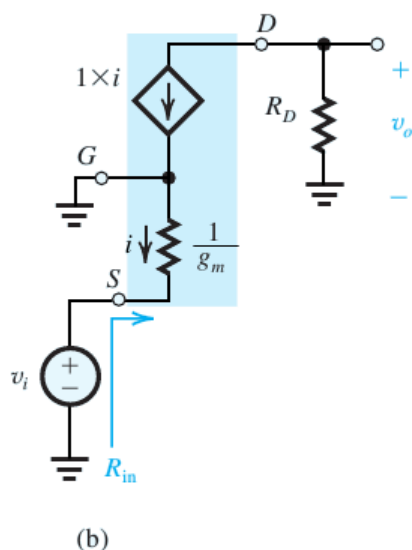

Basic MOSFET Amplifier Configurations

Basic MOSFET Amplifier Configurations

- we have already determined that
 - almost-linear amplification can be obtained by
 - biasing the MOSFET at a suitable point Q in
 - its saturation region of operation
 - and by keeping the signal v_{gs} small

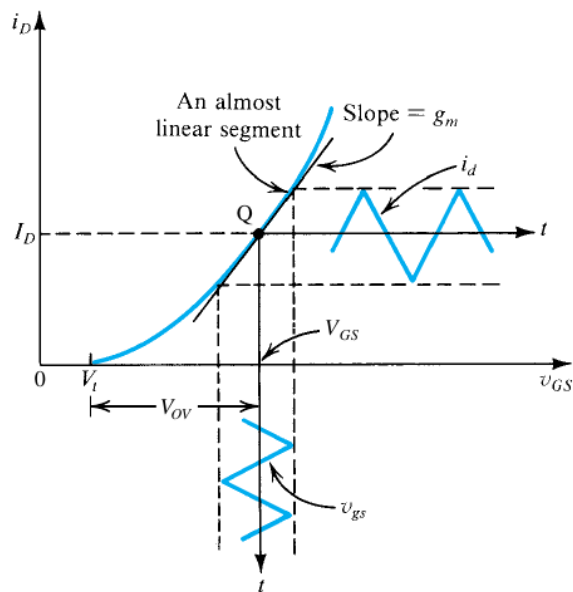
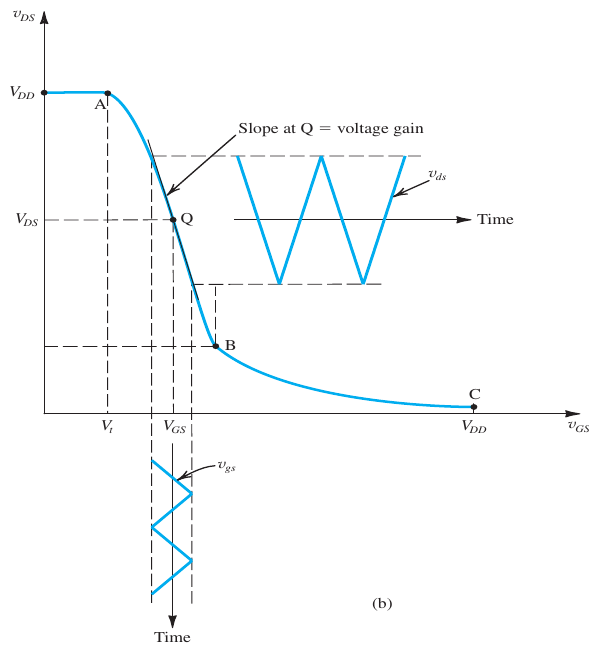


Figure 5.35 Small-signal operation of the MOSFET amplifier.

Basic MOSFET Amplifier Configurations

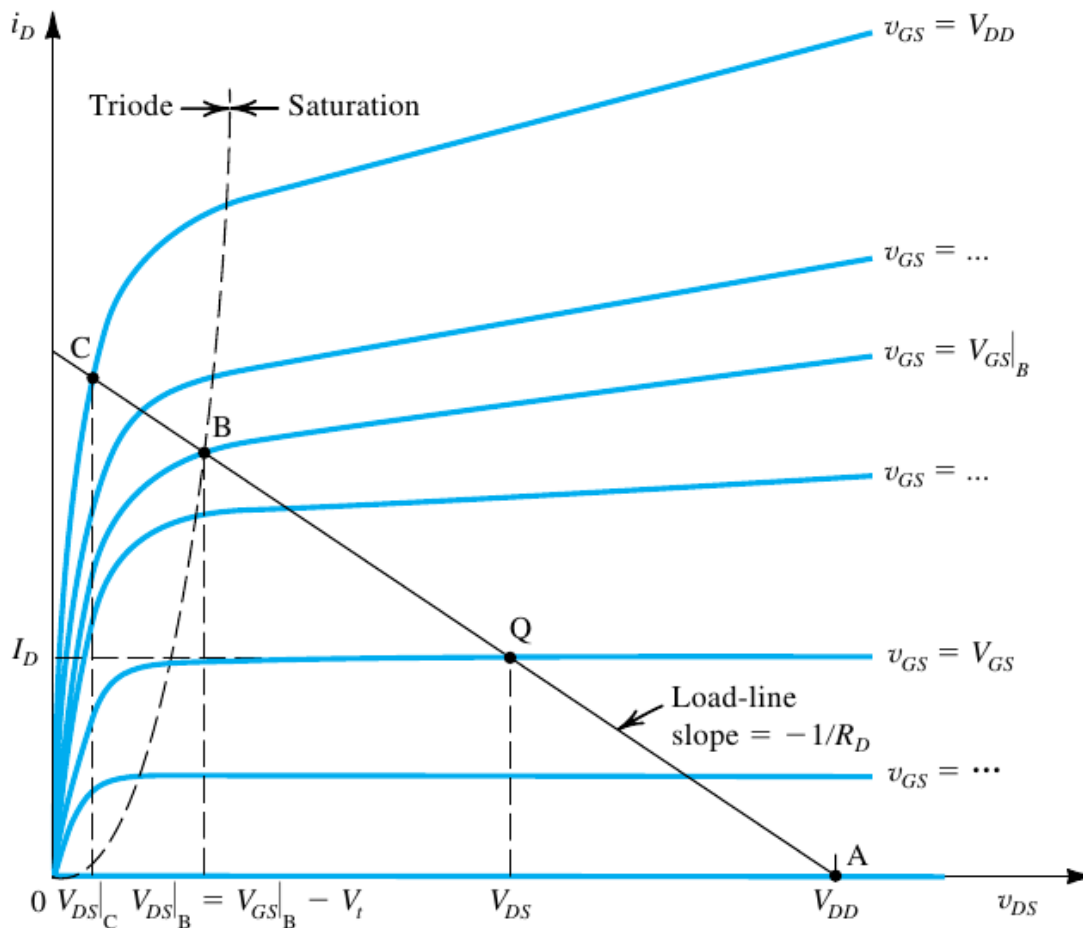


Figure 5.31 Graphical construction to determine the voltage transfer characteristic of the amplifier in Fig. 5.29(a).

- Also when v_{gs} is small, the MOSFET can be replaced by its small-signal circuit model (either hybrid- π model or the T-model)
 - the resultant ac circuit can be used to determine the amplifier parameters like
 - the voltage gain,
 - the input resistance
 - and the output resistance

Table 5.3 Small-Signal Equivalent-Circuit Models for the MOSFET	
Small-Signal Parameters	
NMOS transistors	
■ Transconductance:	$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$
■ Output resistance:	$r_o = V_A / I_D = 1 / \lambda I_D$
PMOS transistors	
Same formulas as for NMOS <i>except</i> using $ V_{OV} $, $ V_A $, and replacing μ_n with μ_p .	
Small-Signal Equivalent Circuit Models	
<p>The figure shows three equivalent circuit models for a MOSFET. The first is the Hybrid-π model, where the gate is connected to ground (G), the source is connected to ground (S), and the drain is the output (D). It features a dependent current source $g_m v_{gs}$ in parallel with the output resistance r_o. The gate-source voltage v_{gs} is applied across the gate and source terminals. The second model is a T model where the gate is connected to ground (G), the source is connected to ground (S), and the drain is the output (D). It features a dependent current source $g_m v_{gs}$ in parallel with r_o, and a resistor $1/g_m$ in series with the gate terminal. The gate-source voltage v_{gs} is applied across the gate and source terminals. The third model is another T model where the gate is connected to ground (G), the source is connected to ground (S), and the drain is the output (D). It features a dependent current source i in parallel with r_o, and a resistor $1/g_m$ in series with the gate terminal. The current i is defined as the current entering the gate terminal.</p>	
	Hybrid- π model
	T models

The Three Basic Configurations

- There are three basic configurations for connecting the MOSFET as an amplifier, namely
 - the Common Source (CS) Amplifier
 - the Common Gate (CG) Amplifier
 - The Common Drain (CD) Amplifier (also called Source Follower)
 - Each of these configurations is obtained by
 - connecting one of the three MOSFET terminals to ground
 - thus creating a two-port network with the grounded terminal
 - being common to the input and output ports
 - The resulting three configurations with biasing arrangement omitted are shown in fig


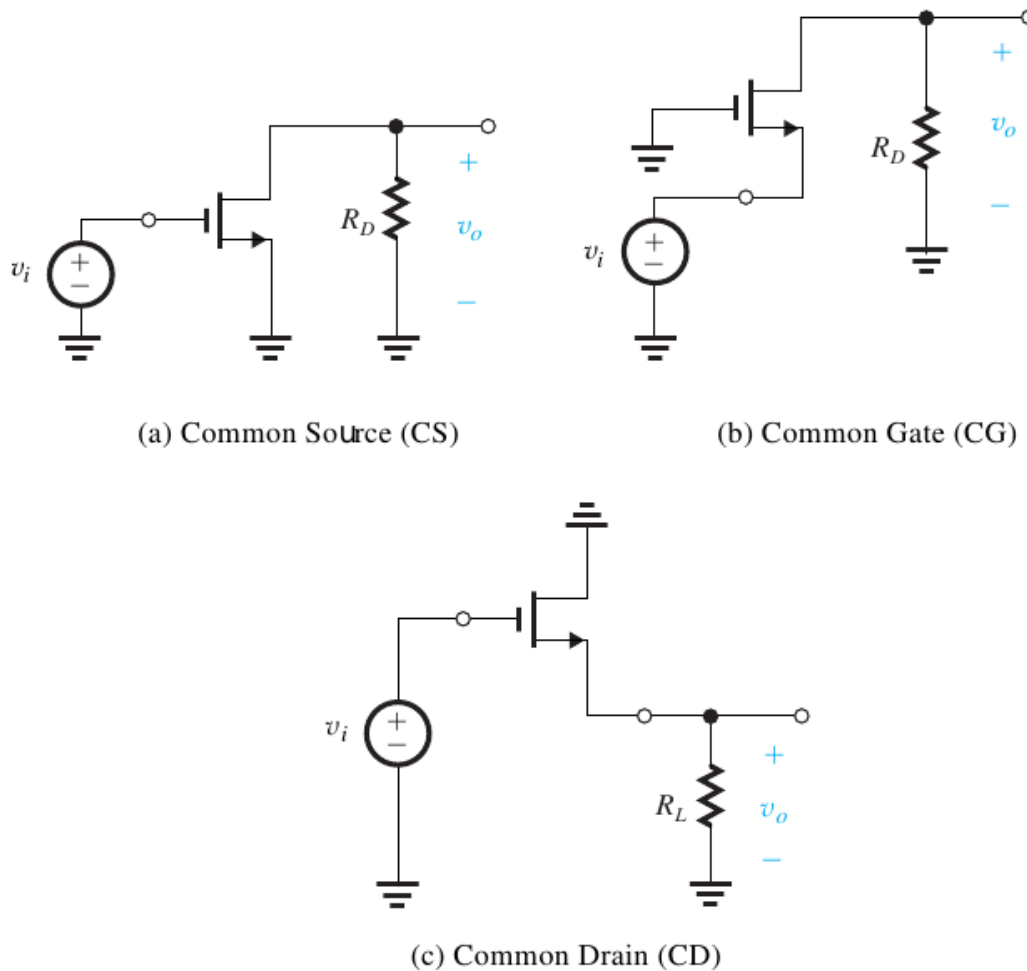


Figure 5.43 The three basic MOSFET amplifier configurations.

Common Source Amplifier

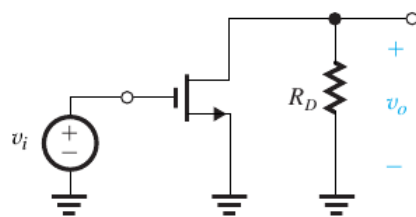- here the source terminal is connected to ground,
 - the input voltage is applied at the gate (w.r.t ground),
 - the output voltage is taken at the drain (w.r.t ground)




(a) Common Source (CS)

- this configuration is called the grounded source or the common source (CS) amplifier
- Note that dc biasing circuit is not shown in figure

Common Gate Amplifier

- The common gate (CG) or grounded gate amplifier is obtained
 - by connecting the gate to ground,
 - applying the input between the source and ground

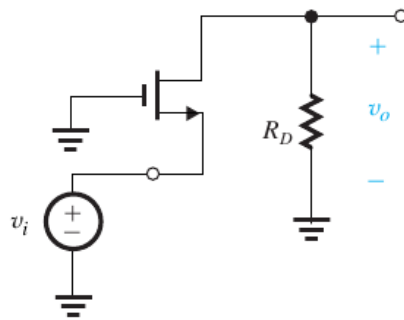- taking the output v_o between the drain and ground




(b) Common Gate (CG)

- Note that dc biasing circuit is not shown in figure

Common Drain Amplifier

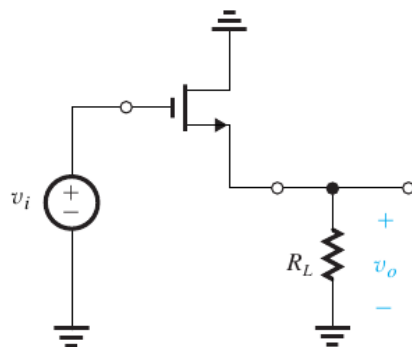- The common drain (CD) or grounded drain amplifier is obtained
 - by connecting the drain terminal to ground,
 - applying the input between the gate and ground
 - taking the output v_o between the source and ground




(c) Common Drain (CD)

- Note that dc biasing circuit is not shown in figure
- the Common Drain amplifier is also called Source Follower

Characterizing Amplifiers

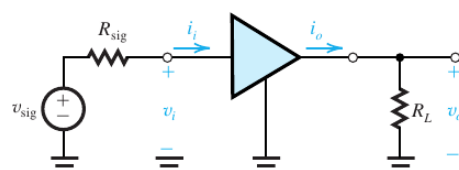
- lets take a look at how to characterize the performance of an amplifier as a circuit building block
 - here an amplifier is fed with a signal source
 - having an open-circuit voltage v_{sig} and an internal resistance R_{sig}



- this voltage source (v_{sig}, R_{sig}) can be an actual signal source
 - or in a cascade amplifier, it can be the Thevenin equivalent of the output circuit of the preceding amplifier.

- the load resistor R_L is connected at the output terminal of the amplifier
 - this R_L can be an actual load resistor
 - or the input resistance of a succeeding amplifier stage in a cascade amplifier

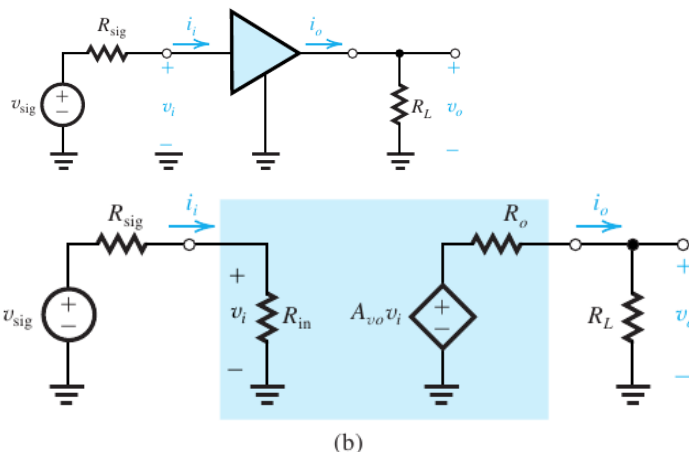- The amplifier block can be replaced by its equivalent circuit model




- the input resistance R_{in}

- indicate the loading effect of the amplifier input on the signal source
- and is given as $R_{in} = \frac{v_i}{i_i}$

- by voltage divider rule

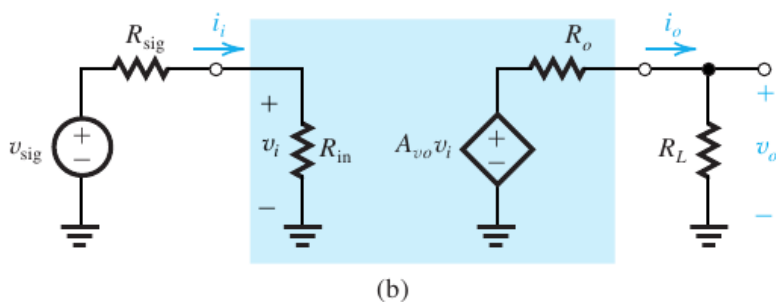
- $v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$




- $v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$

- A_{vo} is the open-circuit voltage gain and is defined as

- $A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L = \infty}$

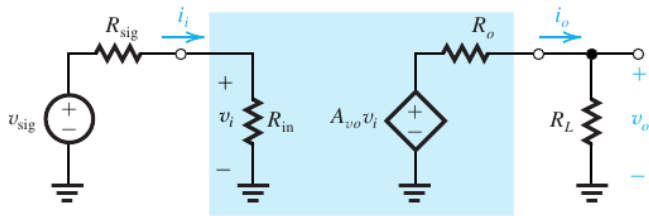


(b)

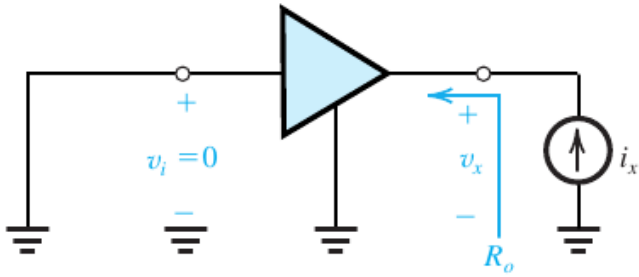

(c)

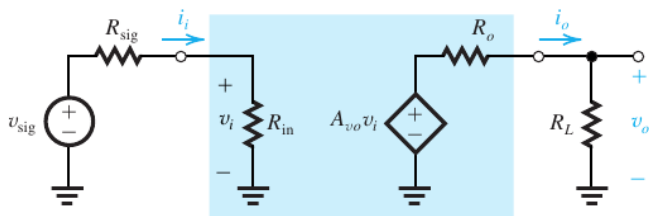- the 3rd parameter that is essential to characterize an amplifier is the output resistance R_o
 - R_o is the resistance seen looking back into the amplifier output terminal with v_i set to zero
 - $\Rightarrow R_o = \frac{v_x}{i_x}$
 - Note that the controlled source $A_{vo}v_i$ and the output resistance R_o
 - represent the Thevenin equivalent of the amplifier output circuit.



(b)

- by voltage divider
 - the output voltage v_o can be given as
 - $v_o = \frac{R_L}{R_L + R_o} (A_{vo}v_i) \Rightarrow \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_o}$
 - thus the voltage gain of the amplifier is
 - $A_v = \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_o}$
 - the overall voltage gain is
 - $G_v = \frac{v_o}{v_{sig}} = A_{vo} \frac{R_L}{R_L + R_o} \frac{v_i}{v_{sig}}$
 - $G_v = A_{vo} \frac{R_L}{R_L + R_o} \frac{R_{in}}{R_{in} + R_{sig}} \because v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$