

## Lecture 8b


### EE-215 Electronic Devices and Circuits

Asst Prof Muhammad Anis Chaudhary

---

## Discrete-Circuit MOS Amplifiers

- Thus any of the above biasing methods can be utilized to implement a MOSFET amplifier
  - A MOSFET amplifier can be a
    - Common Source Amplifier
      - Common Gate Amplifier
      - or a Source Follower
    - here we will utilize the constant-current biasing scheme,
      - to implement the three basic configurations of MOS amplifiers

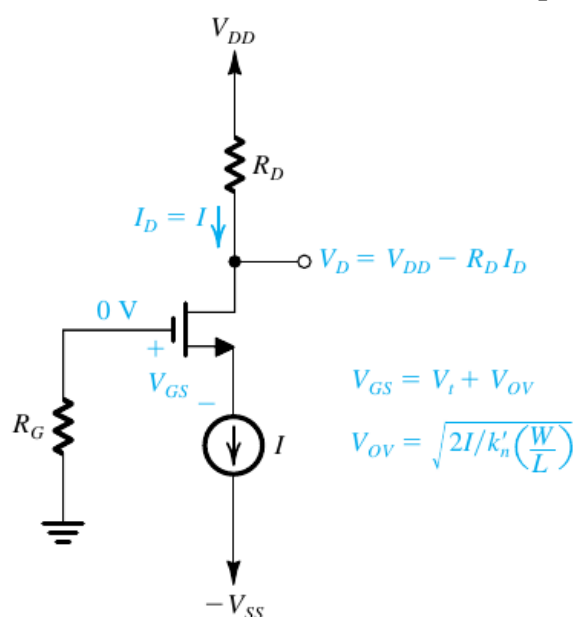


**Figure 5.56** Basic structure of the circuit used to realize single-stage, discrete-circuit MOS amplifier configurations.
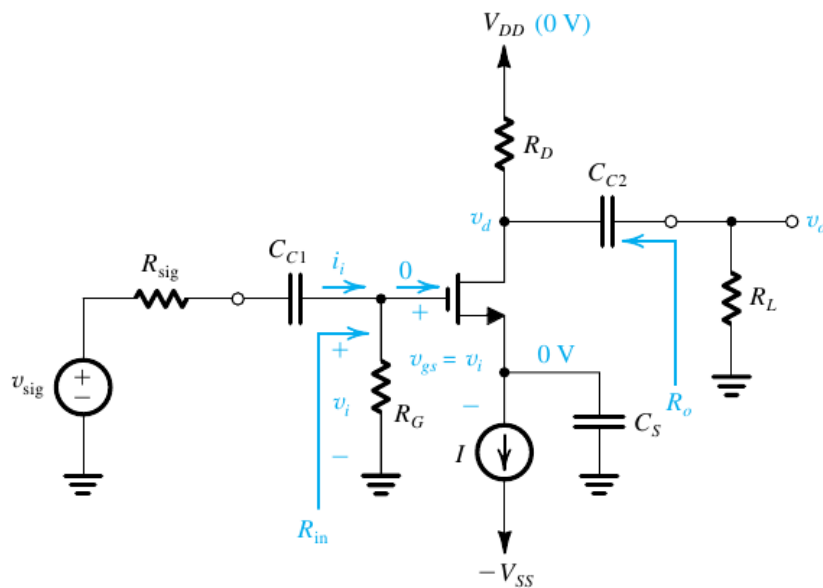
## The Common-Source (CS) Amplifier


- A common-source amplifier realized using the constant-current biasing is shown here
  - here a signal ground (or ac ground) at the source is
    - realized by connecting a capacitor  $C_S$  between the source and ground
    - the value of  $C_S$  should be large enough so as to provide a very low impedance at the desired frequencies

(i.e.  $\frac{1}{j\omega C_S}$  should be very small)




(a)

- this capacitor  $C_S$  thus acts as a short circuit for the ac signal frequencies
  - the signal current passes through  $C_S$  to ground and thus bypass the output resistance of current source  $I$
  - $C_S$  is therefore called a bypass capacitor
    - $C_{C1}$  is used to couple the ac signal source to the gate of MOSFET
      - this capacitor blocks dc and acts as a short circuit at ac and is called a coupling capacitor
- $C_{C2}$  is also a coupling capacitor which is utilized to connect the load to the drain terminal
  - As a consequence of the coupling and bypass capacitors,
    - the dc equivalent circuit stays the same as the basic constant-current source biasing circuit
- As a consequence of the coupling and bypass capacitors,
  - the dc equivalent circuit stays the same as the basic constant-current source biasing circuit

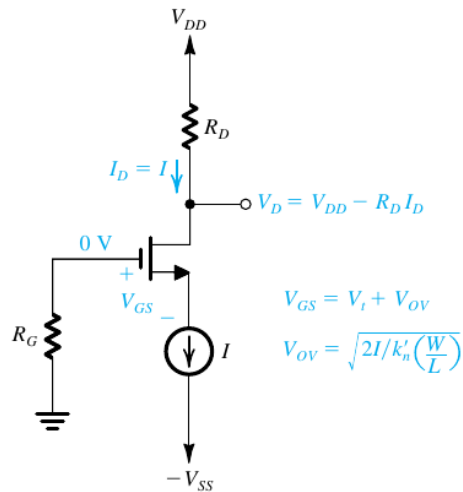


**Figure 5.56** Basic structure of the circuit used to realize single-stage, discrete-circuit MOS amplifier configurations.

- Now to determine the terminal characteristics of the CS amplifier (i.e.  $R_{in}$ ,  $R_o$ ,  $A_v$ ,  $G_v$ ),
  - we replace the CS amplifier by its equivalent small-signal circuit
  - i.e. we replace the MOSFET by its small-signal model
    - suppress the dc sources
    - replace capacitors by short-circuits (if  $\frac{1}{j\omega C} \rightarrow 0$ )

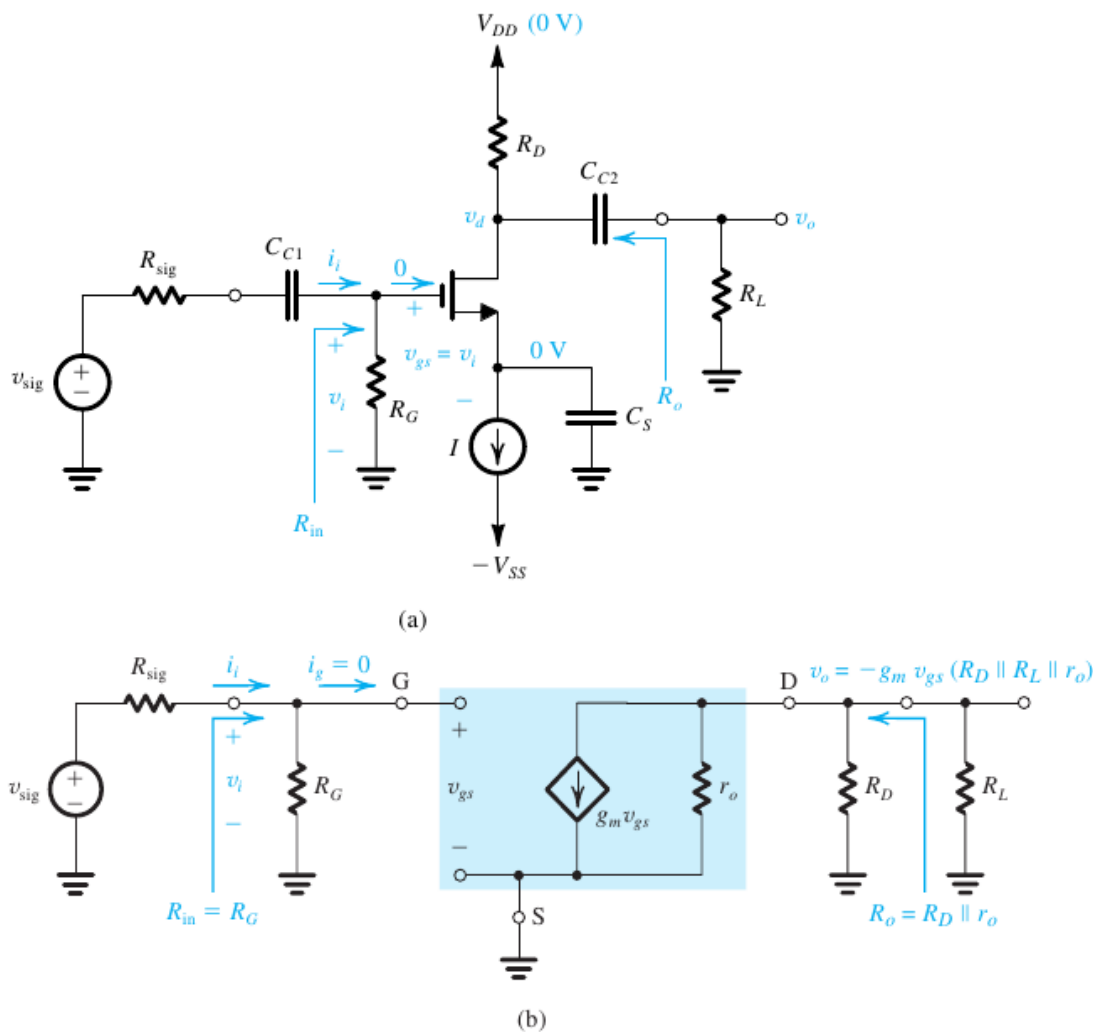


**Figure 5.57** (a) Common-source amplifier based on the circuit of Fig. 5.56. (b) Equivalent circuit of the amplifier for small-signal analysis.

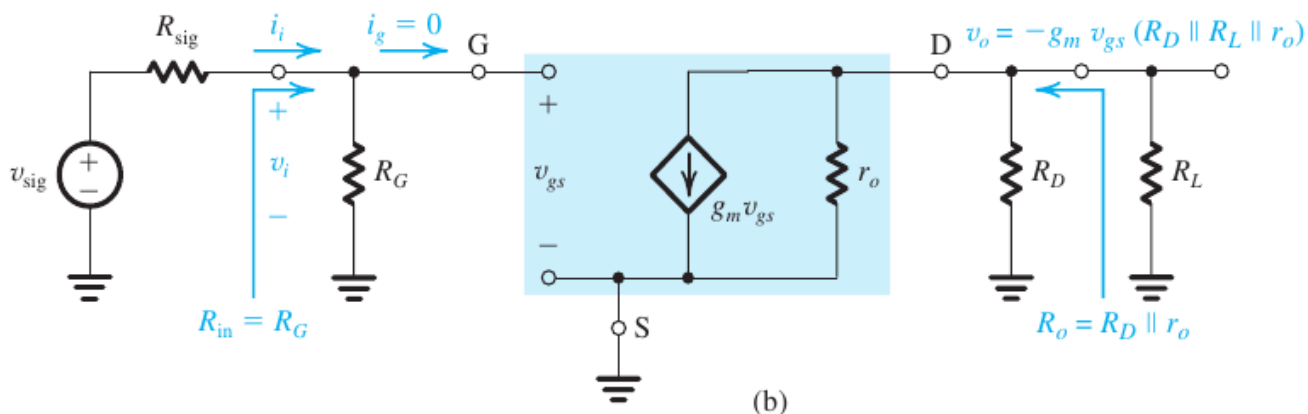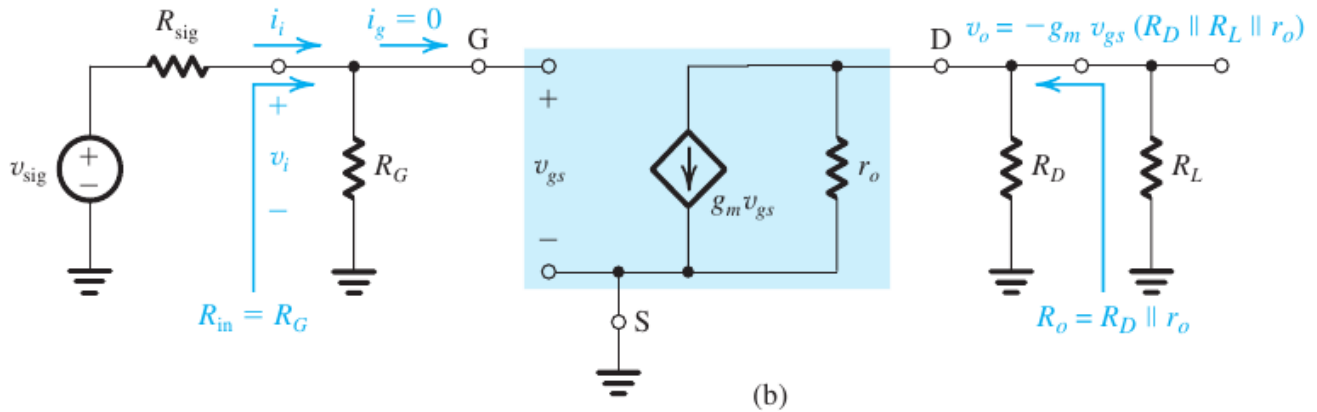- here the input resistance ,  $R_{in} = R_G$ 
  - to determine  $R_o$ 
    - we apply a test source at the output, suppress the independent sources i.e.  $v_i = 0$
    - $v_{gs} = v_i$
    - $v_i = 0 \Rightarrow v_{gs} = 0 \Rightarrow g_m v_{gs} = 0$
    - $\Rightarrow R_o = R_D \parallel r_o$




- $A_v = \frac{v_o}{v_i}$ 
  - as  $r_o$ ,  $R_D$  and  $R_L$  are in parallel
    - $\Rightarrow -g_m v_{gs} = \frac{v_o}{r_o \parallel R_D \parallel R_L}$
    - or  $-g_m (r_o \parallel R_D \parallel R_L) = \frac{v_o}{v_{gs}}$
  - As  $v_{gs} = v_i \Rightarrow A_v = \frac{v_o}{v_i} = -g_m (r_o \parallel R_D \parallel R_L)$
  - and  $A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L \rightarrow \infty} = -g_m (r_o \parallel R_D)$




- $G_v = \frac{v_o}{v_{sig}} = \frac{v_i}{v_{sig}} \frac{v_o}{v_i} = \frac{v_i}{v_{sig}} A_v$ 
  - by voltage divider  $v_i = \frac{R_G}{R_G + R_{sig}} v_{sig}$
  - $\Rightarrow G_v = \frac{v_i}{v_{sig}} A_v = \frac{R_G}{R_G + R_{sig}} A_v$
  - As  $A_v = -g_m (r_o \parallel R_D \parallel R_L)$
  - $\Rightarrow G_v = \left( \frac{R_G}{R_G + R_{sig}} \right) \left[ -g_m (r_o \parallel R_D \parallel R_L) \right]$
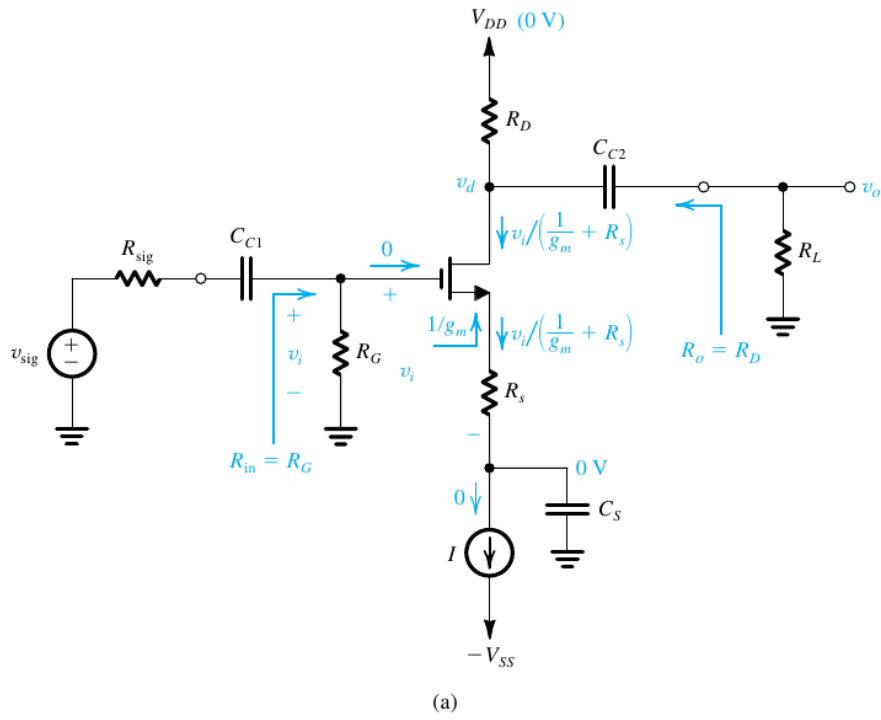
## The Common-Source Amplifier with a Source Resistance


- the Common-source amplifier with a source resistance, utilizing the constant-current biasing scheme is shown in figure



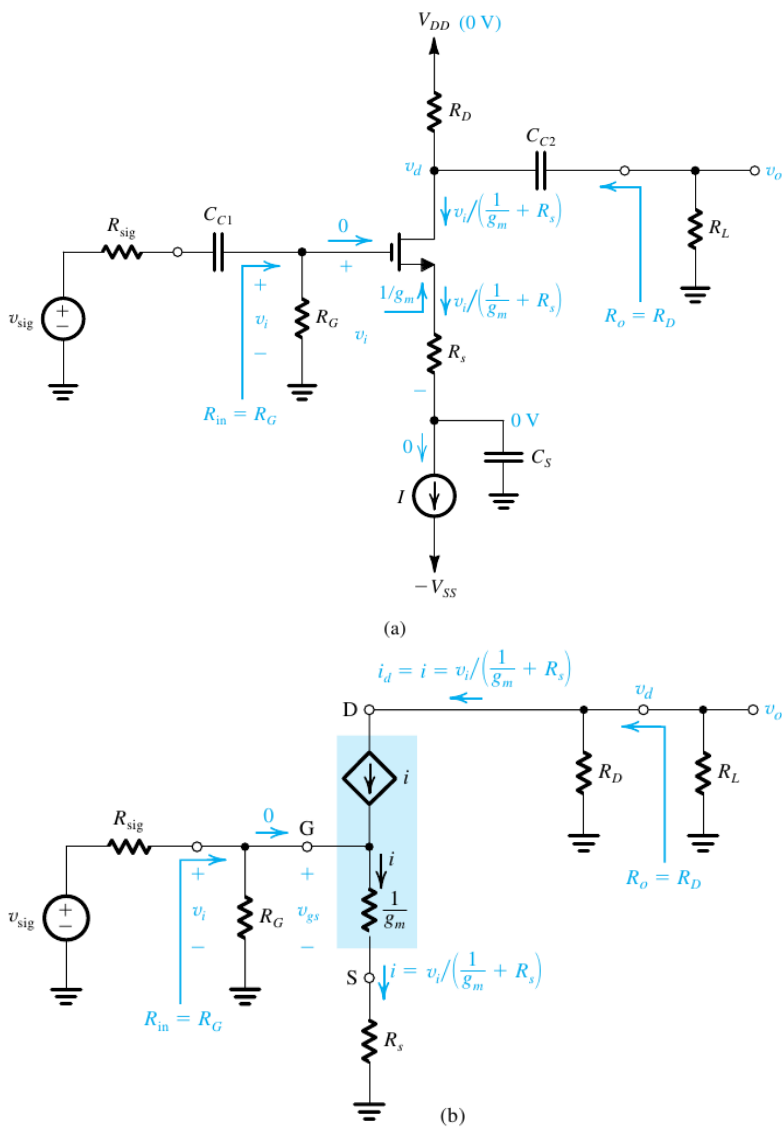- small signal equivalent circuit for fig a, can be given as



- here  $R_{in} = R_G$

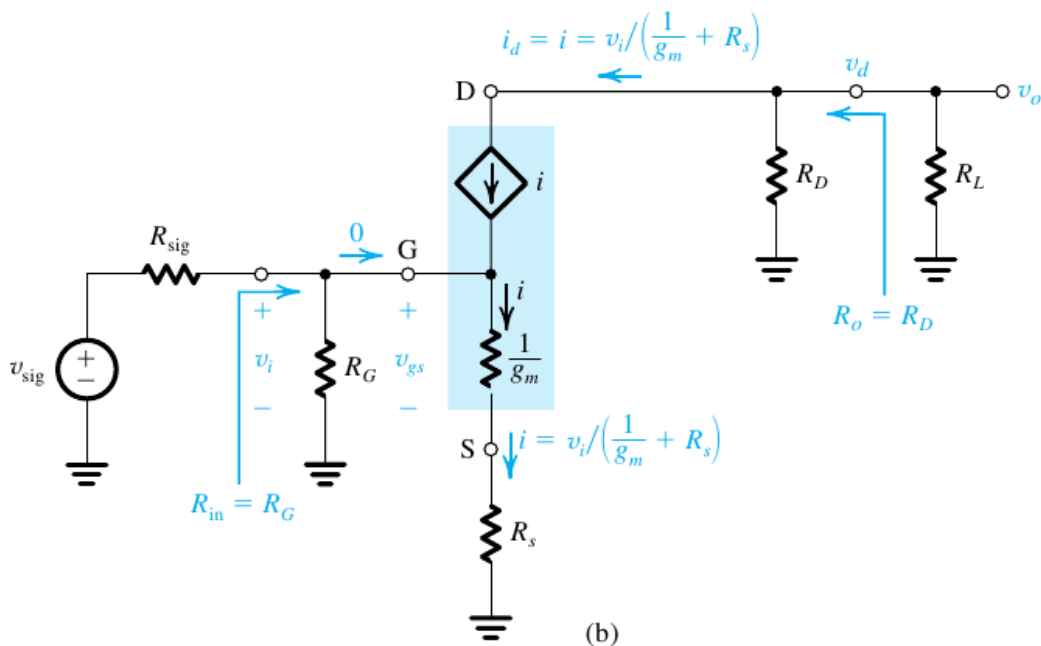


- here  $v_{gs} = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_s} v_i$  ,  $v_i = \frac{R_G}{R_G + R_{sig}} v_{sig}$

◦  $\Rightarrow v_{gs} = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_s} \frac{R_G}{R_G + R_{sig}} v_{sig} \Rightarrow$  if  $v_{sig} = 0$  then  $v_{gs} = 0$


- to determine  $R_o$ , we set  $v_i = 0 \Rightarrow v_{gs} = 0 \Rightarrow g_m v_{gs} = 0$  or  $i = 0$

◦  $\Rightarrow R_o = R_D$

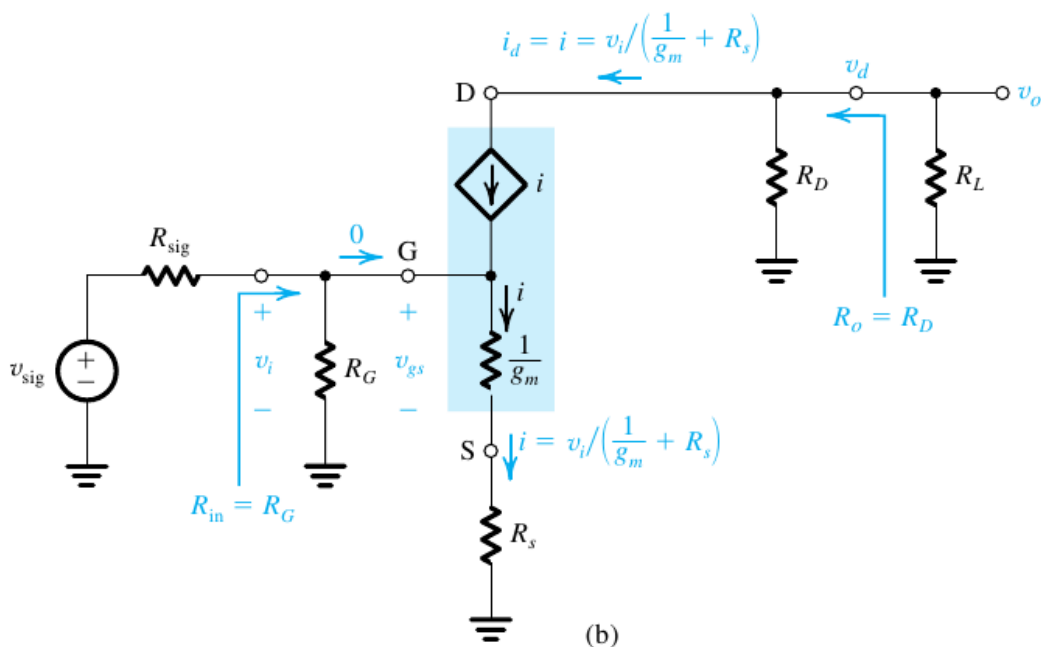

- $i = \frac{v_i}{\frac{1}{g_m} + R_s} = -\frac{v_o}{R_D || R_L}$


◦  $\Rightarrow \frac{v_o}{v_i} = \frac{-R_D || R_L}{\frac{1}{g_m} + R_s} = A_v \Rightarrow A_{vo} = . A_v |_{R_L \rightarrow \infty} = \frac{-R_D}{\frac{1}{g_m} + R_s}$

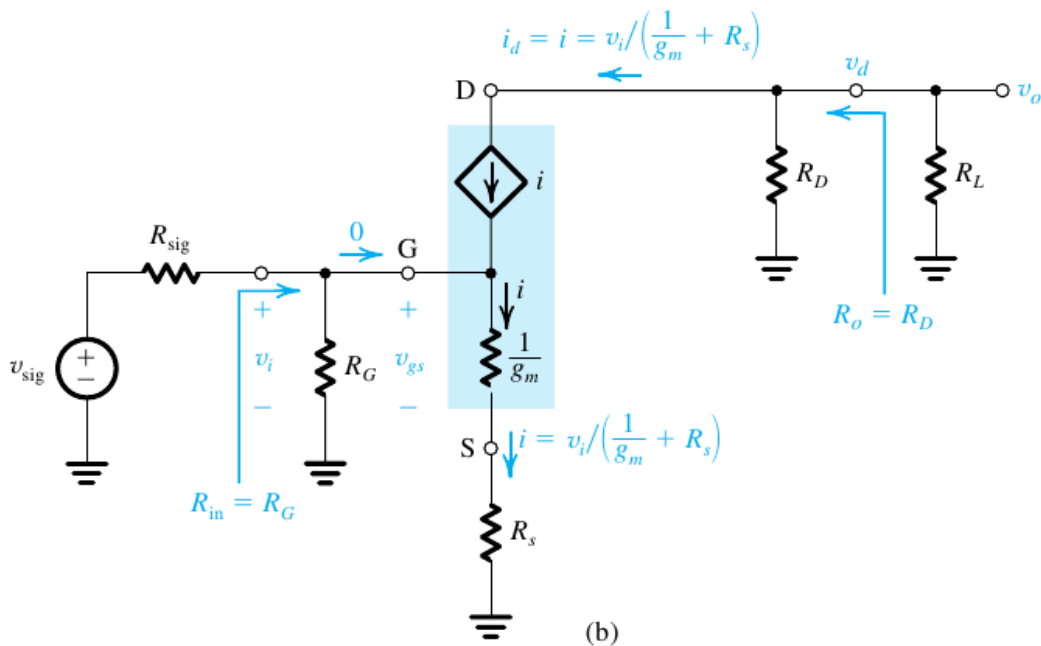

- $G_v = \frac{v_o}{v_{sig}} = \frac{v_i}{v_{sig}} \frac{v_o}{v_i} = \frac{R_G}{R_G + R_{sig}} \frac{v_o}{v_i} \because v_i = \frac{R_G}{R_G + R_{sig}} v_{sig}$
- $G_v = \frac{R_G}{R_G + R_{sig}} A_v = \frac{R_G}{R_G + R_{sig}} \left( \frac{-R_D || R_L}{\frac{1}{g_m} + R_S} \right)$


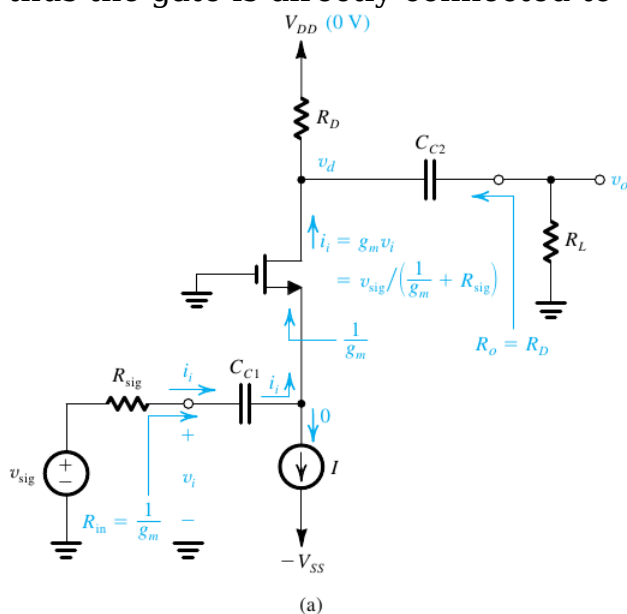
## The Common-Gate (CG) Amplifier

- here both the dc and ac voltages at the gate are to be zero,
  - thus the gate is directly connected to the ground




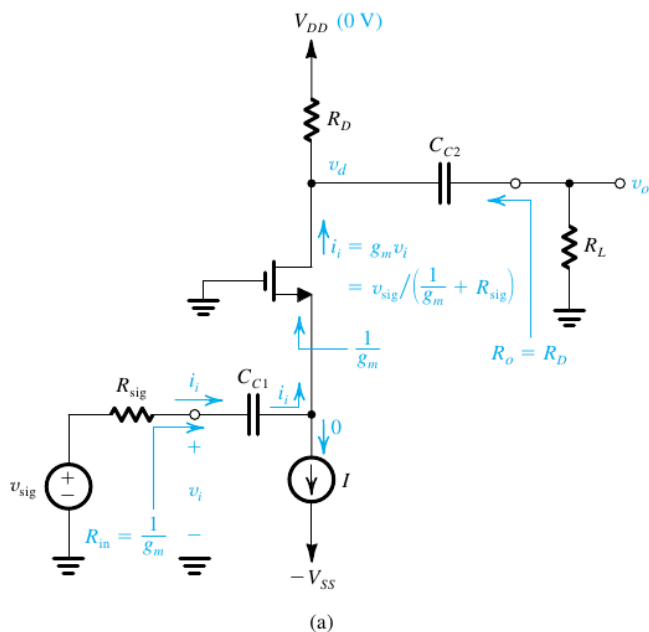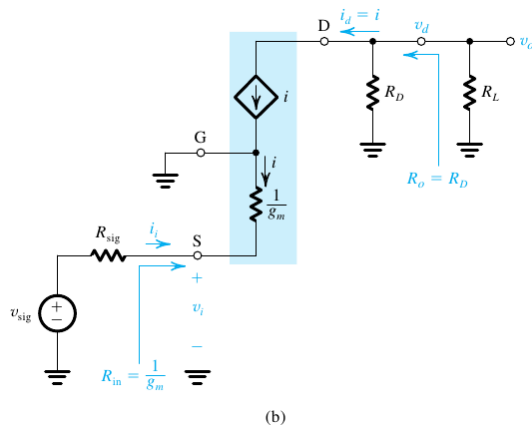- the small-signal equivalent circuit can be given as





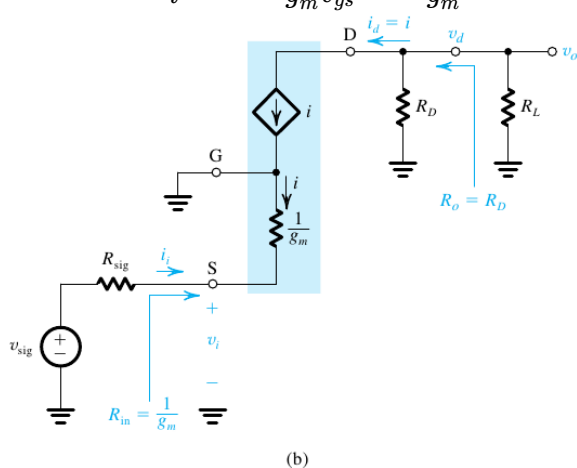
- here  $R_{in} = \frac{v_i}{i_i} = \frac{v_i}{-i} = \frac{-v_{gs}}{-i} \because v_i = -v_{gs}$
- $R_{in} = \frac{-v_{gs}}{-i} = \frac{-v_{gs}}{-g_m v_{gs}} = \frac{1}{g_m}$




- by voltage divider

- $v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig} = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_{sig}} v_{sig}$
- and  $v_i = -v_{gs}$

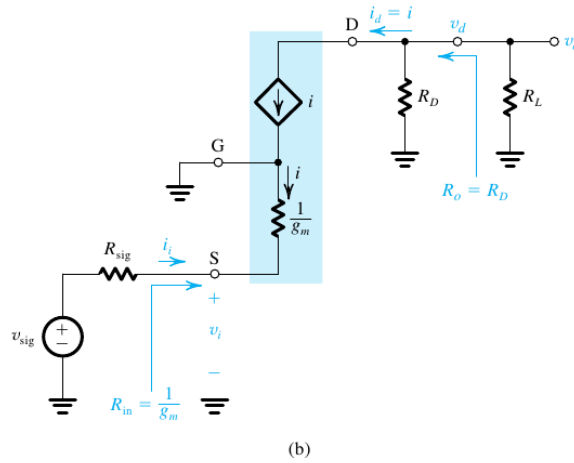
- to determine  $R_o$ , we apply test source at the output and set  $v_i = 0$
- $v_i = 0 \Rightarrow v_{gs} = -v_i = 0 \Rightarrow g_m v_{gs} = 0$  or  $i = 0$
- $\Rightarrow R_o = R_D$



- $i = g_m v_{gs} = \frac{-v_o}{R_D \parallel R_L}$ 
  - as  $v_{gs} = -v_i$ 
    - $\Rightarrow i = -g_m v_i = \frac{-v_o}{R_D \parallel R_L}$ 
      - or  $v_o = g_m (R_D \parallel R_L) v_i$
    - $\Rightarrow A_v = \frac{v_o}{v_i} = g_m (R_D \parallel R_L)$
    - and  $A_{vO} = A_v |_{R_L \rightarrow \infty} = g_m R_D$

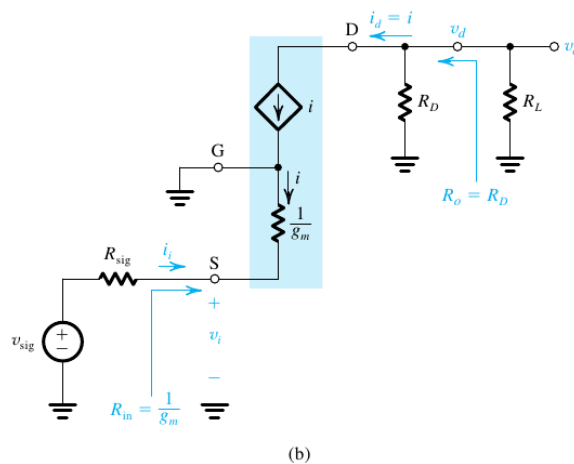


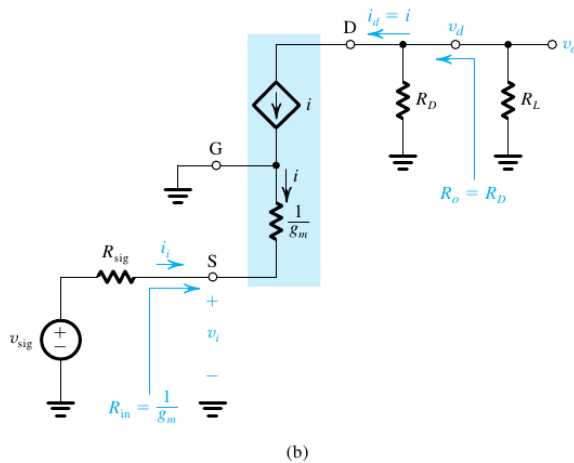- $A_v = \frac{v_o}{v_i} = g_m (R_D \parallel R_L)$ 
  - $G_v = \frac{v_o}{v_{sig}} = \frac{v_i}{v_{sig}} \frac{v_o}{v_i} = \frac{v_i}{v_{sig}} A_v$ 
    - $\Rightarrow G_v = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_{sig}} A_v = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_{sig}} g_m (R_D \parallel R_L)$
    - or  $G_v = \frac{R_D \parallel R_L}{\frac{1}{g_m} + R_{sig}}$




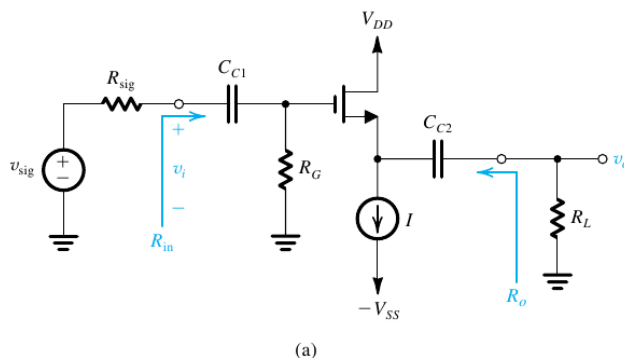
## The Source Follower

- In this common drain amplifier,
  - As the drain is to function as a signal ground, there is no need for resistor  $R_D$
  - therefore  $R_D$  has been eliminated
    - the input signal is applied via  $C_{C1}$  to the MOSFET gate
    - the output signal is taken at the MOSFET source and is coupled to the load  $R_L$  via  $C_{C2}$



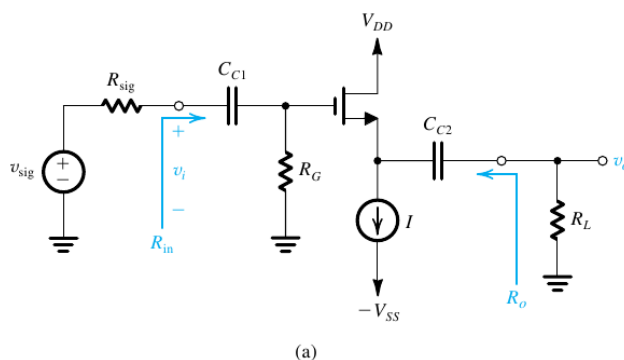
- Small signal equivalent circuit for this amplifier can be obtained
  - by replacing MOSFET with its T-model,
    - by suppressing dc sources
    - and by replacing capacitors by short circuits (as  $\frac{1}{j\omega C}$  is very small at the frequency of interest)




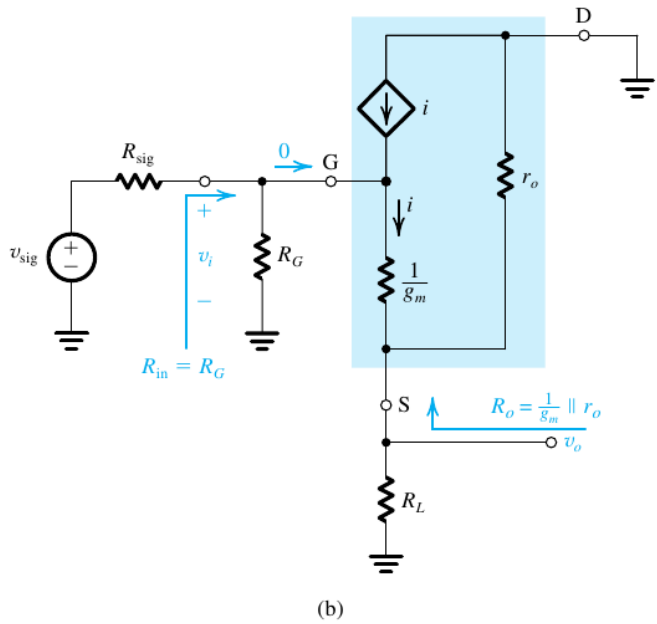

- here  $R_{in} = R_G$
- $R_o$ :

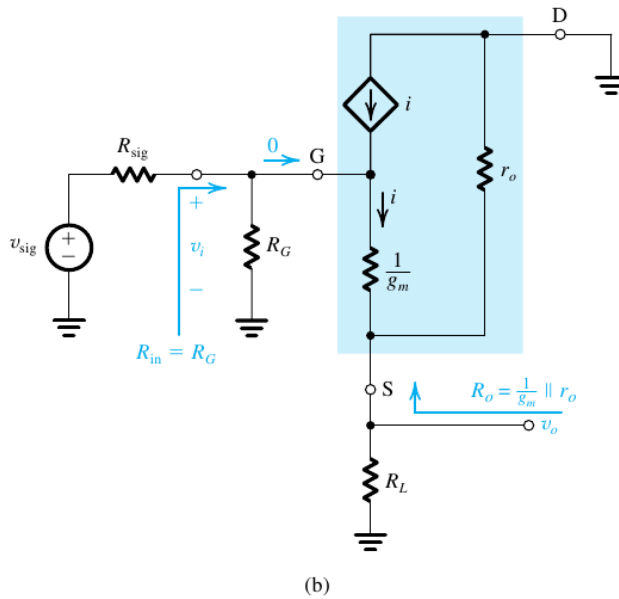- to determine  $R_o$  , we set  $v_i = 0$
- Remove  $R_L$  and apply a test source
  - $v_i = 0 \Rightarrow v_g = 0$



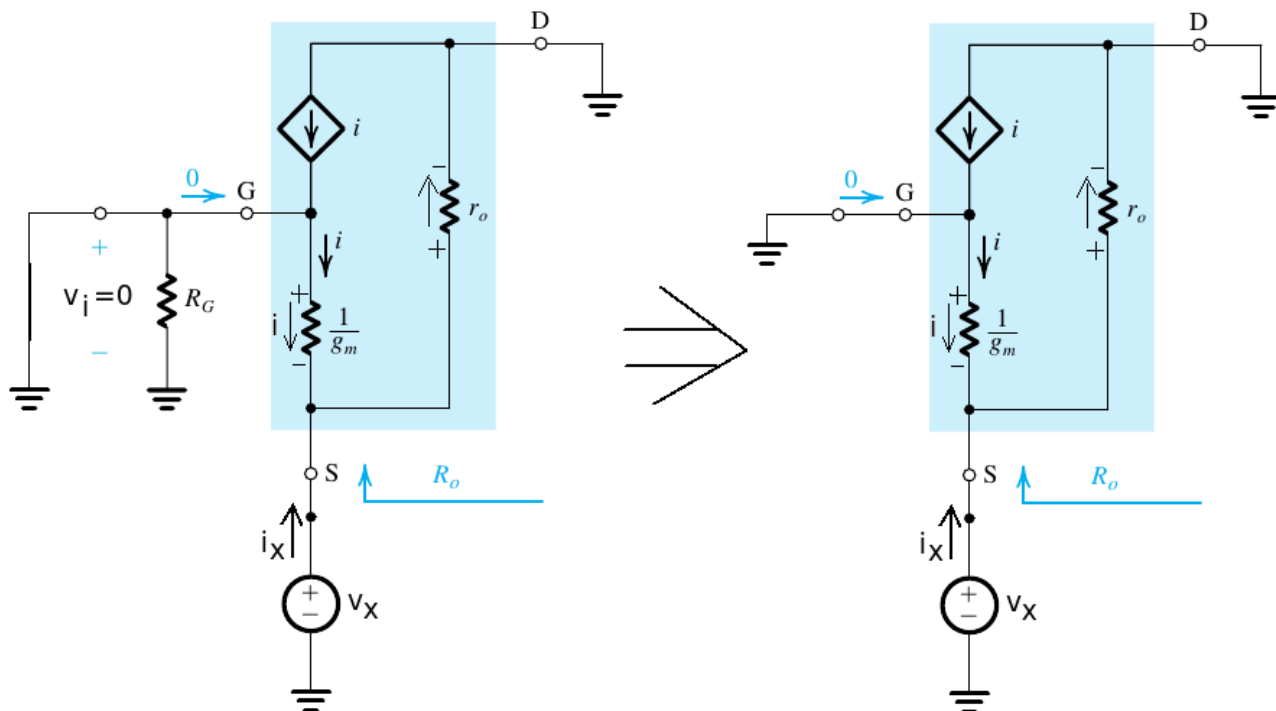

• KCL at MOSFET Source terminal

○  $\Rightarrow i_x + i = \frac{v_x - 0}{r_o} \Rightarrow i_x = \frac{v_x}{r_o} - i$

○ Ohm's Law across resistor  $\frac{1}{g_m}$

■  $\Rightarrow v_g - v_s = \frac{1}{g_m} i$

$\Rightarrow i = g_m(v_g - v_s) = g_m(0 - v_x) = -g_m v_x$

○ eliminating i from above 2 equations

■  $\Rightarrow i_x = \frac{v_x}{r_o} - i = \frac{v_x}{r_o} - (-g_m v_x)$


■  $i_x = \frac{v_x}{r_o} + g_m v_x = v_x \left( \frac{1}{r_o} + g_m \right)$

■  $\frac{i_x}{v_x} = \frac{1}{r_o} + g_m$

■  $\Rightarrow R_o = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_o} + g_m} = \frac{1}{\frac{1}{r_o} + \frac{1}{1/g_m}} = r_o \parallel \left( \frac{1}{g_m} \right)$

$R_{out}$ :

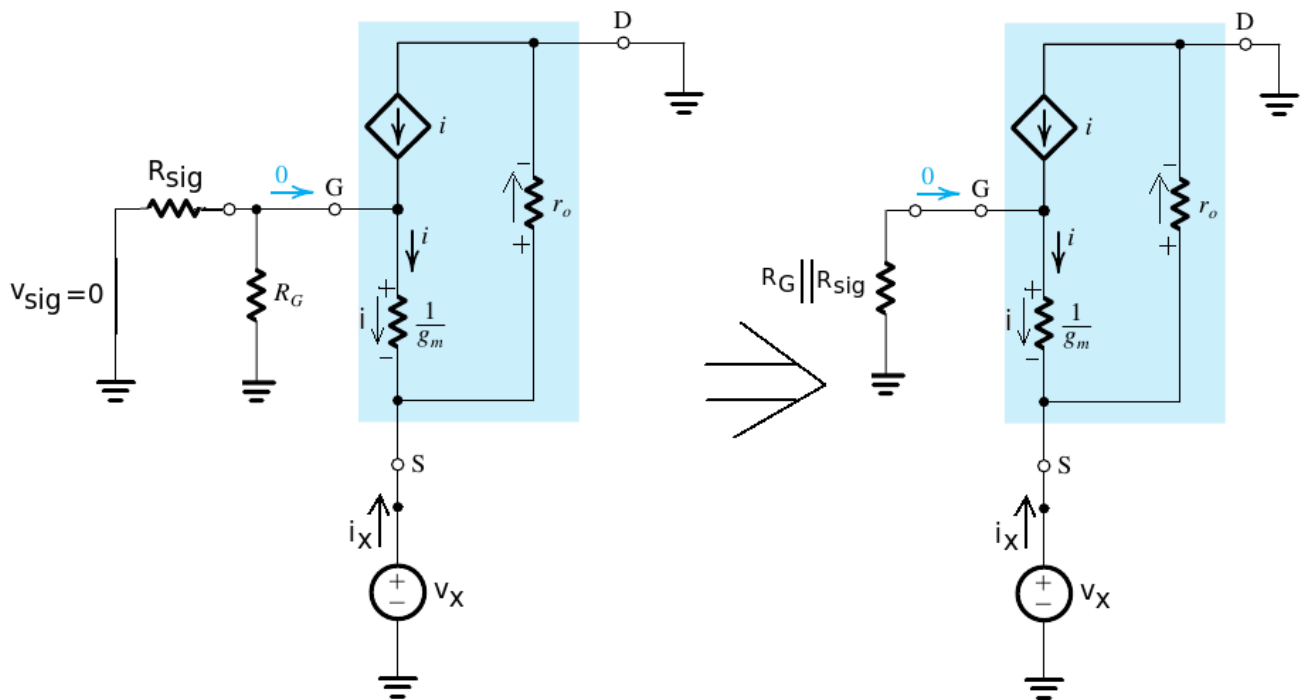- to determine  $R_{out}$ , we set  $v_{sig} = 0$ , disconnect  $R_L$  and apply a test source at the source terminal of MOSFET



• KCL at MOSFET Source terminal

○  $\Rightarrow i_x + i = \frac{v_x - 0}{r_o} \Rightarrow i_x = \frac{v_x}{r_o} - i$

○ Ohm's Law across resistor  $\frac{1}{g_m}$

■  $\Rightarrow v_g - v_s = \frac{1}{g_m} i \Rightarrow i = g_m (v_g - v_s)$

■  $\Rightarrow i = g_m (0 - v_x) = -g_m v_x \therefore i_g = 0 \Rightarrow v_g = 0$

○ eliminating i from above 2 equations

■  $\Rightarrow i_x = \frac{v_x}{r_o} - i = \frac{v_x}{r_o} - (-g_m v_x)$

■  $i_x = \frac{v_x}{r_o} + g_m v_x = v_x \left( \frac{1}{r_o} + g_m \right)$

■  $\frac{i_x}{v_x} = \frac{1}{r_o} + g_m$

■  $\Rightarrow R_{out} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_o} + g_m} = \frac{1}{\frac{1}{r_o} + \frac{1}{(1/g_m)}} = r_o \parallel \left( \frac{1}{g_m} \right)$

$A_v$ :

• By KVL

○  $v_i = v_{gs} + v_o = \left( \frac{1}{g_m} \right) i + v_o$


■ but  $i = \frac{v_o}{R_L \parallel r_o}$

■  $\Rightarrow v_i = \frac{1}{g_m} \left( \frac{v_o}{R_L \parallel r_o} \right) + v_o$

■  $v_i = v_o \left( \frac{1}{g_m (R_L \parallel r_o)} + 1 \right)$


■  $v_i = v_o \left( \frac{1 + g_m (R_L \parallel r_o)}{g_m (R_L \parallel r_o)} \right)$

- $A_v = \frac{v_o}{v_i} = \frac{g_m(R_L \parallel r_o)}{1 + g_m(R_L \parallel r_o)}$
- $A_{vo} = . A_v |_{R_L \rightarrow \infty} = \frac{g_m r_o}{1 + g_m r_o}$

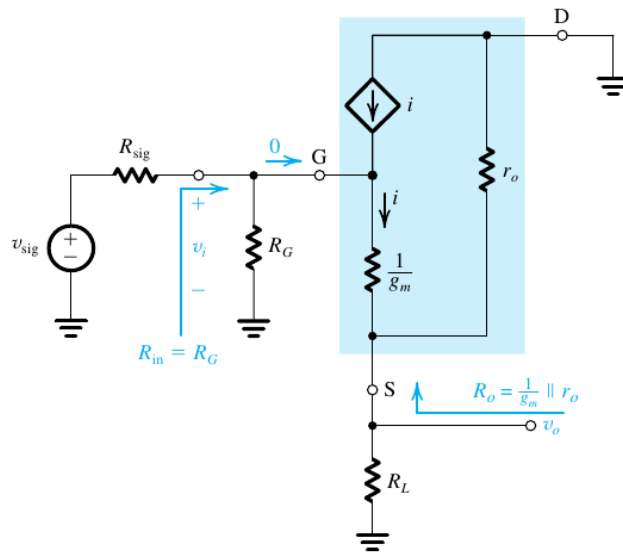

(b)

- $A_v = \frac{v_o}{v_i} = \frac{g_m(R_L \parallel r_o)}{1 + g_m(R_L \parallel r_o)}$
- $G_v = \frac{v_o}{v_{sig}} = \frac{v_i}{v_{sig}} \frac{v_o}{v_i} = \frac{v_i}{v_{sig}} A_v = \frac{v_i}{v_{sig}} \frac{g_m(R_L \parallel r_o)}{1 + g_m(R_L \parallel r_o)}$ 
  - o by voltage divider  $v_i = \frac{R_G}{R_G + R_{sig}} v_{sig}$
  - $\Rightarrow G_v = \frac{R_G}{R_G + R_{sig}} \frac{g_m(R_L \parallel r_o)}{1 + g_m(R_L \parallel r_o)}$
  - or  $G_v = \frac{R_G}{R_G + R_{sig}} \left( \frac{R_L \parallel r_o}{\frac{1}{g_m} + R_L \parallel r_o} \right)$

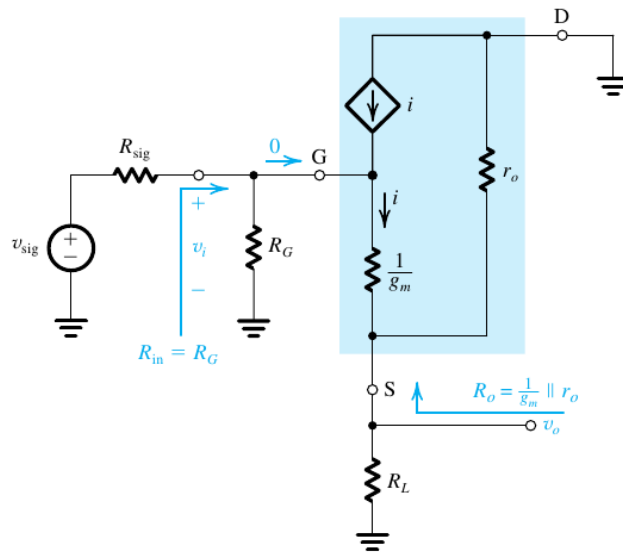


(b)

## The Amplifier Frequency Response

- Uptill now, we have considered the gain of MOSFET to be constant,

- and independent of the frequency of the input signal, which is not true
- A MOSFET has a finite bandwidth (i.e. the gain of MOSFET is depends upon the frequency of the input signal)
- fig shows the frequency response of a CS amplifier (i.e. gain is plotted versus frequency)

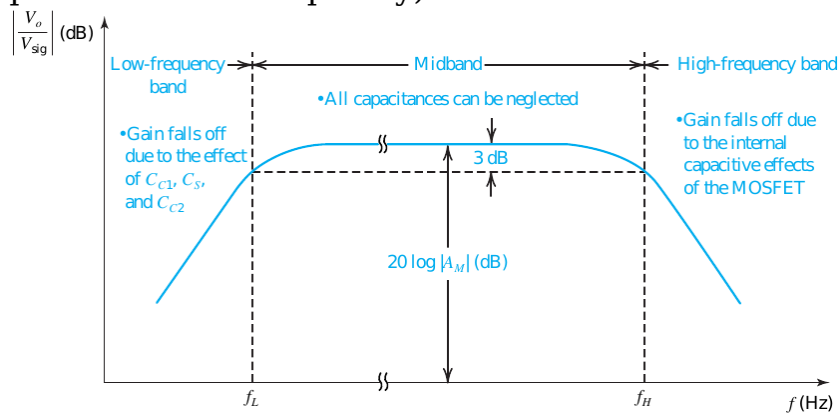

**Figure 5.61** A sketch of the frequency response of a CS amplifier delineating the three frequency bands of interest.


- Note that there is a wide frequency range over which the gain remains almost constant
  - this is the useful frequency range (called the midband) of operation for a particular amplifier
- At lower frequencies, the magnitude of amplifier gain falls off
  - because the coupling capacitors, no longer have low impedances
    - i.e.  $\frac{1}{j\omega C}$  is large at low frequencies
- At higher frequencies, the gain falls off because of the internal capacitive effects in the MOSFET
  - thus for every MOS amplifier, there is a finite band over which the gain is almost constant.
  - the boundaries of this useful frequency band (called midband), are the two frequencies  $f_L$  and  $f_H$
- Note that at  $f_L$  and  $f_H$ , the gain drops by 3dB below its value at midband
  - thus the amplifier 3dB bandwidth can be defined as
    - $BW = f_H - f_L$
  - as  $f_L < f_H \Rightarrow BW \approx f_H$
- A figure of merit for the amplifier is its gain-bandwidth product i.e.  $GB = |A_M| BW$ 
  - where  $|A_M|$  is the magnitude of the amplifier gain in the midband
    - this relation  $\Rightarrow$  in amplifier design, it should be possible to trade off gain for bandwidth


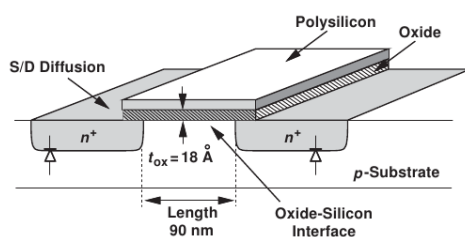
## The Role of the Substrate-The Body Effect

- Thus far, it has been assumed that the source and body terminals are connected  $\Rightarrow V_{SB} = 0$ 
  - with  $V_{SB} = 0$ , the MOSFET behaves as if it were a three terminal device
  - However, in integrated circuits, the substrate is common to many MOS transistors.
  - In order to maintain the cutoff condition for all the substrate to drain/source junctions,
  - the substrate is connected to the most negative power supply in an NMOS circuit (the most +ve power supply for PMOS devices)

$$\blacksquare \Rightarrow V_{SB} \neq 0$$



$$\bullet V_{SB} \neq 0$$

- this non-zero value of  $V_{SB}$  affects the i-v characteristics of the MOSFET, by changing its threshold voltage.
- this effect is called the body effect and can be modeled as (for an NMOS)

$$\blacksquare V_t = V_{t0} + \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$\blacksquare \text{ where } V_{t0} \text{ is the threshold voltage for } V_{SB} = 0$$

$$\blacksquare \phi_f \text{ is a physical parameter (with } 2\phi_f \text{ typically } 0.6\text{V)}$$

- $\gamma$  is a fabrication parameter given by

$$\blacksquare \gamma = \frac{\sqrt{2qN_A\epsilon_S}}{C_{ox}}, \text{ where } q \text{ is the electron charge}$$

$$\blacksquare N_A \text{ is the doping concentration of the p-type substrate}$$

$$\blacksquare \epsilon_S \text{ is the permittivity of silicon} = 11.7\epsilon_o$$

- the parameter  $\gamma$  has the dimension of  $\sqrt{V}$  and is typically  $0.4V^{1/2}$

- for a PMOS transistor

$$\circ V_{tp} = V_{t0} + \gamma \left[ \sqrt{2\phi_f + V_{BS}} - \sqrt{2\phi_f} \right]$$

$$\blacksquare \text{ here } \gamma \text{ is -ve and is given as } \gamma = -\frac{\sqrt{2qN_D\epsilon_S}}{C_{ox}}$$


$$\blacksquare \text{ where } N_D \text{ is the doping concentration of the n-well in which PMOS is formed}$$

- for PMOS transistor

- $2\phi_f$  is typically 0.75V
- $\gamma$  is typically  $-0.5V^{\frac{1}{2}}$
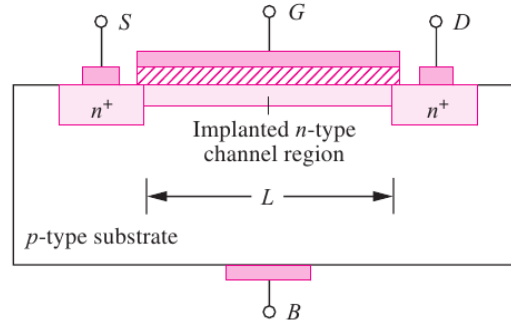
## The Depletion-Type MOSFET

- The structure of depletion-type MOSFET is similar to the
  - enhancement-type MOSFET with one important difference
  - The depletion MOSFET has a physically implanted channel



- (b)
  - thus an n-channel depletion-type MOSFET has a built-in n-type channel
    - in the device so that the  $n^+$  drain and  $n^+$  source regions are
    - connected through this channel even when  $v_{GS} = 0$
  - $\Rightarrow$  if a voltage  $v_{DS}$  is applied between the drain and source, a current  $i_D$  flows for  $v_{GS} = 0$
  - A negative voltage must be applied to the gate,  $v_{GS}$  to deplete the n-type channel region
    - and eliminate the current path between the source and drain
    - (hence the name depletion-type MOSFET)
- thus for depletion-type MOSFET, applying a +ve  $v_{GS}$  enhances
  - the channel by attracting more electrons into it
  - and by applying a -ve  $v_{GS}$ , electrons can be repelled from
    - the channel and thus the channel will become shallower
  - i.e. the -ve  $v_{GS}$  deplete the channel of its charge carriers
    - and this mode of operation (-ve  $v_{GS}$ ) is called depletion mode
  - As  $v_{GS}$  is made more -ve, a value is reached at which
    - the channel is completely depleted of charge carriers  $\Rightarrow i_D = 0$
  - and this value of  $v_{GS}$  is the threshold voltage of the n-channel depletion type MOSFET
- thus the depletion-type MOSFET can be operated
  - in the enhancement mode by applying a +ve  $v_{GS}$

- and in the depletion mode by applying a -ve  $v_{GS}$


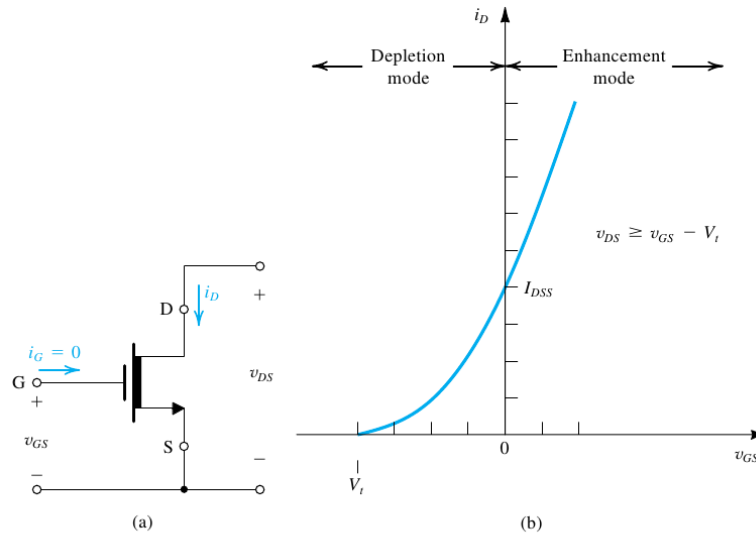


Figure 5.63 The circuit symbol (a) and the  $i_D$ - $v_{GS}$  characteristic in saturation; (b) for an n-channel depletion-type MOSFET.

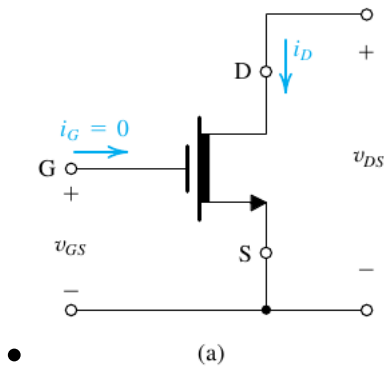

- Note that the device symbol denotes the existing channel
  - via the shaded area next to the vertical line
- the  $i_D - v_{DS}$  characteristics for this device are the same as those for the enhancement type MOSFET
  - except for the negative  $V_{tn}$

